

# Processor Data Path and Control

CIT 595  
Spring 2007

## What Do We Know?

Already discovered:

- Gates (AND, OR..)
- Combinational logic circuits (decoders, mux)
- Memory (latches, flip-flops)
- Sequential logic circuits (state machines)
- Simple processors (programmable traffic sign)


What's next?

- Apply all this to build a working processor

CIT 595

7 - 2


## Von Neumann Model

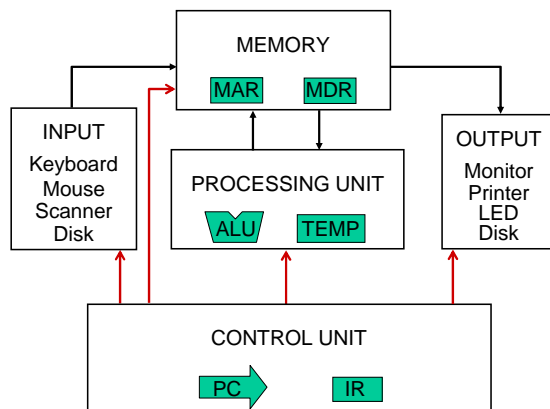

CIT 595

7 - 3

## LC-3 Processor Von Nuemann Model

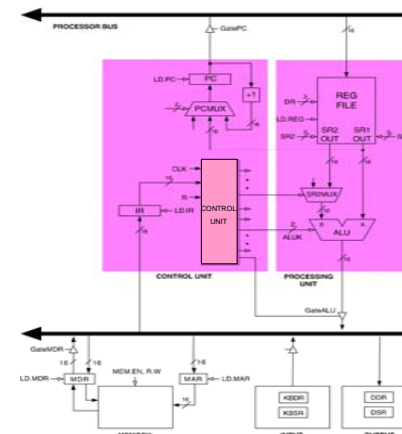


CIT 595

7 - 4

## LC-3 Data Path

The **data path** of a computer is all the logic used to process information

Filled arrow = info to be processed.  
Unfilled arrow = control signal.

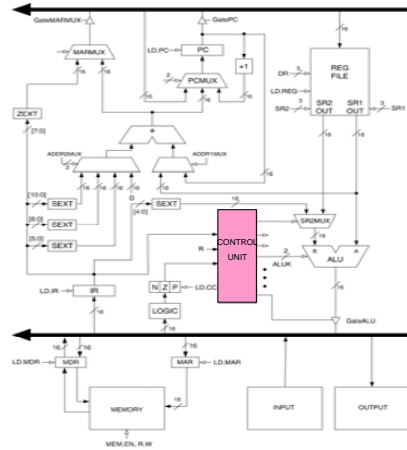

CIT 595


7 - 5

## One More Device

Tri-state buffer

- NOT an inverter!
- Device with a special output that can take a *third* state (i.e. besides 0 and 1)

| E | D | Q |
|---|---|---|
| 1 | 0 | 0 |
| 1 | 1 | 1 |
| 0 | 0 | Z |
| 0 | 1 | Z |

 

Z = "high impedance" state

Allows wires to be "shared"

- Alternative to mux
- Only one source may drive at a time!
- Usually used to control data over a bus

CIT 595

7 - 6

## Data Path Components

Global bus

- Set of wires that carry 16-bit signals to many components
- Inputs to bus are controlled by triangle structure called tri-state devices
  - Place signal on bus when enabled
  - Only one (16-bit) signal should be enabled at a time
  - Control unit decides which signal "drives" the bus
- Any number of components can read bus
  - Register only captures bus data if write-enabled by the control unit


Memory and I/O

- Control signals and data registers for memory and I/O devices
- Memory: MAR, MDR (also control signal for read/write)
- Input (keyboard): KBSR, KBDR
- Output (text display): DSR, DDR

CIT 595

7 - 7

## LC-3 Data Path

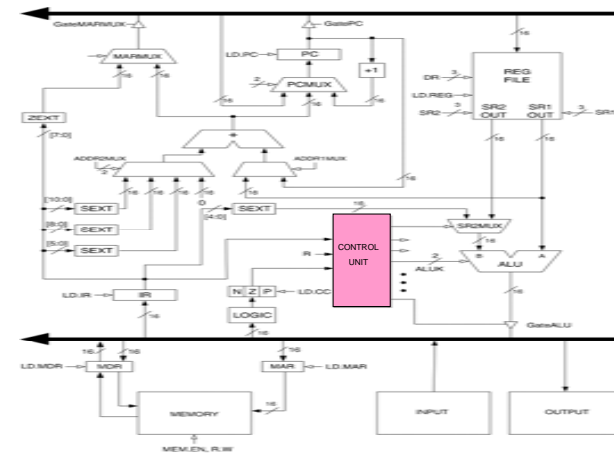

CIT 595

Filled arrow = info to be processed. Unfilled arrow = control signal.

7 - 8

## Data Path Components (cont.)

### ALU

- Input: register file or sign-extended bits from IR (immediate field)
- Output: bus; used by...
  - Condition code registers
  - Register file
  - Memory and I/O registers

### Register File

- Two read addresses, one write address (3 bits each)
- Input: 16 bits from bus
  - Result of ALU operation or memory (or I/O) read
- Outputs: two 16-bit
  - Used by ALU, PC, memory address
  - Data for store instructions passes through ALU

CIT 595

7 - 9

## Data Path Components (contd..)

### PC and PCMUX

- Three inputs to PC, controlled by PCMUX
  1. Current PC plus 1 (normal operation)
  2. Adder output (BR, JMP, ...)
  3. Bus (TRAP)

### MAR and MARMUX

- Some inputs to MAR, controlled by MARMUX
  1. Zero-extended IR[7:0] (used for TRAP; more later)
  2. Adder output (LD, ST, ...)

CIT 595

7 - 10

## Data Path Components (cont..)

### Condition Code Logic

- Looks at value (from ALU) on bus and generates N, Z, P signals
- N,Z,P Registers are set only when control unit enables them

### Control Unit

- For each stage in instruction processing decides:
  - Who drives the bus?
  - Which registers are write enabled?
  - Which operation should ALU perform?

Lets Look at Instruction Processing next..

CIT 595

7 - 11

## Instructions

Fundamental unit of work

Constituents





- *Opcode*: operation to be performed
- *Operands*: data/locations to be used for operation

Encoded as a sequence of bits (*just like data!*)

- Sometimes have a fixed length (e.g., 16 or 32 bits)
- Atomic: operation is either executed completely, or not at all


CIT 595

7 - 12

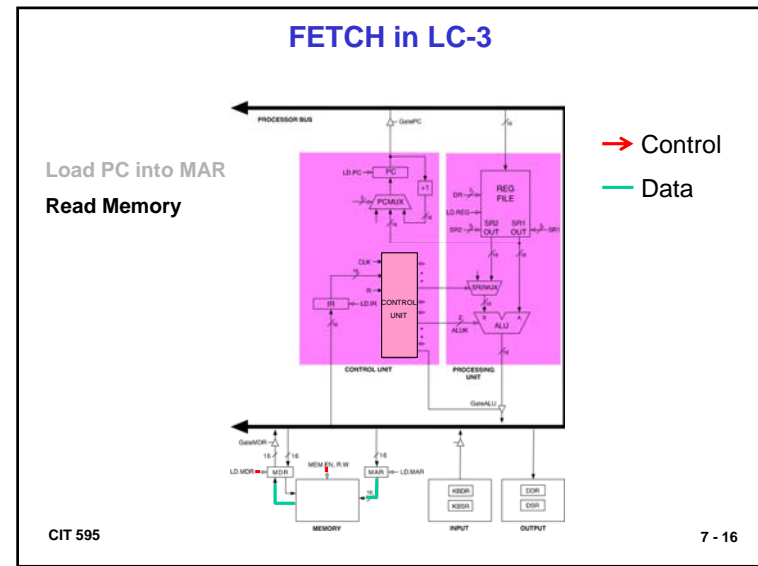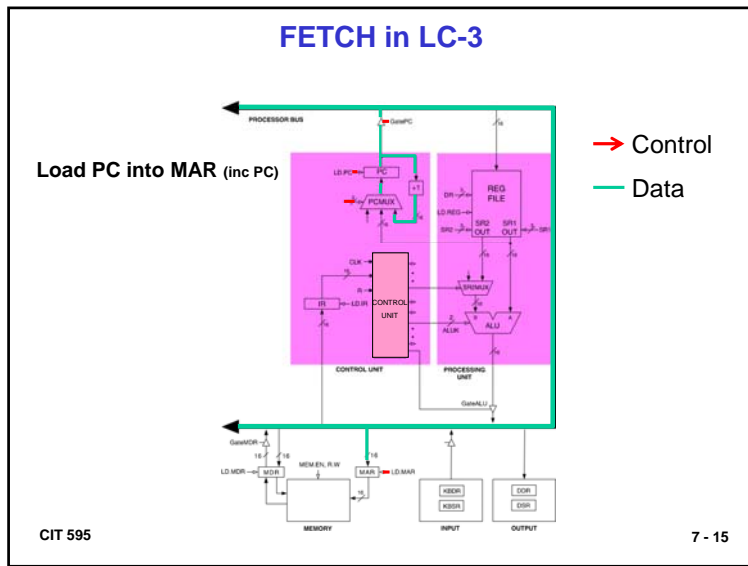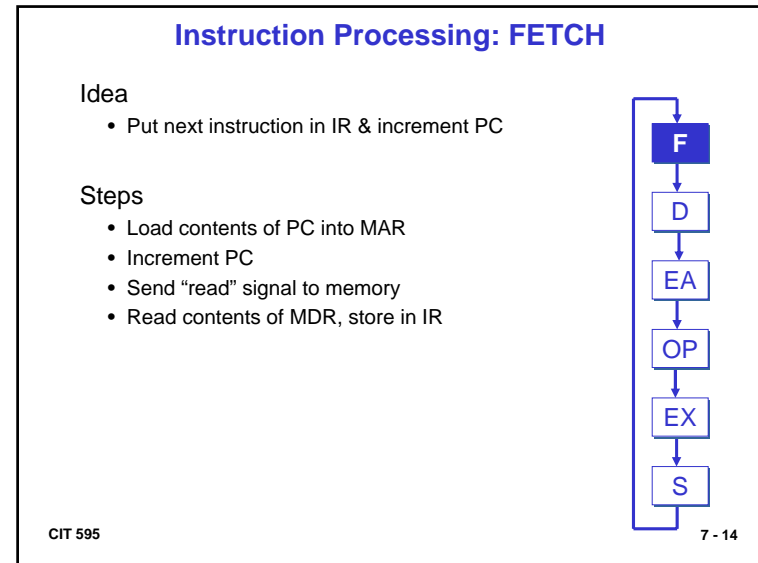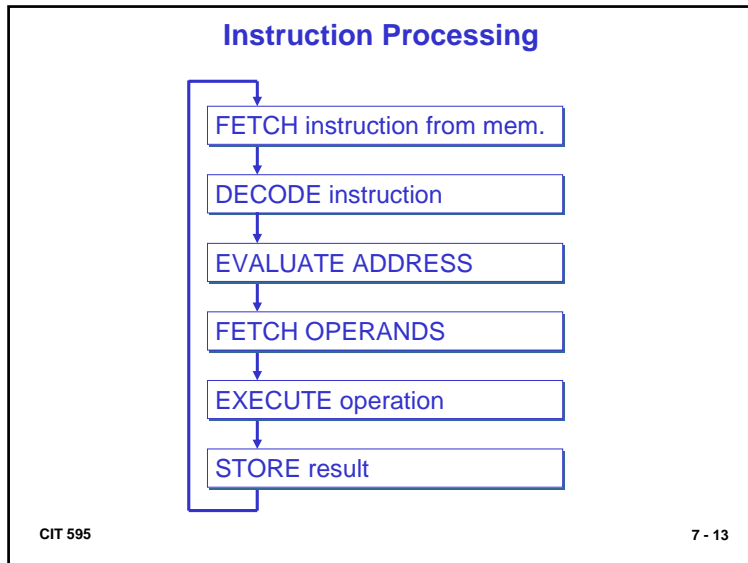
 
### FETCH in LC-3

Load PC into MAR  
Read Memory  
Copy MDR into IR



→ Control  
— Data

CIT 595

7 - 17


### Instruction Processing: DECODE

Identify opcode

- In LC-3, always first four bits of instruction
- 4-to-16 decoder asserts control line corresponding to desired opcode

Identify operands from the remaining bits

- Depends on opcode  
e.g., for LDR, last six bits give offset  
e.g., for ADD, last three bits name source operand #2

 


CIT 595

7 - 18

### DECODE in LC-3

Decoding usually a part of the Control Unit but can be separate

 

CIT 595

7 - 19


### Instruction Processing: EVALUATE ADDRESS

Compute address

- For loads and stores
- For control-flow instructions

Examples

- Add offset to base register (as in LDR)
- Add offset to PC (as in LD and BR)

 


CIT 595

7 - 20

### EVALUATE ADDRESS in LC-3

Load/Store

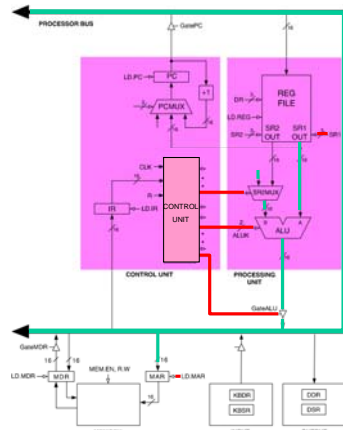

CIT 595

7 - 21

### Instruction Processing: FETCH OPERANDS

Get source operands for operation

Examples

- Read data from register file (ADD)
- Load data from memory (LDR)




CIT 595

7 - 22

### FETCH OPERANDS in LC-3

ADD

 


CIT 595

7 - 23

### FETCH OPERANDS in LC-3

LDR

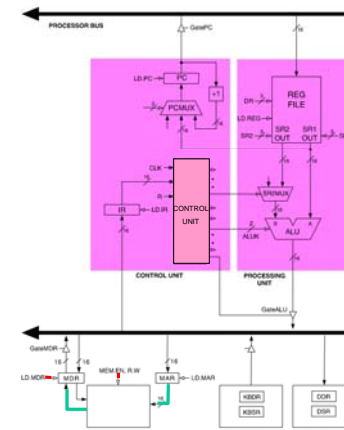

CIT 595


7 - 24

## Instruction Processing: EXECUTE

Actually perform operation

Examples

- Send operands to ALU and assert ADD signal
- Do nothing (e.g., for loads and stores)

 


CIT 595

7 - 25

## EXECUTE in LC-3

ADD

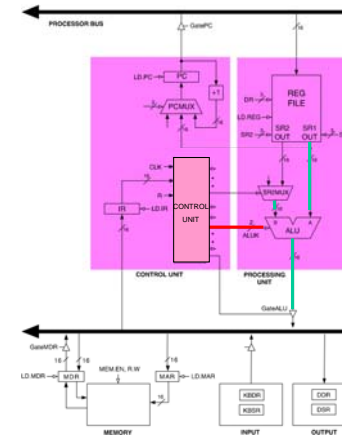

CIT 595

7 - 26


## Instruction Processing: STORE

Write results to destination

- Register or memory

Examples

- Result of ADD is placed in destination reg.
- Result of load instruction placed in destination reg.
- For store instruction, place data in memory
  - Set MDR
  - Assert WRITE signal to memory

 


CIT 595

7 - 27




## STORE in LC-3

ADD

 

CIT 595

7 - 28

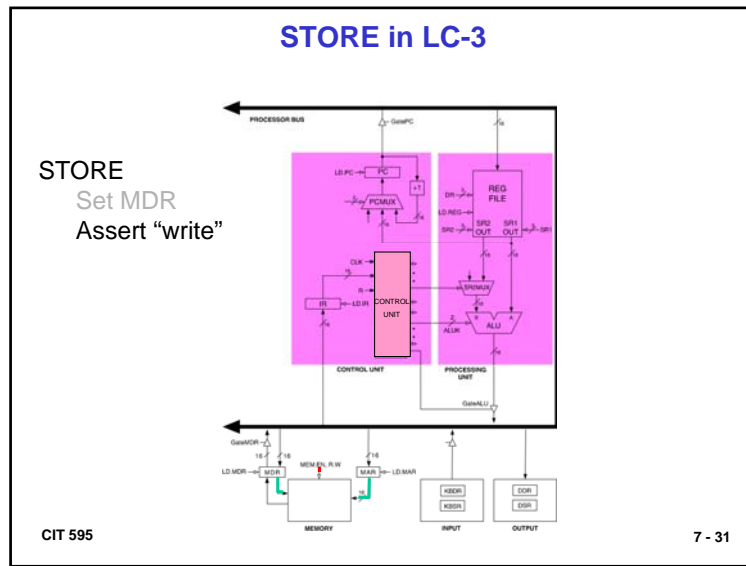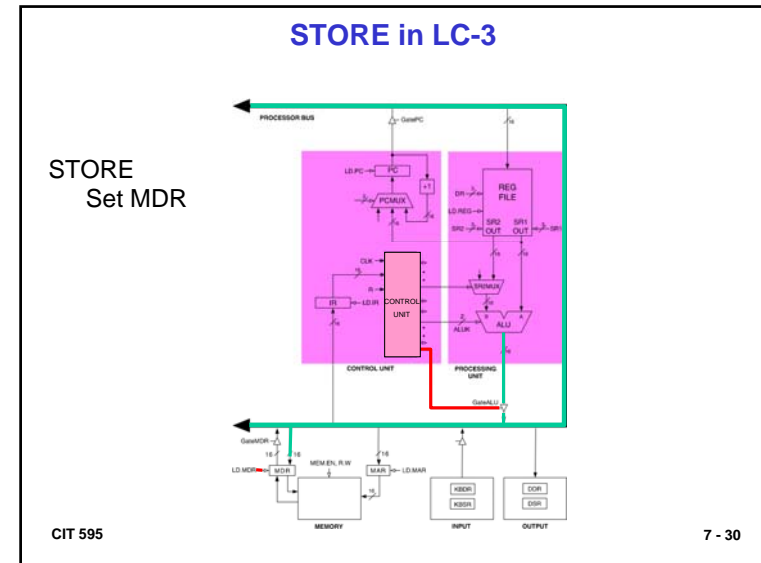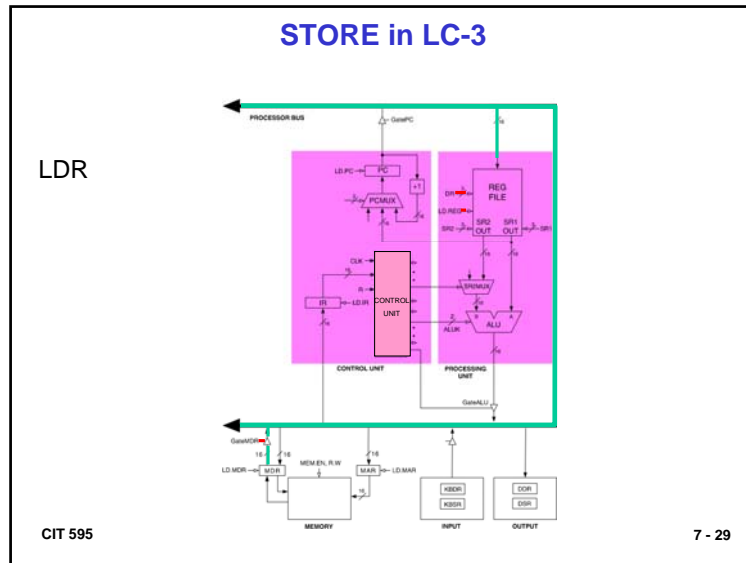

- ### Time to Complete One Instruction
- It takes fixed number of clock ticks (repetition of rising or falling edge) to execute each instruction
    - The time interval between ticks is known as **clock cycle**
    - Thus instruction performance is measured in clock cycles
  - Hence the clock sequences **each phase** of an instruction by raising the right signals as the right time
  - So what determines the time between ticks i.e. the length of the clock cycle?
- CIT 595 7 - 32



## Clocking Methodology


- Defines when **signals** can be read and when they can be written
- It is important to specify the timing of reads and writes because, if a value is written at the same time it is read, the value of read could be old, new or mix of both
- All values are stored on clock edge (edge-triggered) i.e. within a defined interval of time (length of the clock cycle)
- In a processor, since only memory elements can store values this means that
  - Any collection of combinational logic must have its inputs coming from a set of memory elements and its outputs written into a set of memory elements

CIT 595

7 - 33
 
## Clocking Methodology (contd..)

- The length of the clock cycle is determined as follows:



- The time necessary for the signals to reach memory element 2 defines the length of the clock cycle
  - i.e. minimum clock cycle time must be at least as great as the maximum propagation delay of the circuit

CIT 595

7 - 34

## How does the control unit work ?

### Two approaches:

- Hardwired Control
- Microprogrammed Control


CIT 595

7 - 35

## Approach I: Hardwired Control

### Hardwired Control


- Directly connects the control lines to actual machine instructions
- The instructions are divided into fields, and bits in the fields are connected to input lines that drives the various digital logic components
- The control signals are some combination of the instruction bit plus other signals such as interrupts, or condition codes from previous instruction

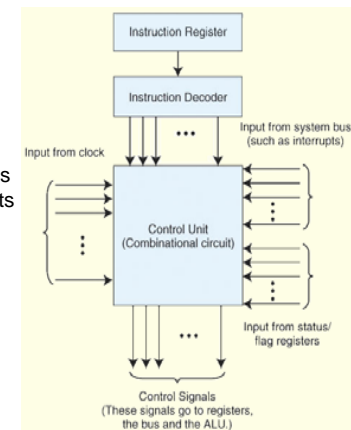

CIT 595

7 - 36
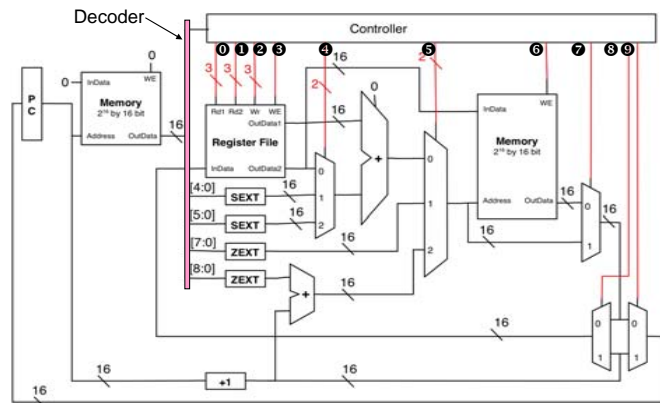
## LC3 as Hardwired Control Implementation




The Control Signals (red colored lines) are outputs by some combination of inputs from the instruction bit fields

CIT 595

7 - 37

## ADD Instruction

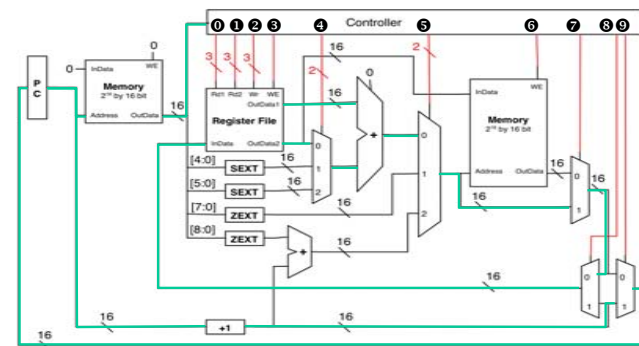

|       | Opcode   |      | Control |        |         |   |    |    |   |   |   |   |
|-------|----------|------|---------|--------|---------|---|----|----|---|---|---|---|
| Instr | I[15:12] | I[5] | 0       | 1      | 2       | 3 | 4  | 5  | 6 | 7 | 8 | 9 |
| ADD   | 0001     | 0    | I[8:6]  | I[2:0] | I[11:9] | 1 | 00 | 00 | 0 | 1 | 0 | 1 |

CIT 595

7 - 38

## Sequencing the Stages in Hardwired Implementation

- The combination Control Unit set all the control lines needed by an instruction
- How do we ensure that we sequence through Instruction cycle i.e. F->D->EA->OP->EX->S?
  - We connect the clock to a synchronous counter and the counter to the decoder
  - The decoder output enabled is based on counter outputs (i.e. which cycle you are in)
  - The decoder output is then used as enable signal (gating) to enable only certain control signals during a particular cycle
  - Note: the diagram does not show sequencing logic to avoid cluttering the diagram

CIT 595

7 - 39

## Sequencing Instruction Stages in Hardwired Implementation (contd..)


Example:

- Suppose the max. number of cycles an instruction takes is 8
- Then we would have 3-bit counter whose outputs are fed into 3 x 8 decoder
- The output of the decoder,  $T_0$  to  $T_7$  are enable based on count i.e.
  - $T_0 = 1$  when count = 000 (cycle 0), all others are disabled
  - ...
  - $T_7 = 1$  when count = 111 (cycle 7), all others are disabled
- The decoder output that is enabled used to define the behavior in a particular cycle
- If < 8 clock cycles are required by another instr., then the counter is reset back to 0 (so the next instruction can properly function as well)

CIT 595

7 - 40


### Hardwire Control with Timing (Sequencing) Control

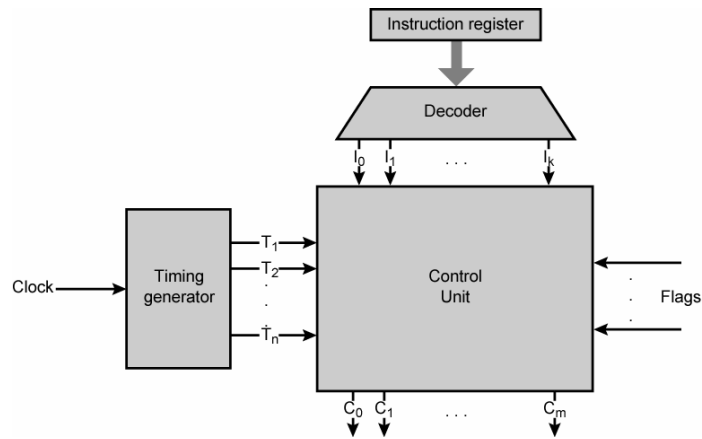

CIT 595

7 - 41

### JMP Instruction

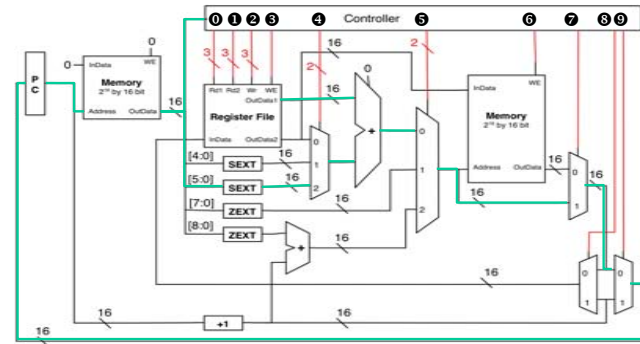


|       | Opcode   |      | Control |   |   |   |    |    |   |   |   |   |
|-------|----------|------|---------|---|---|---|----|----|---|---|---|---|
| Instr | I[15:12] | I[5] | 0       | 1 | 2 | 3 | 4  | 5  | 6 | 7 | 8 | 9 |
| JMP   | 1100     | -    | I[8:6]  | - | - | 0 | 10 | 00 | 0 | 1 | x | 0 |

CIT 595

7 - 42

### LDR Instruction

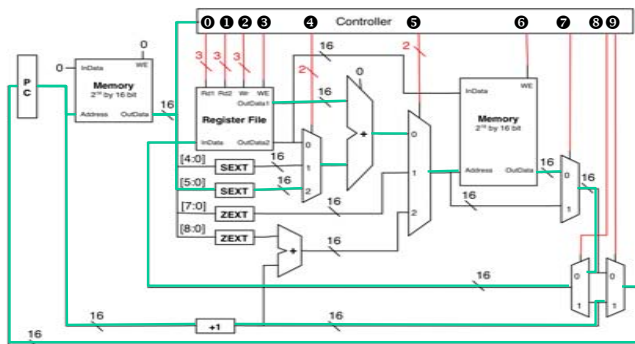

|       | Opcode   |      | Control |   |         |   |    |    |   |   |   |   |
|-------|----------|------|---------|---|---------|---|----|----|---|---|---|---|
| Instr | I[15:12] | I[5] | 0       | 1 | 2       | 3 | 4  | 5  | 6 | 7 | 8 | 9 |
| LDR   | 0110     | -    | I[8:6]  | - | I[11:9] | 1 | 10 | 00 | 0 | 0 | 0 | 1 |


BaseR

DR

CIT 595

7 - 43

### TRAP Instruction

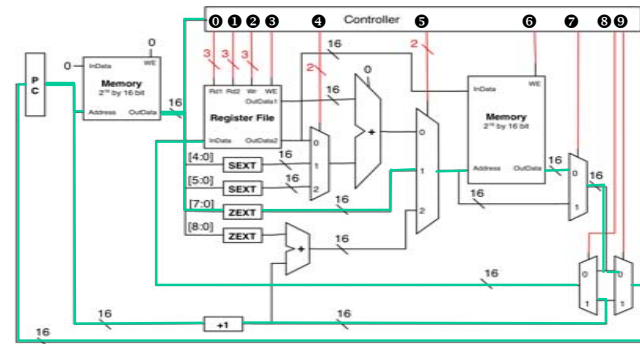


|       | Opcode   |      | Control |   |     |   |    |    |   |   |   |   |
|-------|----------|------|---------|---|-----|---|----|----|---|---|---|---|
| Instr | I[15:12] | I[5] | 0       | 1 | 2   | 3 | 4  | 5  | 6 | 7 | 8 | 9 |
| TRAP  | 1111     | -    | -       | - | 111 | 1 | xx | 01 | 0 | 0 | 1 | 0 |

CIT 595

7 - 44
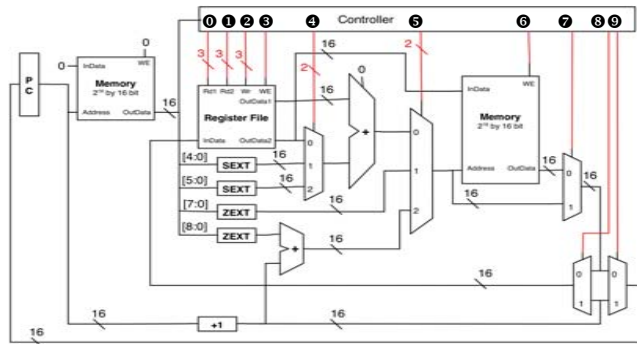
## Implementation Diagram is not complete



What about AND? NOT? BR? What changes would you make?

CIT 595

7 - 45


## Approach II: Microprogrammed Control

- In microprogrammed control, each machine instruction is in turn implemented by a series of microinstructions
- Machine instructions are the input for a microprogram that converts the 1s and 0s of an instruction into control signals
- The microinstructions are often stored in firmware or read only memory, which is also called the control store
- Microprogram is also known as Microcode in some literature
- Microprogram Control is essentially a Finite State Machine

CIT 595

7 - 46

## Microprogrammed Control is a FSM

 

CIT 595

7 - 47

## LC3 Microprogrammed Control: State Diagram


Finite state machine

- Input: PC, IR, etc..
- Output: *many* control signals

Need to map abstract ops to control signals

- E.g.,  $MAR \leftarrow PC$   
 $\Rightarrow$  GatePC and LD.MAR
- E.g.,  $PC \leftarrow PC + 1$   
 $\Rightarrow$  PCMUX=2 and LD.PC

If in state 1, then the **micro-instruction** for state 1 will encode information for GatePC, LD.MAR, PCMUX, LD.PC and next state as state 2

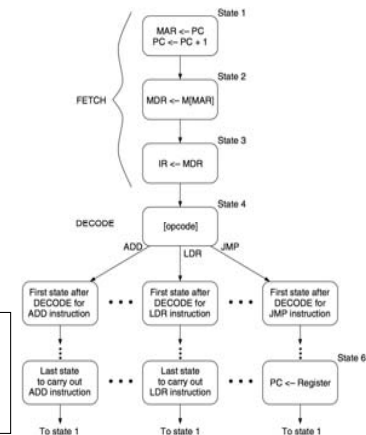


CIT 595

7 - 48
 
## LC3 Implemented using Microprogram Control

- The behavior of LC-3 during a given clock cycle is completely described by the 49 bit microinstruction
  - 39 control signals to assert datapath components
  - 10 signals + 9 other to determine the control signals for the next clock cycle
- Each phase of instruction cycle may require more than one microinstruction
- Hence a microinstruction is retrieved during each clock cycle




Microprogram Control  
7 - 49

CIT 595
 
## LC3 Implemented using Microprogram Control (contd..)


- All possible processor behavior (state) is stored into memory called **Control Store**
  - i.e. each location stores one microinstruction
  - There are 52 possible microinstructions (states) that can describe LC3's behavior
  - Hence need a 6-bit address to lookup the control store
- The microsequencer produces the 6 bit address from combination of 10 bits of Microinstruction + 9 bit additional info, which will correspond to the next behavior of the processor



Microprogram Control  
7 - 50

CIT 595


## Big Picture: LC3 as Microprogrammed Control

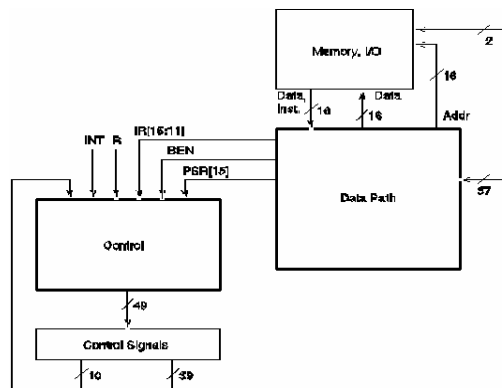

CIT 595

7 - 51

## Appendix C of Patt & Patel Fig C.2

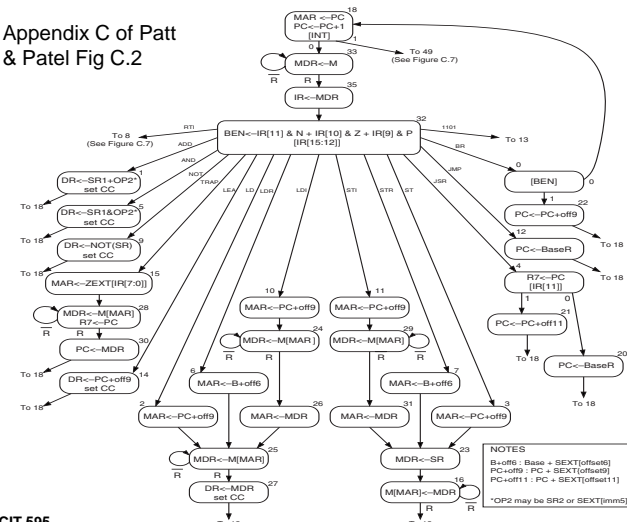

CIT 595

7 - 52

### LC3 Microprogram: Control Signals for Current State

| CURR STATE | GATE  |    |     |     | LD |     |     |     |     | MUX |             |       |         | MISC       |          |     |        |
|------------|-------|----|-----|-----|----|-----|-----|-----|-----|-----|-------------|-------|---------|------------|----------|-----|--------|
|            | MARMX | PC | ALU | MDR | PC | REG | C C | I R | MAR | MAR | PC          | SR2   | SR1     | ALUK       | DR       | R.W | MEM EN |
| 18         | 0     | 1  | 0   | 0   | 1  | 0   | 0   | 0   | 1   | X   | 0<br>(PC+1) | X     | X       | X          | X        | 0   | 0      |
| 1          | 0     | 0  | 1   | 0   | 0  | 1   | 1   | 0   | 0   | X   | X           | IR[5] | IR[8:6] | 0<br>(ADD) | IR[11:9] | 0   | 0      |

The table above provides the control signal values (some of the 39 signals) for two states (18, 1)

State 18: Is performing part of the FETCH stage

State 1: Is performing stages OP-EX-STORE for ADD inst

**Note:**

- Assume all Register and Memory Read/Write signal are set 0 unless in case of write (i.e. set to 1)
- Also there is no need of timing circuit like in hardwired control, as each signal behavior is defined for every clock cycle

CIT 595

7 - 53

### LC3 Microprogram: Next State

Depends on:

- 10 bits of current microinstruction
  - J (6-bits): encodes the next state (mostly likely states of the possible next states)
  - COND (3-bits): field indicates special tests that must occur to compute the true next state
    - 0 – Unconditional (that next state is the encoded state)
    - 1 – Memory Read
    - 2 – Branch
    - 3 – Addressing Mode (for JSR and JSRR instructions)
    - 5 – Interrupt Test
  - IRD (1-bit) : If set to IRD = 1, ignore J and COND. This only happens in state 32 and as we want to use the bits from the IR to select the next state

CIT 595

7 - 54

### LC3 Microprogram: Next State (contd..)

Depends on (contd..):

- INT: To indicate interrupt from another program or device, Only tested if in state 18 (because that is before the start of an instruction cycle)
- R: indicate the end of memory operation
- IR[15:11]: current opcode
- PSR[15]: processor executing in supervisor or user mode
- BEN: indicates whether or not a branch should be taken

CIT 595

7 - 55

### LC3 Next State Example


| CURR STATE | J  | COND | IRD | POSSIBLE NEXT STATE (depends also on 9 other Bits) |
|------------|----|------|-----|--|
| 18         | 33 | 5    | 0   | 33,49  |
| 1          | 18 | 0    | 0   | 18   |
| 32         | 0  | 0    | 1   | 0-15   |

- State 18: Most likely next state is 33 but need to check for INT (COND = 5). If INT = 1, Next State = 49
- State 1: Next State is just 18 (this because you are done finishing ADD instr and want to start a new instr. Cycle)
- State 32: J and COND ignored as IRD = 1, 0 – 15 are your next possible states

CIT 595

7 - 56


## Generic Microprogram Control

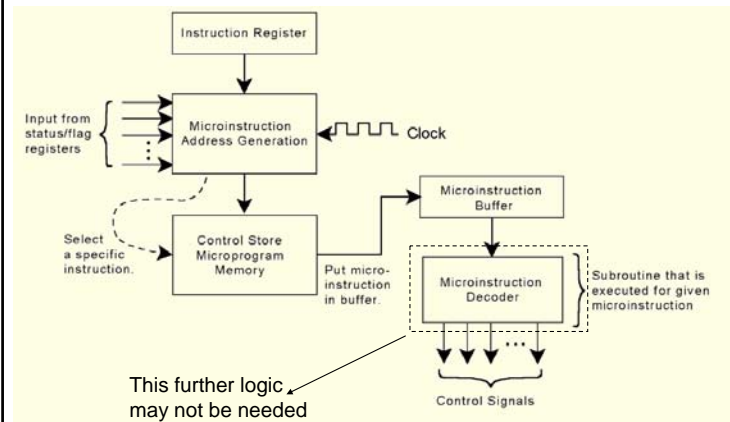

CIT 595

7 - 57

## LC3 Processor

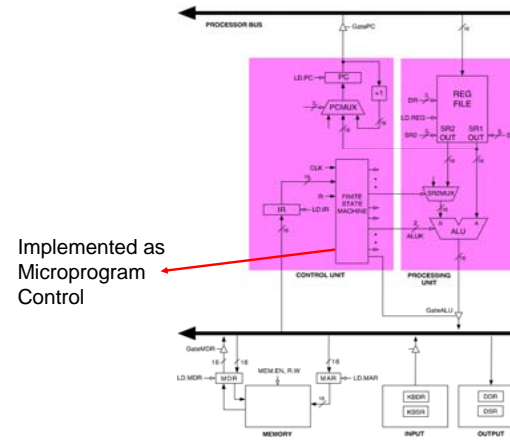

CIT 595

7 - 58

## Hardwired vs. Microprogrammed

### Complexity

- There is an extra level of instruction interpretation in microprogrammed control, which makes it slower than hardwired control

### Flexibility

- Instruction and Control Logic are tied together in hardwired control, which makes it difficult to modify
- New instructions can be easily added by only making changes to the microprogram in microprogrammed control implementation

CIT 595

7 - 59