

Design of Digital Systems II

Combinational Logic Design Principles

Moslem Amiri, Václav Přenosil

Embedded Systems Laboratory
Faculty of Informatics, Masaryk University
Brno, Czech Republic

`amiri@mail.muni.cz`
`prenosil@fi.muni.cz`

October, 2012

- **Combinational logic circuit**

- A circuit whose outputs depend only on its current inputs
- May contain an arbitrary number of logic gates and inverters but no feedback loops
 - A **feedback loop** is a signal path that allows output of a gate to propagate back to input of that same gate
 - Such a loop creates sequential circuit behavior

- **Combinational circuit analysis**

- We start with a logic diagram and proceed to a formal description of function performed by that circuit, such as a truth table or a logic expression

- **Combinational circuit synthesis**

- Reverse of analysis
- Starting with a formal description and proceeding to a logic diagram

- **Boolean algebra**

- A two-valued algebraic system
- Is used to formulate propositions that are true or false, combine them to make new propositions, and determine truth or falsehood of the new propositions

- **Switching algebra**

- Adaptation of Boolean algebra to analyze and describe behavior of circuits
- A physical condition—voltage HIGH or LOW, capacitor charged or discharged, and so on—is represented by a variable X that can have one of two possible values, 0 or 1

● **Axioms** or **postulates**

- A minimal set of basic definitions that we assume to be true, from which all other information about system can be derived
- The first two axioms of switching algebra embody digital abstraction

$$(A1) \quad X = 0 \quad \text{if } X \neq 1 \qquad (A1') \quad X = 1 \quad \text{if } X \neq 0$$

- The only difference between $A1$ and $A1'$ is interchange of 0 and 1
 - This is a characteristic of all axioms of switching algebra
 - This is basis of duality principle
 - If X denotes an inverter's input signal, X' denotes its output value
- $$(A2) \quad \text{If } X = 0, \text{ then } X' = 1 \qquad (A2') \quad \text{If } X = 1, \text{ then } X' = 0$$
- AND and OR operations (AND has precedence)

$$(A3) \quad 0 \cdot 0 = 0$$

$$(A3') \quad 1 + 1 = 1$$

$$(A4) \quad 1 \cdot 1 = 1$$

$$(A4') \quad 0 + 0 = 0$$

$$(A5) \quad 0 \cdot 1 = 1 \cdot 0 = 0$$

$$(A5') \quad 1 + 0 = 0 + 1 = 1$$

- The five pairs of axioms, $A1$ – $A5$ and $A1'$ – $A5'$, completely define switching algebra
 - All other facts about system can be proved using these axioms as a starting point

● Switching-algebra **theorems**

- True statements that allow us to manipulate algebraic expressions to allow simpler analysis or more efficient synthesis of corresponding circuits

Table 1: Switching-algebra theorems with one variable.

| | | | | |
|------|--------------|-------|------------------|-----------------|
| (T1) | $X + 0 = X$ | (T1') | $X \cdot 1 = X$ | (Identities) |
| (T2) | $X + 1 = 1$ | (T2') | $X \cdot 0 = 0$ | (Null elements) |
| (T3) | $X + X = X$ | (T3') | $X \cdot X = X$ | (Idempotency) |
| (T4) | $(X')' = X$ | | | (Involution) |
| (T5) | $X + X' = 1$ | (T5') | $X \cdot X' = 0$ | (Complements) |

● **Perfect induction**

- A technique to prove theorems in switching algebra
- Since a variable can take on only 0 and 1, prove a theorem involving a single variable X by proving that it is true for both $X = 0$ and $X = 1$
- E.g., to prove T1

$$[X = 0] \longrightarrow 0 + 0 = 0 \longrightarrow \text{true, according to axiom } A4'$$

$$[X = 1] \longrightarrow 1 + 0 = 1 \longrightarrow \text{true, according to axiom } A5'$$

Table 2: Switching-algebra theorems with two or three variables.

| | | | | |
|--------|---|--------|---|------------------|
| (T6) | $X + Y = Y + X$ | (T6') | $X \cdot Y = Y \cdot X$ | (Commutativity) |
| (T7) | $(X + Y) + Z = X + (Y + Z)$ | (T7') | $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$ | (Associativity) |
| (T8) | $X \cdot Y + X \cdot Z = X \cdot (Y + Z)$ | (T8') | $(X + Y) \cdot (X + Z) = X + Y \cdot Z$ | (Distributivity) |
| (T9) | $X + X \cdot Y = X$ | (T9') | $X \cdot (X + Y) = X$ | (Covering) |
| (T10) | $X \cdot Y + X \cdot Y' = X$ | (T10') | $(X + Y) \cdot (X + Y') = X$ | (Combining) |
| (T11) | $X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$ | | | (Consensus) |
| (T11') | $(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$ | | | |

- Theorems in Tab. 2 are proved by perfect induction, by evaluating theorem statements for all possible combinations of X and Y (and Z)
- Proof of T9: $X + X \cdot Y = X \cdot 1 + X \cdot Y = X \cdot (1 + Y) = X \cdot 1 = X$
- In T11, if $Y \cdot Z = 1$, either $X \cdot Y$ or $X' \cdot Z$ must also be 1
 - Thus, $Y \cdot Z$ term is redundant
 - Consensus theorem is used to eliminate certain timing hazards
- It is possible to replace each variable in Tab. 2 with a logic expression

Table 3: Switching-algebra theorems with n variables.

| | | |
|--------|--|----------------------------------|
| (T12) | $X + X + \cdots + X = X$ | (Generalized idempotency) |
| (T12') | $X \cdot X \cdot \cdots \cdot X = X$ | |
| (T13) | $(X_1 \cdot X_2 \cdot \cdots \cdot X_n)' = X_1' + X_2' + \cdots + X_n'$ | (DeMorgan's theorems) |
| (T13') | $(X_1 + X_2 + \cdots + X_n)' = X_1' \cdot X_2' \cdot \cdots \cdot X_n'$ | |
| (T14) | $[F(X_1, X_2, \dots, X_n, \cdot)]' = F(X_1', X_2', \dots, X_n', \cdot, +)$ | (Generalized DeMorgan's theorem) |
| (T15) | $F(X_1, X_2, \dots, X_n) = X_1 \cdot F(1, X_2, \dots, X_n) + X_1' \cdot F(0, X_2, \dots, X_n)$ | (Shannon's expansion theorems) |
| (T15') | $F(X_1, X_2, \dots, X_n) = [X_1 + F(0, X_2, \dots, X_n)] \cdot [X_1' + F(1, X_2, \dots, X_n)]$ | |

- Theorems in Tab. 3 are proved using **finite induction**

- Basis step*: prove theorem is true for $n = 2$

- Induction step*: if theorem is true for $n = i$, it is also true for $n = i + 1$

- Example: T12

- For $n = 2$, T12 = T3, therefore true

- If it is true for a logical sum of i X 's, it is also true for a sum of $i + 1$ X 's

$$\underbrace{X + X + X + \cdots + X}_{i+1 \text{ } X\text{'s}} = X + \underbrace{(X + X + \cdots + X)}_{i \text{ } X\text{'s}} = X + \underbrace{(X)}_{\text{if T12 is true for } n=i} \stackrel{T3}{=} X$$

Switching Algebra: n -Variable Theorems

 


Figure 1: Equivalent circuits according to DeMorgan's theorem T13: (a) AND-NOT; (b) NOT-OR; (c) logic symbol for a NAND gate; (d) equivalent symbol for a NAND gate.

 


Figure 2: Equivalent circuits according to DeMorgan's theorem T13': (a) OR-NOT; (b) NOT-AND; (c) logic symbol for a NOR gate; (d) equivalent symbol for a NOR gate.

- **Principle of duality**

- Any theorem or identity in switching algebra remains true if 0 and 1 are swapped and \cdot and $+$ are swapped throughout
- This is true because duals of all axioms are true, so duals of all switching-algebra theorems can be proved using duals of axioms

- **Dual of a logic expression**

$$F^D(X_1, X_2, \dots, X_n, +, \cdot, ') = F(X_1, X_2, \dots, X_n, \cdot, +, ')$$

- Generalized DeMorgan's theorem

$$\begin{aligned} [F(X_1, X_2, \dots, X_n, +, \cdot)]' &= F(X_1', X_2', \dots, X_n', \cdot, +) \\ &= F^D(X_1', X_2', \dots, X_n', +, \cdot) \end{aligned}$$

Switching Algebra: Duality



| X | Y | Z |
|------|------|------|
| LOW | LOW | LOW |
| LOW | HIGH | LOW |
| HIGH | LOW | LOW |
| HIGH | HIGH | HIGH |



| X | Y | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |



| X | Y | Z |
|---|---|---|
| 1 | 1 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 0 | 0 | 0 |

Figure 3: A "type-1" logic gate: (a) electrical function table; (b) logic function table and symbol with positive logic; (c) logic function table and symbol with negative logic.



| X | Y | Z |
|------|------|------|
| LOW | LOW | LOW |
| LOW | HIGH | HIGH |
| HIGH | LOW | HIGH |
| HIGH | HIGH | HIGH |



| X | Y | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |



| X | Y | Z |
|---|---|---|
| 1 | 1 | 1 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 0 | 0 | 0 |

Figure 4: A "type-2" logic gate: (a) electrical function table; (b) logic function table and symbol with positive logic; (c) logic function table and symbol with negative logic.

Switching Algebra: Duality

 


Figure 5: Circuit for a logic function using inverters and type-1 and type-2 gates under a positive-logic convention.

 


Figure 6: Negative-logic interpretation of the previous circuit.

- Figs. 5 and 6

- Fig. 5 shows a circuit corresponding to expression $F(X_1, X_2, \dots, X_n)$ following positive-logic convention
- Circuit of Fig. 6 is that of Fig. 5 without change, but logic convention is changed from positive to negative
 - For every possible combination of input voltages (HIGH and LOW), the circuit still produces the same output voltage
 - But from point of view of switching algebra, output value—0 or 1—is opposite of what it was under positive-logic convention
 - Likewise, each input value is opposite of what it was
- Therefore, for each possible input combination to circuit in Fig. 5, output is opposite of that produced by opposite input combination applied to circuit in Fig. 6

$$F(X_1, X_2, \dots, X_n) = [F^D(X'_1, X'_2, \dots, X'_n)]'$$

By complementing both sides, we get generalized DeMorgan's theorem

$$[F(X_1, X_2, \dots, X_n)]' = F^D(X'_1, X'_2, \dots, X'_n)$$

Standard Representations of Logic Functions

- The most basic representation of a logic function is **truth table**
 - It lists output of circuit for every possible input combination

Table 4: General truth table structure for a 3-variable logic function, $F(X, Y, Z)$.

| Row | X | Y | Z | F |
|-----|---|---|---|------------|
| 0 | 0 | 0 | 0 | $F(0,0,0)$ |
| 1 | 0 | 0 | 1 | $F(0,0,1)$ |
| 2 | 0 | 1 | 0 | $F(0,1,0)$ |
| 3 | 0 | 1 | 1 | $F(0,1,1)$ |
| 4 | 1 | 0 | 0 | $F(1,0,0)$ |
| 5 | 1 | 0 | 1 | $F(1,0,1)$ |
| 6 | 1 | 1 | 0 | $F(1,1,0)$ |
| 7 | 1 | 1 | 1 | $F(1,1,1)$ |

Table 5: Truth table for a particular 3-variable logic function, $F(X, Y, Z)$.

| Row | X | Y | Z | F |
|-----|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 1 |

- **Literal**

- A variable or complement of a variable
- Examples: X , Y , X' , Y'

- **Product term**

- A single literal or a logical product of two or more literals
- Examples: Z' , $W \cdot X \cdot Y$, $X \cdot Y' \cdot Z$, $W' \cdot Y' \cdot Z$

- **Sum-of-products expression**

- A logical sum of product terms
- Example: $Z' + W \cdot X \cdot Y + X \cdot Y' \cdot Z + W' \cdot Y' \cdot Z$

- **Sum term**

- A single literal or a logical sum of two or more literals
- Examples: Z' , $W + X + Y$, $X + Y' + Z$, $W' + Y' + Z$

- **Product-of-sums expression**

- A logical product of sum terms
- Example: $Z' \cdot (W + X + Y) \cdot (X + Y' + Z) \cdot (W' + Y' + Z)$

● Normal term

- A product or sum term in which no variable appears more than once
- A nonnormal term can always be simplified to a constant or a normal term
- Examples of nonnormal terms:
 $W \cdot X \cdot X \cdot Y'$, $W + W + X' + Y$, $X \cdot X' \cdot Y$
- Examples of normal terms: $W \cdot X \cdot Y'$, $W + X' + Y$

● n -variable **minterm**

- A normal product term with n literals
- There are 2^n such product terms
- Examples of 4-variable minterms:
 $W' \cdot X' \cdot Y' \cdot Z'$, $W \cdot X \cdot Y' \cdot Z$, $W' \cdot X' \cdot Y \cdot Z'$

● n -variable **maxterm**

- A normal sum term with n literals
- There are 2^n such sum terms
- Examples of 4-variable maxterms:
 $W' + X' + Y' + Z'$, $W + X' + Y' + Z$, $W' + X' + Y + Z'$

Standard Representations of Logic Functions

- Correspondence between truth table and minterms and maxterms
 - A minterm is defined as a product term that is 1 in exactly one row of truth table
 - A maxterm is defined as a sum term that is 0 in exactly one row of truth table

Table 6: Minterms and maxterms for a 3-variable logic function, $F(X, Y, Z)$.

| Row | X | Y | Z | F | Minterm | Maxterm |
|------------|----------|----------|----------|----------|------------------------|----------------|
| 0 | 0 | 0 | 0 | F(0,0,0) | $X' \cdot Y' \cdot Z'$ | $X + Y + Z$ |
| 1 | 0 | 0 | 1 | F(0,0,1) | $X' \cdot Y' \cdot Z$ | $X + Y + Z'$ |
| 2 | 0 | 1 | 0 | F(0,1,0) | $X' \cdot Y \cdot Z'$ | $X + Y' + Z$ |
| 3 | 0 | 1 | 1 | F(0,1,1) | $X' \cdot Y \cdot Z$ | $X + Y' + Z'$ |
| 4 | 1 | 0 | 0 | F(1,0,0) | $X \cdot Y' \cdot Z'$ | $X' + Y + Z$ |
| 5 | 1 | 0 | 1 | F(1,0,1) | $X \cdot Y' \cdot Z$ | $X' + Y + Z'$ |
| 6 | 1 | 1 | 0 | F(1,1,0) | $X \cdot Y \cdot Z'$ | $X' + Y' + Z$ |
| 7 | 1 | 1 | 1 | F(1,1,1) | $X \cdot Y \cdot Z$ | $X' + Y' + Z'$ |

- **Minterm i**

- The minterm corresponding to row i of truth table
- A variable is complemented if corresponding bit in binary is 0
- Example: row 5 \rightarrow binary: 101 \rightarrow minterm 5: $X \cdot Y' \cdot Z$

- **Maxterm i**

- The maxterm corresponding to row i of truth table
- A variable is complemented if corresponding bit in binary is 1
- Example: row 5 \rightarrow binary: 101 \rightarrow maxterm 5: $X' + Y + Z'$

- **Canonical sum** of a logic function

- A sum of minterms corresponding to truth-table rows (input combinations) for which the function produces a 1 output

- **Canonical product** of a logic function

- A product of maxterms corresponding to input combinations for which the function produces a 0 output

- In Tab. 5

- Canonical sum

$$F = \sum_{X,Y,Z} (0, 3, 4, 6, 7)$$
$$= X' \cdot Y' \cdot Z' + X' \cdot Y \cdot Z + X \cdot Y' \cdot Z' + X \cdot Y \cdot Z' + X \cdot Y \cdot Z$$

Notation $\sum_{X,Y,Z}(0, 3, 4, 6, 7)$ is a **minterm list** or **on-set**

- Canonical product

$$F = \prod_{X,Y,Z} (1, 2, 5) = (X + Y + Z') \cdot (X + Y' + Z) \cdot (X' + Y + Z')$$

Notation $\prod_{X,Y,Z}(1, 2, 5)$ is a **maxterm list** or **off-set**

| Row | X | Y | Z | F |
|-----|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 1 |

- Conversion between a minterm list and a maxterm list
 - For a function of n variables, possible minterm and maxterm numbers are in the set $\{0, 1, \dots, 2^n - 1\}$
 - To switch between list types, take the set complement
 - Example

$$\sum_{A,B,C} (0, 1, 2, 3) = \prod_{A,B,C} (4, 5, 6, 7)$$

$$\sum_{X,Y} (1) = \prod_{X,Y} (0, 2, 3)$$

$$\sum_{W,X,Y,Z} (0, 1, 2, 3, 5, 7, 11, 13) = \prod_{W,X,Y,Z} (4, 6, 8, 9, 10, 12, 14, 15)$$

- Each of these representations specifies exactly the same information
 - ① A truth table
 - ② An algebraic sum of minterms, the canonical sum
 - ③ A minterm list using \sum notation
 - ④ An algebraic product of maxterms, the canonical product
 - ⑤ A maxterm list using \prod notation

- We analyze a combinational logic circuit by obtaining a formal description of its logic function
- Operations possible after obtaining a formal description
 - Determining behavior of logic circuit for various input combinations
 - Manipulating an algebraic description to suggest different circuit structures
 - Transforming an algebraic description into a standard form corresponding to an available circuit structure
 - E.g., a sum-of-products expression corresponds directly to circuit structure used in PLAs, and a truth table corresponds to lookup memory used in most FPGAs
 - Using an algebraic description of circuit's functional behavior in analysis of a larger system that includes the circuit

Combinational-Circuit Analysis

- The most basic functional description is truth table
 - Obtain truth table of an n -input circuit by working the way through all 2^n input combinations
 - For each input combination, determine all of gate outputs produced by that input, propagating information from circuit inputs to outputs
 - Truth table is written by transcribing output sequence of final gate

 


Figure 7: Gate outputs created by all input combinations.

Table 7: Truth table for the logic circuit of Fig. 7.

| <i>Row</i> | X | Y | Z | F |
|------------|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 1 |
| 3 | 0 | 1 | 1 | 0 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 1 | 1 |
| 6 | 1 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 1 |

- The number of input combinations of a logic circuit grows exponentially with the number of inputs
 - Instead of exhaustive approach, we normally use an algebraic approach
 - Complexity of algebraic approach is linearly proportional to size of circuit

- Algebraic approach

- Build up a parenthesized logic expression corresponding to logic operators and structure of circuit
- Start at circuit inputs and propagate expressions through gates toward output
- Simplify expressions while going, or defer all algebraic manipulations until an output expression is obtained

 


Figure 8: Logic expressions for signal lines.

- In Fig. 8, a sum of products is obtained by "multiplying out" output function

$$\begin{aligned} F &= ((X + Y') \cdot Z) + (X' \cdot Y \cdot Z') \\ &= X \cdot Z + Y' \cdot Z + X' \cdot Y \cdot Z' \end{aligned}$$

This new expression corresponds to a different circuit for the same logic function, as shown in Fig. 9

 


Figure 9: Two-level AND-OR circuit.

Combinational-Circuit Analysis

- Similarly, a product of sums is obtained by "adding out" output function of Fig. 8

$$\begin{aligned}F &= ((X + Y') \cdot Z) + (X' \cdot Y \cdot Z') \\ &= (X + Y' + X') \cdot (X + Y' + Y) \cdot (X + Y' + Z') \cdot (Z + X') \cdot (Z + Y) \cdot (Z + Z') \\ &= 1 \cdot 1 \cdot (X + Y' + Z') \cdot (X' + Z) \cdot (Y + Z) \cdot 1 \\ &= (X + Y' + Z') \cdot (X' + Z) \cdot (Y + Z)\end{aligned}$$

 


Figure 10: Two-level OR-AND circuit.

Combinational-Circuit Analysis

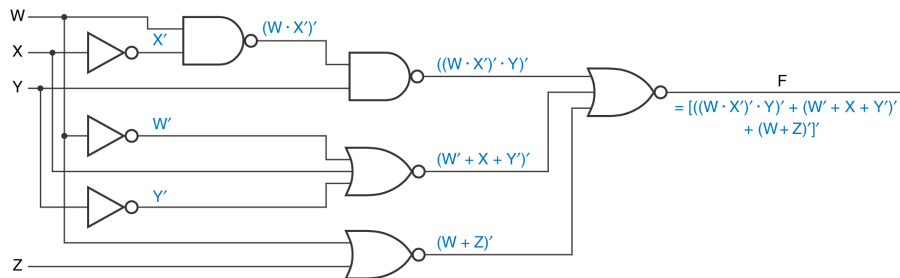


Figure 11: Algebraic analysis of a logic circuit with NAND and NOR gates.

$$\begin{aligned} F &= [((W \cdot X')' \cdot Y)' + (W' + X + Y)' + (W + Z)]' \\ &= ((W' + X)' + Y)' \cdot (W \cdot X' \cdot Y)' \cdot (W' \cdot Z)' \\ &= ((W \cdot X')' \cdot Y) \cdot (W' + X + Y)' \cdot (W + Z) \\ &= ((W' + X) \cdot Y) \cdot (W' + X + Y)' \cdot (W + Z) \end{aligned}$$

Combinational-Circuit Analysis

- DeMorgan's theorem can be applied *graphically* to simplify algebraic analysis
 - We can cancel out some of inversions
 - In Fig. 12, this manipulation leads us to a simplified output expression directly

$$F = ((W' + X) \cdot Y) \cdot (W' + X + Y') \cdot (W + Z) \quad (1)$$

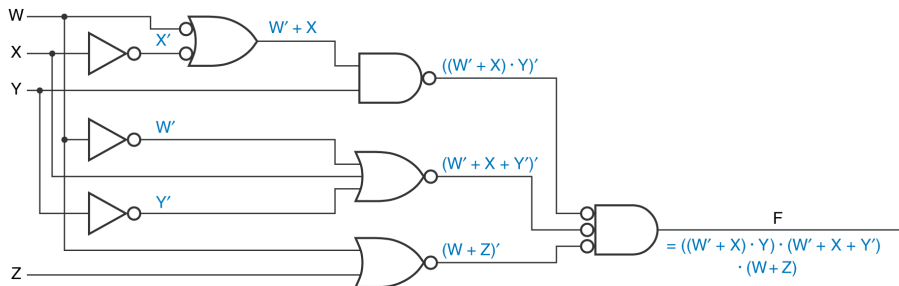


Figure 12: Algebraic analysis of the circuit in Fig. 11 after substituting some NAND and NOR symbols.

Combinational-Circuit Analysis

- When we simplify a logic expression, we get an expression corresponding to a different physical circuit
 - E.g., simplified expression (1) corresponds to circuit of Fig. 13

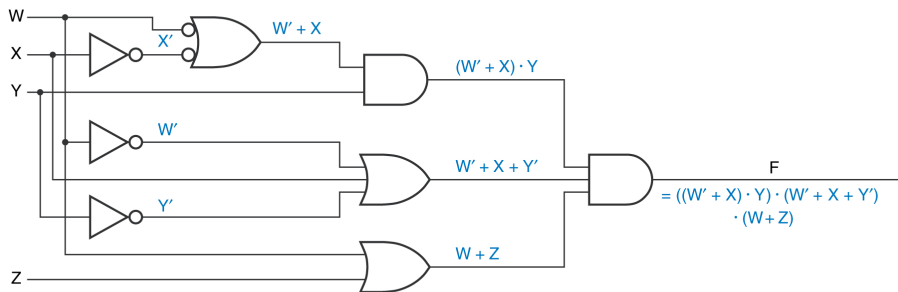


Figure 13: A different circuit for same logic function.

- We could also multiply out and add out expression (1) to obtain sum-of-products and product-of-sums expressions corresponding to two more physically different circuits for same logic function

Combinational-Circuit Analysis

- Logic expressions are not always used to convey information about physical structure of a circuit
 - An expression might describe more than one circuit structure
 - The only sure way to determine a circuit's structure is via its drawing
 - But, for certain classes of circuits, structural information could be described without reference to drawing
 - E.g., "a two-level NAND-NAND circuit for $W \cdot X \cdot Y + Y \cdot Z$ "

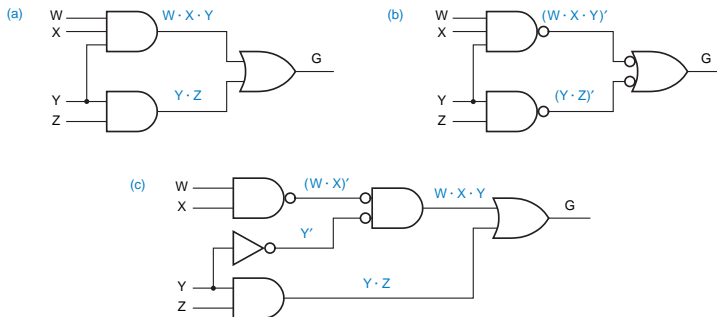


Figure 14: Three circuits for $G(W, X, Y, Z) = W \cdot X \cdot Y + Y \cdot Z$: (a) two-level AND-OR; (b) two-level NAND-NAND; (c) with 2-input gates only.

- Sometimes, a logic circuit description is a list of input combinations, verbal equivalent of a truth table or \sum or \prod notation
 - Example (prime-number detector): "Given a 4-bit input combination $N = N_3N_2N_1N_0$, produce a 1 output for $N = 1, 2, 3, 5, 7, 11, 13$ and 0 otherwise"
 - A logic function described in this way can be designed directly from canonical sum or product expression

$$\begin{aligned} F &= \sum_{N_3, N_2, N_1, N_0} (1, 2, 3, 5, 7, 11, 13) \\ &= N'_3 \cdot N'_2 \cdot N'_1 \cdot N_0 + N'_3 \cdot N'_2 \cdot N_1 \cdot N'_0 + N'_3 \cdot N'_2 \cdot N_1 \cdot N_0 \\ &\quad + N'_3 \cdot N_2 \cdot N'_1 \cdot N_0 + N'_3 \cdot N_2 \cdot N_1 \cdot N_0 + N_3 \cdot N'_2 \cdot N_1 \cdot N_0 \\ &\quad + N_3 \cdot N_2 \cdot N'_1 \cdot N_0 \end{aligned}$$

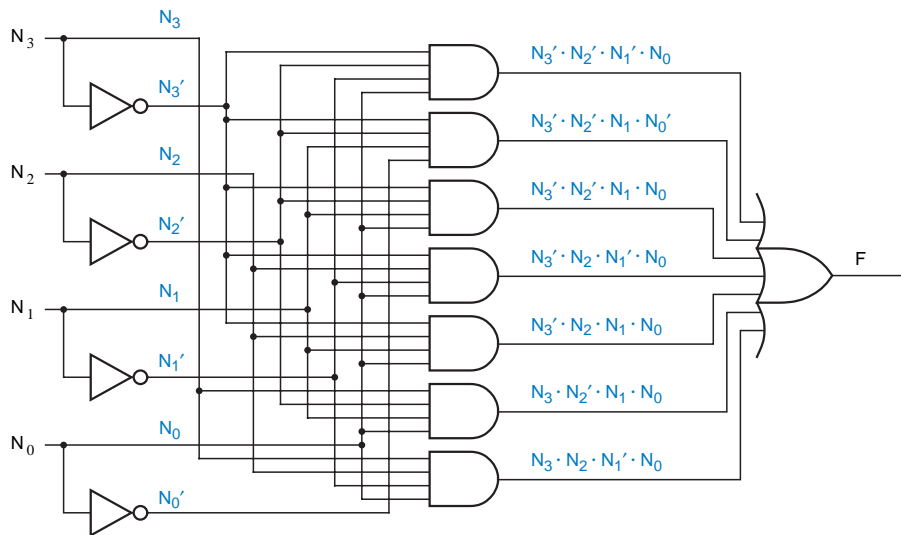


Figure 15: Canonical-sum design for 4-bit prime-number detector.

- Often, we describe a logic function using English-language connectives "and," "or," and "not"
 - Example (alarm circuit): "ALARM output is 1 if PANIC input is 1, or if ENABLE input is 1, EXITING input is 0, and house is not secure; house is secure if WINDOW, DOOR, and GARAGE inputs are all 1"
 - Such a description can be translated directly into algebraic expressions

$$\text{ALARM} = \text{PANIC} + \text{ENABLE} \cdot \text{EXITING}' \cdot \text{SECURE}'$$

$$\text{SECURE} = \text{WINDOW} \cdot \text{DOOR} \cdot \text{GARAGE}$$

$$\text{ALARM} = \text{PANIC} + \text{ENABLE} \cdot \text{EXITING}' \cdot (\text{WINDOW} \cdot \text{DOOR} \cdot \text{GARAGE})'$$

 


Figure 16: Alarm circuit derived from logic expression.

- Having an expression for a logic function, we can do some other operations
 - We can manipulate it to get different circuits
 - E.g., ALARM expression can be multiplied out to get sum-of-products circuit
 - We can construct the truth table for the expression and use any of synthesis methods that apply to truth tables
 - E.g., canonical sum or product method and minimization methods

 


Figure 17: Sum-of-products version of alarm circuit.

Combinational-Circuit Synthesis: Circuit Manipulations

- We can translate any logic expression into an equivalent sum-of-products expression by multiplying it out
 - Such an expression may be realized directly with AND and OR gates
 - By substituting gates: two-level AND-OR \rightarrow two-level NAND-NAND

 


Figure 18: Alternative sum-of-products realizations: (a) AND-OR; (b) AND-OR with extra inverter pairs; (c) NAND-NAND.

Combinational-Circuit Synthesis: Circuit Manipulations

 


Figure 19: Another two-level sum-of-products circuit: (a) AND-OR; (b) AND-OR with extra inverter pairs; (c) NAND-NAND.

Combinational-Circuit Synthesis: Circuit Manipulations

- We can translate any logic expression into an equivalent product-of-sums expression by adding it out
 - Such an expression has both OR-AND and NOR-NOR circuit realizations

 


Figure 20: Realizations of a product-of-sums expression: (a) OR-AND; (b) OR-AND with extra inverter pairs; (c) NOR-NOR.

Combinational-Circuit Synthesis: Circuit Manipulations

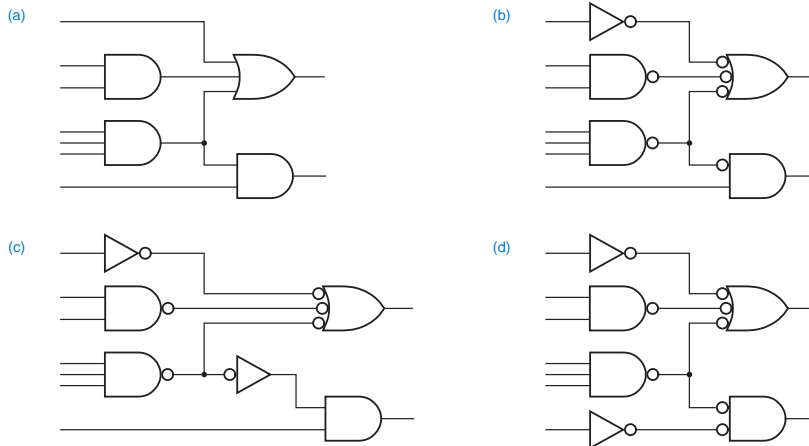


Figure 21: Logic-symbol manipulations: (a) original circuit; (b) transformation with a nonstandard gate; (c) inverter used to eliminate nonstandard gate; (d) preferred inverter placement; one level of gate delay is eliminated, and bottom gate becomes a NOR instead of AND.

- Combinational-circuit-minimization methods have as their starting point a truth table or, equivalently, a minterm list or maxterm list
 - Given a logic function that is not expressed in this form, we must convert it to an appropriate form before using these methods
- Minimization methods reduce cost of a two-level AND-OR, OR-AND, NAND-NAND, or NOR-NOR circuit in three ways
 - ① By minimizing number of first-level gates
 - ② By minimizing number of inputs on each first-level gate
 - ③ By minimizing number of inputs on second-level gate
 - This is a side effect of the first reduction
- Minimization methods do not consider cost of input inverters
 - They assume both true and complemented versions of all input variables are available
 - Not always the case in gate-level or ASIC design
 - But, appropriate for PLD-based design where both true and complemented versions of all input variables are available for free

- Most minimization methods are based on combining theorems, T10 and T10'

$$\begin{aligned} \text{given product term} \cdot Y + \text{given product term} \cdot Y' &= \text{given product term} \\ (\text{given sum term} + Y) \cdot (\text{given sum term} + Y') &= \text{given sum term} \end{aligned}$$

- Applying this method repeatedly to combine minterms 1, 3, 5, and 7 of prime-number detector shown in Fig. 15

$$\begin{aligned} F &= \sum_{N_3, N_2, N_1, N_0} (1, 3, 5, 7, 2, 11, 13) \\ &= N'_3 \cdot N'_2 \cdot N'_1 \cdot N_0 + N'_3 \cdot N'_2 \cdot N_1 \cdot N_0 + N'_3 \cdot N_2 \cdot N'_1 \cdot N_0 + N'_3 \cdot N_2 \cdot N_1 \cdot N_0 + \dots \\ &= (N'_3 \cdot N'_2 \cdot N'_1 \cdot N_0 + N'_3 \cdot N'_2 \cdot N_1 \cdot N_0) + (N'_3 \cdot N_2 \cdot N'_1 \cdot N_0 + N'_3 \cdot N_2 \cdot N_1 \cdot N_0) + \dots \\ &= N'_3 \cdot N'_2 \cdot N_0 + N'_3 \cdot N_2 \cdot N_0 + \dots \\ &= N'_3 \cdot N_0 + \dots \end{aligned}$$

Combinational-Circuit Synthesis: Minimization

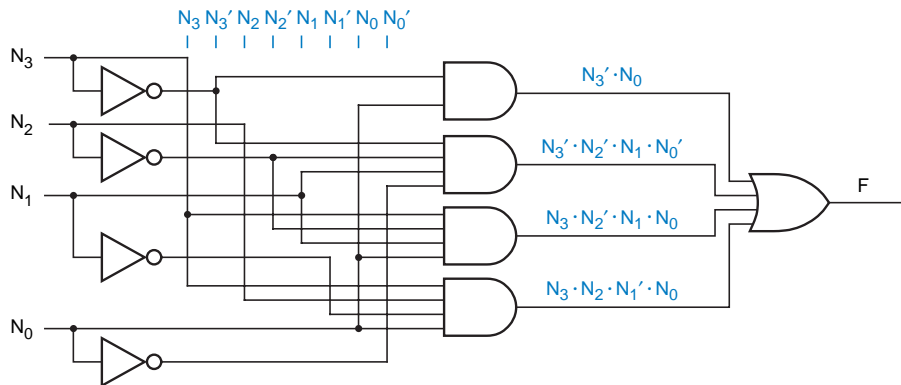


Figure 22: Simplified sum-of-products realization for 4-bit prime-number detector.

- Working more on preceding expression, we could save a couple more first-level gate inputs

● Karnaugh map

- A graphical representation of a logic function's truth table
- Map for an n -input logic function is an array with 2^n cells, one for each possible input combination or minterm
- Number inside each cell is corresponding minterm number in truth table
 - Truth-table inputs are labeled alphabetically from left to right (e.g., X, Y, Z)
 - E.g., cell 13 in 4-variable map corresponds to truth table row in which $WXYZ = 1101$

 


Figure 23: Karnaugh maps: (a) 2-variable; (b) 3-variable; (c) 4-variable.

Combinational-Circuit Synthesis: Karnaugh Maps

- To represent a logic function on a Karnaugh map, we copy 1s and 0s from truth table or equivalent to the corresponding cells of map

 


Figure 24: Karnaugh maps for logic functions: (a) $F = \sum_{X,Y}(3)$; (b) $F = \sum_{X,Y,Z}(0, 3, 4, 6, 7)$; (c) $F = \sum_{W,X,Y,Z}(1, 2, 3, 5, 7, 11, 13)$.

- Particular order of row and column numbers in a Karnaugh map makes each cell correspond to an input combination that differs from each of its immediately adjacent neighbors in only one variable
 - Corresponding cells on left/right or top/bottom borders also differ in one variable and hence neighbors; e.g., cells 12 and 14 in 4-variable map
- Each input combination with a "1" in truth table corresponds to a minterm in logic function's canonical sum
 - Pairs of adjacent "1" cells in map have minterms that differ in only one variable
 - Thus, minterm pairs can be combined into a single product term
$$\text{term} \cdot Y + \text{term} \cdot Y' = \text{term}$$
 - Thus, we can use a Karnaugh map to simplify canonical sum of a logic function

Com.-Circuit Synthesis: Minimizing Sums of Products

 


Figure 25: $F = \sum_{X,Y,Z}(1,2,5,7)$: (a) truth table; (b) Karnaugh map; (c) combining adjacent 1-cells.

● In Fig. 25(b)

For cells 5 and 7:

$$\begin{aligned}
 F &= \dots + X \cdot Y' \cdot Z + X \cdot Y \cdot Z \\
 &= \dots + (X \cdot Z) \cdot Y' + (X \cdot Z) \cdot Y \\
 &= \dots + X \cdot Z
 \end{aligned}$$

For cells 1 and 5:

$$\begin{aligned}
 F &= X' \cdot Y' \cdot Z + X \cdot Y' \cdot Z + \dots \\
 &= X' \cdot (Y' \cdot Z) + X \cdot (Y' \cdot Z) + \dots \\
 &= Y' \cdot Z + \dots
 \end{aligned}$$

- We can simplify a logic function by first combining pairs of adjacent 1-cells (minterms) wherever possible and then selecting a set of product terms that covers all of 1-cells and summing them
 - Fig. 25(c) shows the result for our example logic function
 - Corresponding AND-OR circuit is shown in Fig. 26

 


Figure 26: Minimized AND-OR circuit.

- In many logic functions, cell-combining procedure can be extended to combine more than two 1-cells into a single product term
 - Number of cells combined is always a power of 2
 - Example

$$\begin{aligned}F &= \sum_{X,Y,Z} (0, 1, 4, 5, 6) \\&= X' \cdot Y' \cdot Z' + X' \cdot Y' \cdot Z + X \cdot Y' \cdot Z' + X \cdot Y' \cdot Z + X \cdot Y \cdot Z' \\&= [(X' \cdot Y') \cdot Z' + (X' \cdot Y') \cdot Z] + [(X \cdot Y') \cdot Z' + (X \cdot Y') \cdot Z] + X \cdot Y \cdot Z' \\&= X' \cdot Y' + X \cdot Y' + X \cdot Y \cdot Z' \\&= [X' \cdot (Y') + X \cdot (Y')] + X \cdot Y \cdot Z' \\&= Y' + X \cdot Y \cdot Z'\end{aligned}$$

- 2^i 1-cells may be combined to form a product term containing $n - i$ literals (n = number of variables in function)
- A set of 2^i 1-cells are combined if there are i variables that take on all 2^i possible combinations within that set, while remaining $n - i$ variables have the same value throughout that set
 - Corresponding product term has $n - i$ literals, where a variable is complemented if it is 0 in all of 1-cells, and uncomplemented if it is 1

- Graphically, we circle *rectangular* sets of 2^i 1s, stretching definition of rectangular to account for wraparound at edges of map
 - For each variable, if a circle covers only areas of map where it is 0, the variable is complemented in product term
 - If a circle covers only areas of map where the variable is 1, the variable is uncomplemented in product term
 - If a circle covers areas of map where the variable is 0 as well as areas where it is 1, the variable does not appear in product term
 - Finally, a sum-of-products expression for a function must contain product terms that cover all of 1s and none of 0s on map
 - By circling largest possible set of 1s, a less expensive realization of logic function is found

Com.-Circuit Synthesis: Minimizing Sums of Products

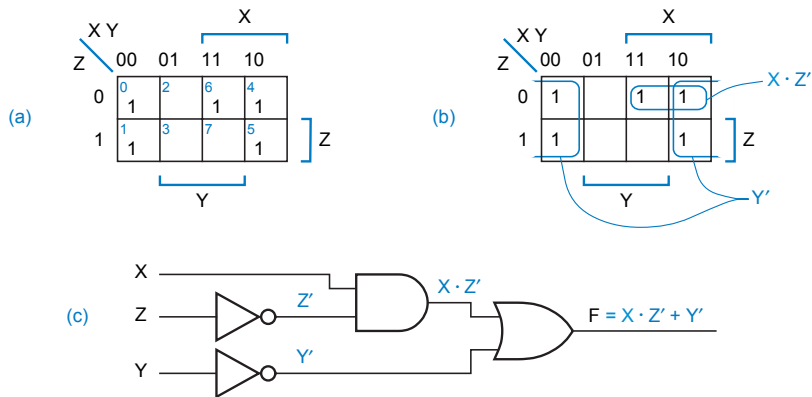


Figure 27: $F = \sum_{X,Y,Z}(0, 1, 4, 5, 6)$: (a) initial Karnaugh map; (b) Karnaugh map with circled product terms; (c) AND/OR circuit.

Com.-Circuit Synthesis: Minimizing Sums of Products

 
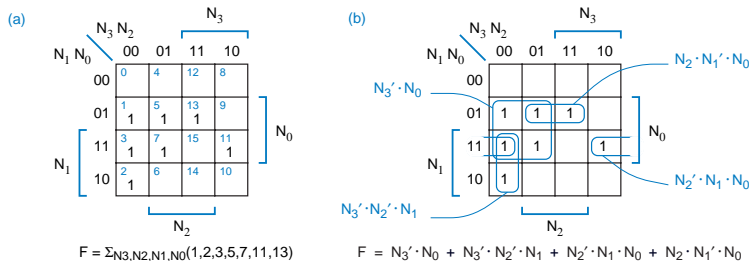


Figure 28: Prime-number detector: (a) initial Karnaugh map; (b) circled product terms; (c) minimized circuit.

- **Minimal sum** of a logic function $F(X_1, \dots, X_n)$
 - ① Has the fewest possible product terms
 - ② Within constraint 1, has the fewest possible literals
- A logic function $P(X_1, \dots, X_n)$ **implies** a logic function $F(X_1, \dots, X_n)$ if for every input combination such that $P = 1$, then $F = 1$ too
 - "P implies F" \equiv "F includes P" \equiv "F covers P" $\equiv P \Rightarrow F$
- **Prime implicant** of a logic function $F(X_1, \dots, X_n)$
 - A normal product term $P(X_1, \dots, X_n)$ that implies F , such that if any variable is removed from P , resulting product term does not imply F
 - In Karnaugh map, a prime implicant of F is a circled set of 1-cells, such that if we make it larger (twice as many cells), it covers one or more 0s
- **Prime-implicant theorem**
 - A minimal sum is a sum of prime implicants

 


Figure 29: $F = \sum_{W,X,Y,Z}(5, 7, 12, 13, 14, 15)$: (a) Karnaugh map; (b) prime implicants.

● Complete sum

- Sum of all prime implicants of a logic function
- Is not always minimal
- E.g., logic function shown in Fig. 30 has five prime implicants, but minimal sum includes only three of them

 


Figure 30: $F = \sum_{W,X,Y,Z}(1, 3, 4, 5, 9, 11, 12, 13, 14, 15)$: (a) Karnaugh map; (b) prime implicants and distinguished 1-cells.

- **Distinguished 1-cell** of a logic function
 - An input combination that is covered by only one prime implicant
- **Essential prime implicant** of a logic function
 - A prime implicant that covers one or more distinguished 1-cells

- First step in prime-implicant selection process
 - Identify distinguished 1-cells and corresponding essential prime implicants, and include them in minimal sum
 - In Fig. 30, three distinguished 1-cells are shaded, and corresponding essential prime implicants are circled with heavier lines
 - All of 1-cells are covered by essential prime implicants, so we need go no further
 - In Fig. 31, all of prime implicants are essential, and so all are included in minimal sum

Com.-Circuit Synthesis: Minimizing Sums of Products

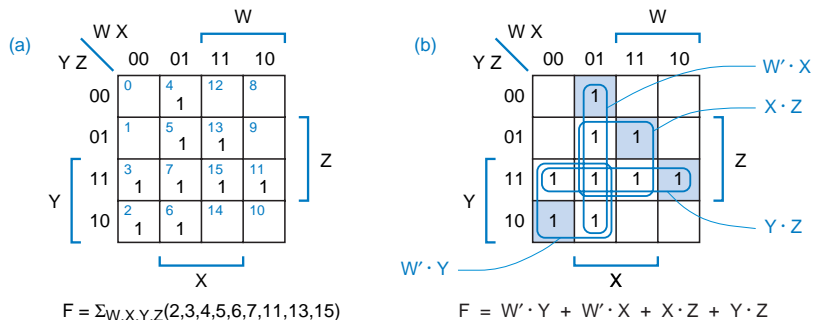


Figure 31: $F = \sum_{W,X,Y,Z}(2, 3, 4, 5, 6, 7, 11, 13, 15)$: (a) Karnaugh map; (b) prime implicants and distinguished 1-cells.

Com.-Circuit Synthesis: Minimizing Sums of Products

 


Figure 32: $F = \sum_{W,X,Y,Z}(0,1,2,3,4,5,7,14,15)$: (a) Karnaugh map; (b) prime implicants and distinguished 1-cells; (c) reduced map after removal of essential prime implicants and covered 1-cells.

- In Fig. 32, by removing essential prime implicants and the 1-cells they cover, we obtain a reduced map with only a single 1-cell and two prime implicants that cover it
 - We use $W' \cdot Z$ product term because it has fewer inputs and therefore lower cost

● Eclipse

- Given two prime implicants P and Q in a reduced map, P is said to eclipse Q ($P \supseteq Q$) if P covers at least all 1-cells covered by Q
- If P eclipses Q , then Q can be ignored when finding a minimal sum
- In Fig. 33(c), $X \cdot Y \cdot Z$ eclipses the other two prime implicants
 - $X \cdot Y \cdot Z$ is a **secondary essential prime implicant** that must be included in minimal sum

 


Figure 33: $F = \sum_{W,X,Y,Z}(2, 6, 7, 9, 13, 15)$: (a) Karnaugh map; (b) prime implicants and distinguished 1-cells; (c) reduced map after removal of essential prime implicants and covered 1-cells.

Com.-Circuit Synthesis: Minimizing Sums of Products

 


Figure 34: $F = \sum_{W,X,Y,Z}(1, 5, 7, 9, 11, 15)$: (a) Karnaugh map; (b) prime implicants (no essential); (c) a minimal sum; (d) another minimal sum.

- Using principle of duality, we can minimize product-of-sums expressions by looking at 0s on a Karnaugh map
 - Each 0 on map corresponds to a maxterm in canonical product of logic function
 - To find **minimal product**, we write sum terms corresponding to circled sets of 0s
- In Fig. 35

$$F = (X + Y' + Z) \cdot (X' + Z') \cdot (Y + Z')$$

 


Figure 35: $F = \prod_{X,Y,Z}(1, 2, 5, 7)$: (a) truth table; (b) Karnaugh map; (c) combining adjacent 0-cells.

- Indirect method to find minimal product
 - For circled sets of 0s in Karnaugh map, write *product terms*
 - Equate F' to *minimal sum*
 - Use DeMorgan's theorem to find F
 - E.g., for Fig. 35(c), product terms of circled 0s are:
 $X' \cdot Y \cdot Z'$, $X \cdot Z$, $Y' \cdot Z$

$$F' = X' \cdot Y \cdot Z' + X \cdot Z + Y' \cdot Z$$

$$[F']' = [X' \cdot Y \cdot Z' + X \cdot Z + Y' \cdot Z]'$$

$$F = (X + Y' + Z) \cdot (X' + Z') \cdot (Y + Z')$$

● PLD minimization

- PLDs have an AND-OR array corresponding to sum-of-products form
- Most PLDs, also have an inverter/buffer at output of AND-OR array, which can be programmed to invert or not
 - Thus, PLD can utilize the equivalent of minimal sum by using AND-OR array to realize complement of desired function and then programming inverter/buffer to invert
 - Most logic-minimization programs for PLDs find both minimal sum and minimal product and select the one that requires fewer terms

- Predicting **steady-state behavior** of combinational logic circuits
 - Predicting a circuit's output as a function of its inputs under assumption that inputs have been stable for a long time, relative to delays in circuit's electronics
 - Circuit delay is ignored
 - But actual delay from an input change to corresponding output change in a real circuit is nonzero
- **Transient behavior** of a combinational logic circuit
 - Considers circuit delays
 - May differ from what is predicted by a steady-state analysis
 - A circuit's output may produce a short pulse, called a **glitch**, at a time when steady-state analysis predicts that output should not change
 - A **hazard** exists when a circuit has possibility of producing such a glitch
 - A logic designer must eliminate hazards

● Static-1 hazard

- A pair of input combinations that
 - ① Differ in only one input variable
 - ② Both give a 1 output

such that it is possible for a momentary 0 output to occur during a transition in the differing input variable

 
 


Figure 36: Circuit with a static-1 hazard: (a) logic diagram; (b) timing diagram ($X = 1, Y = 1, Z : 1 \rightarrow 0$, propagation delay through each gate or inverter is one unit time).

● Static-0 hazard

- A pair of input combinations that
 - ① Differ in only one input variable
 - ② Both give a 0 output

such that it is possible for a momentary 1 output to occur during a transition in the differing input variable

 


Figure 37: Circuit with static-0 hazards: (a) logic diagram; (b) timing diagram.

Timing Hazards: Static Hazards

- A Karnaugh map can be used to detect static hazards in a two-level sum-of-products or product-of-sums circuit
- A properly designed two-level sum-of-products (AND-OR) circuit has no static-0 hazards
 - A static-0 hazard would exist only if both a variable and its complement were connected to the same AND gate, which would be silly
 - But the circuit may have static-1 hazards

 
 


Figure 38: Karnaugh map for the circuit of Fig. 36: (a) as originally designed; (b) with static-1 hazard eliminated.

- In Fig. 38
 - There is no single product term that covers both input combinations $X, Y, Z = 111$ and $X, Y, Z = 110$
 - Possible for output to glitch momentarily to 0 if AND gate output that covers one of combinations goes to 0 before AND gate output covering the other input combination goes to 1
 - To eliminate hazard, include an extra product term (AND gate) to cover hazardous input pair
 - The extra product term to be added is consensus of the two original terms

 


Figure 39: Circuit of Fig. 36 with static-1 hazard eliminated.

Timing Hazards: Static Hazards


 



Figure 40: Karnaugh map for another sum-of-products circuit: (a) as originally designed; (b) with extra product terms to cover static-1 hazards.

Timing Hazards: Static Hazards

 - A properly designed two-level product-of-sums (OR-AND) circuit has no static-1 hazards
 - But, it may have static-0 hazards
 - These hazards can be detected and eliminated by studying adjacent 0s in Karnaugh map



$$F = (X' + Z) \cdot (Y' + Z')$$

 

$$F = (X' + Z) \cdot (Y' + Z') \cdot (X' + Y')$$

Figure 41: Karnaugh map for a product-of-sums circuit: (a) as originally designed; (b) with extra sum term to cover the static-0 hazard.

● Dynamic hazard

- Possibility of an output changing more than once as the result of a single input transition
- Multiple output transitions can occur if there are multiple paths with different delays from the changing input to the changing output

 


Figure 42: Circuit with a dynamic hazard.

- In Fig. 42
 - Three different paths with different delays from input X to output F
 - If all of gates except the two marked "slow" and "slower" are very fast, the transitions shown in black occur first, and output goes to 0
 - Then, output of "slow" OR gate changes, creating transitions shown in nonitalic color, and output goes to 1
 - Finally, output of "slower" OR gate changes, creating transitions shown in italic color, and output goes to 0
- Dynamic hazards do not occur in a properly designed two-level AND-OR or OR-AND circuit
 - In such a circuit, no variable and its complement are connected to the same first-level gate

-  JOHN F. WAKERLY, *Digital Design: Principles and Practices (4th Edition)*, PRENTICE HALL, 2005.