

Design of Digital Systems II

Sequential-Circuit Design with Verilog

Moslem Amiri, Václav Přenosil

Embedded Systems Laboratory
Faculty of Informatics, Masaryk University
Brno, Czech Republic

`amiri@mail.muni.cz`
`prenosil@fi.muni.cz`

Fall, 2014

- Majority of Verilog-based digital design is directed to clocked, synchronous systems that use edge-triggered flip-flops
- Like combinational behavior, edge-triggered behavior is specified using `always` blocks
 - Difference between combinational and edge-triggered behavior is in sensitivity list of `always` block
 - Keyword `posedge` or `negedge` is placed in front of signal name to indicate that the statements in block should be executed only at positive (rising) or negative (falling) edge of named signal

Table 1: Behavioral Verilog for a positive-edge-triggered D flip-flop.

```
module VrposDff(CLK, D, Q);  
  input CLK, D;  
  output Q;  
  reg Q;  
  
  always @ (posedge CLK)  
    Q <= D;  
endmodule
```

Table 2: Behavioral Verilog for a positive-edge-triggered D flip-flop with preset and clear.

```
module Vrposdffpc(CLK, PR_L, CLR_L, D, Q);  
  input CLK, PR_L, CLR_L, D;  
  output Q;  
  reg Q;  
  
  always @ (posedge CLK or negedge PR_L or negedge CLR_L)  
    if (PR_L==0) Q<= 1;  
    else if (CLR_L==0) Q <= 0;  
    else Q <= D;  
endmodule
```

- Tab. 2 models a positive edge-triggered D flip-flop with asynchronous active-low preset and clear inputs
 - An edge-sensitivity keyword, `negedge`, is applied to a level, asynchronous input
 - Verilog compilers are set up to recognize this particular representation of edge-triggered-plus-asynchronous behavior, and in synthesis they will pick up right flip-flop component to implement it

Table 3: Two modules for a positive-edge-triggered D ff with a QN output.

```
module VrposDffQN1(CLK, D, Q, QN);
    input CLK, D;
    output Q, QN;
    reg Q, QN;

    always @ (posedge CLK) begin
        Q <= D; QN <= !D;
    end
endmodule

module VrposDffQN2(CLK, D, Q, QN);
    input CLK, D;
    output Q, QN;
    reg Q, QN;

    always @ (posedge CLK)
        Q <= D;
    always @ (Q)
        QN <= !Q;
endmodule
```

• Tab. 3

- A typical synthesis tool infers two separate D flip-flops from the first module—one for Q and the other for QN
- For the second module, QN is generated from Q using an inverter

- Always use nonblocking assignments (\leq) in sequential `always` blocks
 - In programs with multiple sequential `always` blocks using *blocking* assignments ($=$), simulation results can vary depending on the order in which the simulator chooses to execute those blocks
 - Using *nonblocking* assignments ensures that righthand sides of all assignments are evaluated before new values are assigned to any of lefthand sides
 - This makes results independent of order in which righthand sides are evaluated

Table 4: Clock generation within a test bench.

```
`timescale 1 ns / 1 ns
module mclkgen(MCLK);
    output MCLK;
    reg MCLK;

    initial begin
        MCLK = 1; // Start clock at 1 at time 0
    end

    always begin          // 10 ns clock generation
        #6 MCLK = 0;      // 6 ns HIGH
        #4 MCLK = 1;     end; // 4 ns LOW

endmodule
```

- Tab. 4 shows generation of a 100-MHz clock with a 60% duty cycle
 - At time 0, MCLK is set to 1 by initial block
 - Then, always block waits 6 ns, sets MCLK to 0, waits 4 ns, sets MCLK to 1, and repeats forever
 - `timescale directive is used to set up the simulator both a default time unit and a precision of 1 ns

- There are many possible coding styles for creating state machines in Verilog, including using no consistent style at all
 - Without discipline of a consistent coding style, it is easy to write syntactically correct code where simulator's operation, synthesized hardware's operation, and what we think the machine should be doing are all different
- In *Verilog state-machine coding style*, code is divided into three parts
 - *State memory*
 - This can be specified in behavioral form using an always block that is sensitive to a signal edge
 - Or it can use a structural style with explicit flip-flop instantiations
 - *Next-state (excitation) logic*
 - This is written as a combinational always block whose sensitivity list includes machine's current state and inputs
 - This block usually contains a case statement that enumerates all values of current state
 - *Output logic*
 - This is another combinational always block that is sensitive to current state and inputs
 - It may or may not include a case statement, depending on complexity of output function

State-Machine Design with Verilog

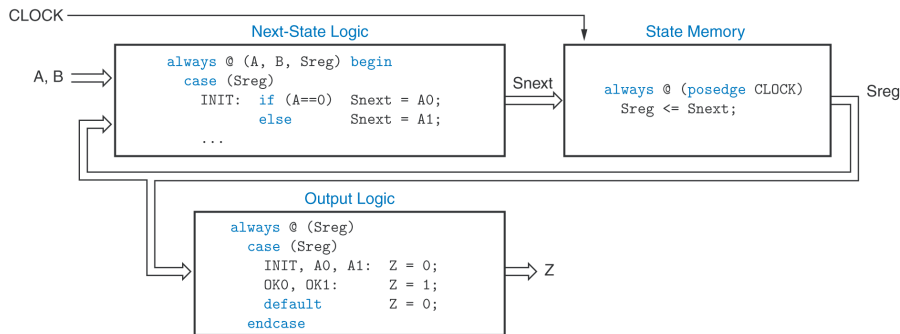


Figure 1: Moore state-machine structure implied by Verilog coding style.

- Detailed coding within each section may vary
 - When there is a tight coupling of next-state and output-logic specifications, it may be desirable to combine them into a single combinational always block, and into a single case statement
 - When pipelined outputs are used, output memory could be specified along with state memory, or a separate process or structural code could be used

A Verilog State-Machine Example

- Design a clocked synchronous state machine with two inputs, A and B, and a single output Z that is 1 if
 - A had the same value at each of two previous clock ticks, or
 - B has been 1 since the last time that the first condition was trueOtherwise, output should be 0
- One approach to writing a program is to construct a state and output table by hand and then manually convert it into a corresponding program

Table 5: State and output table for the example state machine.

<i>S</i>	<i>A B</i>				<i>Z</i>
	<i>00</i>	<i>01</i>	<i>11</i>	<i>10</i>	
INIT	A0	A0	A1	A1	0
A0	OK0	OK0	A1	A1	0
A1	A0	A0	OK1	OK1	0
OK0	OK0	OK0	OK1	A1	1
OK1	A0	OK0	OK1	OK1	1

A Verilog State-Machine Example

Table 6: Verilog program for state-machine example.

```
module VrSMex( CLOCK, A, B, Z );
  input  CLOCK, A, B;
  output Z;
  reg Z;
  reg [2:0] Sreg, Snext; // State register and next state
  parameter [2:0] INIT = 3'b000, // Define the states
                 A0   = 3'b001,
                 A1   = 3'b010,
                 OK0  = 3'b011,
                 OK1  = 3'b100;

  always @ (posedge CLOCK) // Create the state memory
    Sreg <= Snext;

  always @ (A, B, Sreg) begin // Next-state logic
    case (Sreg)
      INIT:  if (A==0) Snext = A0;
              else     Snext = A1;
      A0:    if (A==0) Snext = OK0;
              else     Snext = A1;
      A1:    if (A==0) Snext = A0;
              else     Snext = OK1;
      OK0:   if (A==0) Snext = OK0;
              else if ((A==1) && (B==0)) Snext = A1;
              else     Snext = OK1;
      OK1:   if ((A==0) && (B==0)) Snext = A0;
              else if ((A==0) && (B==1)) Snext = OK0;
              else     Snext = OK1;
    default Snext = INIT;
  endcase
end

  always @ (Sreg) // Output logic
  case (Sreg)
    INIT, A0, A1: Z = 0;
    OK0, OK1:    Z = 1;
  default       Z = 0;
  endcase
endmodule
```

S	A B				Z
	00	01	11	10	
INIT	A0	A0	A1	A1	0
A0	OK0	OK0	A1	A1	0
A1	A0	A0	OK1	OK1	0
OK0	OK0	OK0	OK1	A1	1
OK1	A0	OK0	OK1	OK1	1

S*

A Verilog State-Machine Example

- First always block (state memory creation) in Tab. 6
 - During synthesis, positive-edge-triggered D flip-flops are inferred for Sreg
 - A synchronous or asynchronous RESET signal is easily provided as shown in Tab. 7

Table 7: Synchronous and asynchronous reset for state machines in Verilog.

```
// State memory with active-high synchronous reset
always @ (posedge CLOCK) // Create state memory
    if (RESET==1) Sreg <= INIT; else Sreg <= Snext;

// State memory with active-high asynchronous reset
always @ (posedge CLOCK or posedge RESET) // Create state memory
    if (RESET==1) Sreg <= INIT; else Sreg <= Snext;
```

A Verilog State-Machine Example

- Second always block (next-state logic) in Tab. 6
 - default case at the end handles unused states, but not uncovered input combinations in other cases
 - In each case, an if statement and a final else is used to ensure that a value is always assigned to Snext
 - If there were any state/input combinations in which no value was assigned to Snext, Verilog compiler would infer an unwanted latch for Snext
 - Variations
 - To establish a default next state for machine if case fails to cover all state/input combinations, precede case statement with "Snext = INIT"
 - When most transitions stay in current state, case statement can be preceded by "Snext = Sreg"
 - Preceding with "Snext = 3'bx" is another variation which is useful in simulation to detect unspecified state/input combinations

- Third `always` block (output logic) in Tab. 6
 - Handles machine's single Moore output, Z , which is set to a value as a function of current state
 - To define Mealy output, output should be a function of inputs as well as state in each enumerated case
 - Inputs should also be added to sensitivity list of `always` block
- **Pipelined outputs**
 - In design of high-speed circuits, it is often necessary to ensure that state-machine outputs are available as early as possible and do not change during each clock period
 - One way to get this behavior is to encode state so that state variables themselves serve as outputs
 - Called *output-coded state assignment*
 - It yields a Moore machine in which output logic is wires
 - Another approach is to design state machine so that outputs during one clock period depend on state and inputs during *previous* clock period
 - Called **pipelined outputs**
 - Obtained by attaching another stage of memory (flip-flops) to a machine's outputs

A Verilog State-Machine Example

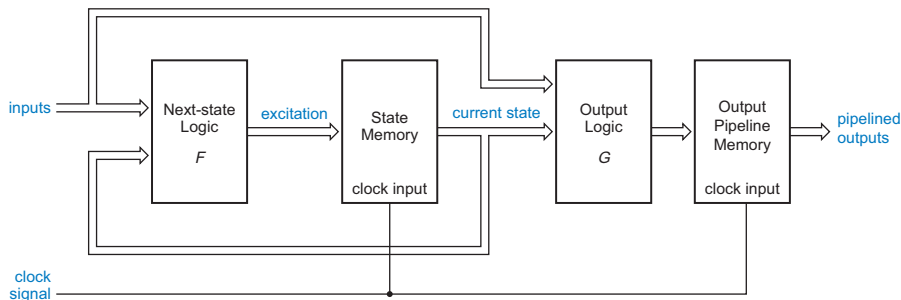


Figure 2: Mealy machine with pipelined outputs.

- In our example Verilog state machine, the module defines a Moore-type state machine with the structure shown in Fig. 1
 - We can convert the machine to have pipelined outputs with the structure shown in Fig. 3
 - To do this, we need only to declare a "next-output" variable Z_n and replace the original Verilog state-memory and output code with code shown in Tab. 8

A Verilog State-Machine Example

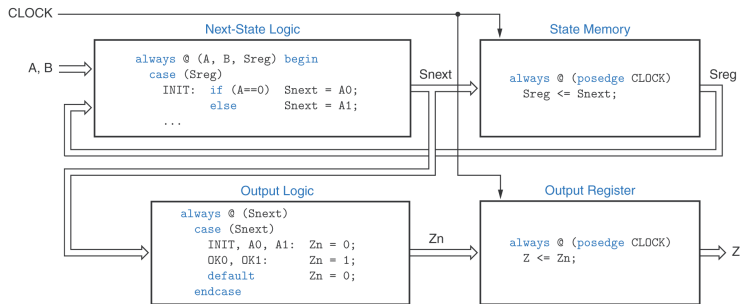


Figure 3: Verilog state machine with pipelined outputs.

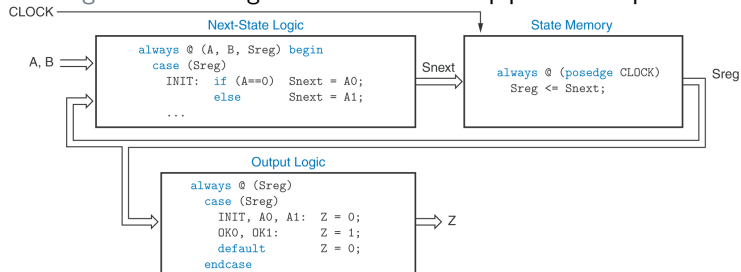


Table 8: Verilog pipelined output code.

```
always @ (posedge CLOCK) // Create output register -- this code
  Z <= Zn; // could be combined with state-memory code if desired

always @ (Snext) // Output logic
  case (Snext)
    INIT, A0, A1: Zn = 0;
    OK0, OK1: Zn = 1;
    default: Zn = 0;
  endcase
```

- New machine's behavior is indistinguishable from that of original machine, except for timing
 - We have reduced propagation delay from CLOCK to Z by producing Z directly on a register output
 - But we have increased setup-time requirements of A and B to CLOCK
 - In addition to their propagation delay through next-state logic, changes in A and B must also get through output logic in time to meet setup time requirement of output flip-flop's D input

A Verilog State-Machine Example

- Direct Verilog coding without a state table
 - It is possible to write a Verilog program directly, without writing out a state table by hand
 - Design a clocked synchronous state machine with two inputs, A and B, and a single output Z that is 1 if
 - A had the same value at each of two previous clock ticks, or
 - B has been 1 since the last time that the first condition was true

Otherwise, output should be 0

 - We need to have a register that keeps track of A (LASTA)
 - Three states must be defined
 - INIT
 - LOOKING: still looking for a match
 - OK: got a match or B has been 1 since last match

Table 9: Simplified Verilog state-machine design.

```
module VrSMexa( CLOCK, RESET, A, B, Z );
  input  CLOCK, RESET, A, B;
  output Z;
  wire Z;           // declared as wire for continuous assignment
  reg  LASTA;       // LASTA holds last value of A
  reg  [1:0] Sreg, Snext; // State register and next state
  parameter [1:0] INIT    = 2'b00, // Define the states
                LOOKING   = 2'b10,
                OK        = 2'b11;

  always @ (posedge CLOCK) begin // State memory (with sync. reset)
    if (RESET==1) Sreg <= INIT; else Sreg <= Snext;
    LASTA <= A;
  end

  always @ (A, B, LASTA, Sreg) begin // Next-state logic
    case (Sreg)
      INIT:    Snext = LOOKING;
      LOOKING: if (A==LASTA) Snext = OK;
               else Snext = LOOKING;
      OK:     if (B==1 || A==LASTA) Snext = OK;
               else Snext = LOOKING;
      default: Snext = INIT;
    endcase
  end

  assign Z = (Sreg==OK) ? 1 : 0; // Output logic
endmodule
```

- Tab. 9
 - First always block creates both state memory and LASTA register
 - Second one creates next-state logic using our simplified approach
 - Z output is a simple combinational decode of OK state, so it is created using a continuous-assignment statement

- Ones-counting machine
 - Design a clocked synchronous state machine with two inputs, X and Y, and one output, Z
 - Output should be 1 if the number of 1 inputs on X and Y since reset is a multiple of 4, and 0 otherwise
- We can write a Verilog module for this problem directly, without constructing a state table

Table 10: Verilog module for a ones-counting machine.

```
module VronesCnt( CLOCK, RESET, X, Y, Z );
  input CLOCK, RESET, X, Y;
  output Z;
  wire Z;           // declared as wire for continuous assignment
  reg [1:0] COUNT, NEXTCNT; // Current and next count, modulo 4
  parameter [1:0] ZERO = 2'b00;

  always @ (posedge CLOCK) // State memory (with sync. reset)
    if (RESET==1) COUNT <= ZERO; else COUNT <= NEXTCNT;

  always @ (COUNT, X, Y) // Counting logic
    NEXTCNT = COUNT + {1'b0, X} + {1'b0, Y};

  assign Z = (COUNT==ZERO) ? 1 : 0; // Output logic
endmodule
```

- In synthesis, counting logic in Tab. 10 does not necessarily yield a compact or speedy circuit
 - With a simple tool, it could yield two 2-bit adders connected in series
 - A good tool may be able to synthesize a more compact incrementer for each of the two additions
 - Another approach is to replace NEXTCNT always block with the one shown in Tab. 11
 - Formulating the choices in a case statement makes for a faster circuit, allowing the two adders or incrementers to operate in parallel
 - A multiplexer can be used to select one of outputs according to choices
 - To ensure that only one full adder is synthesized, we use code shown in Tab. 12

Table 11: Alternative Verilog counting logic for ones-counting machine.

```
always @ (COUNT, X, Y) case ({X, Y}) // Counting logic
    2'b01, 2'b10: NEXTCNT = COUNT + 2'b01;
    2'b11:       NEXTCNT = COUNT + 2'b10;
    default     NEXTCNT = COUNT;
endcase
```

Table 12: Fastest and smallest Verilog counting logic for ones-counting machine.

```
always @ (COUNT, X, Y) begin // Counting logic
    XY1s[0] = X ^ Y;
    XY1s[1] = X & Y;
    NEXTCNT = COUNT + XY1s;
end
```

- Tab. 12
 - A 2-bit reg variable XY1s is declared
 - The two equations create a half adder
 - Only one full adder is synthesized

- Combination-lock state machine

- Design a clocked synchronous state machine with one input, X , and one output, UNLK

UNLK output should be 1 if and only if X is 0 and the sequence of inputs received on X at preceding seven clock ticks was 0110111

- Output of the machine at any time is completely determined by its inputs during current and preceding seven clock ticks
 - Thus, we use a "finite-memory" approach to design this machine
 - With this approach, we explicitly keep track of past seven inputs and then form output as a combinational function of these and current inputs
- Tab. 13
 - This module keeps track of last seven values of X using a "shift register"
 - Bits are shifted left on each clock tick
 - Next-state logic is put into the same `always` block as state memory
 - `XHISTORY` is initialized to all 1s at reset so the user does not get benefit of a "free" 0 right after reset to begin combination pattern

Table 13: Verilog module for finite-memory design of combination-lock state machine.

```
module Vrcomblock( CLOCK, RESET, X, UNLK );
  input  CLOCK, RESET, X;
  output UNLK;
  wire  UNLK;          // declared as wire for continuous assignment
  reg [7:1] XHISTORY; // 7-tick history of X
  parameter [7:1] COMBINATION = 7'b0110111;

  always @ (posedge CLOCK) // State memory (with sync. reset)
    if (RESET==1) XHISTORY <= 7'b1111111;
    else XHISTORY <= {XHISTORY[6:1], X}; // next-state logic

  // Output logic -- Detect combination
  assign UNLK = (XHISTORY==COMBINATION && X==0) ? 1 : 0;
endmodule
```




JOHN F. WAKERLY, *Digital Design: Principles and Practices (4th Edition)*, PRENTICE HALL, 2005.