 


## Verilog for Finite State Machines


- Strongly recommended style for FSMs
- Works for both Mealy and Moore FSMs
- You can break the rules
  - But you have to live with the consequences

## Mealy and Moore machines

### ■ Moore



### ■ Mealy

 

## Constructing State Machines in Verilog

- We need register to hold
  - the current state
    - `always @(posedge clk) block`
- We need next state function
  - Where do we go from each state given the inputs
  - state by state case analysis
    - next state determined by current state and inputs
- We need the output function
  - State by state analysis
  - Moore: output determined by current state only
  - Mealy: output determined by current state and inputs

## State Register

- Declare two values
  - `state` : current state – output of state register
  - `nxtState` : next state – input to state register
  - We rely on next state function to give us `nxtState`
- Declare symbols for states with state assignment

```
localparam IDLE=0, WAITFORB=1,  
           DONE=2, ERROR=3;  
  
reg [1:0] state, // Current state  
       nxtState; // Next state
```

## State Register

- Simple code for register
  - Define reset state
  - Otherwise, just move to `nxtState` on clock edge

```
localparam IDLE=0, WAITFORB=1,
           DONE=2, ERROR=3;
reg [1:0] state, // Current state
        nxtState; // Next state

always @(posedge clk) begin
  if (reset) begin
    state <= IDLE; // Initial state
  end else begin
    state <= nxtState;
  end
end
```

## Next State Function

- Combinational logic function
  - Inputs : state, inputs
  - Output : `nxtState`
- We could use assign statements
- We will use an `always @(*)` block instead
  - Allows us to use more complex statements
  - `if`
  - `case`

## always @(\*) Block

- Used for combinational logic functions
- Is always active – like assign statements
- Assignment ( = ) used to assign function value
- Output can be assigned more than once
  - e.g. multiple if statements
  - The last one counts
- **All outputs must be assigned at least once**
  - No matter how ifs and cases are executed
  - Otherwise function is undefined
  - Use default assignments to help you

## Next State Function

- Describe what happens in each state
- Case statement is natural for this


```
always @(*) begin
    nxtState = state; // Default next state: don't move
    case (state)
        IDLE : begin
            if (B) nxtState = ERROR;
            else if (A) nxtState = WAITFORB;
        end
        WAITFORB : begin
            if (B) nxtState = DONE;
        end
        DONE : begin
        end
        ERROR : begin
        end
    endcase
end
```

## Output Function

- Describe the output of each state

```
always @(*) begin
  nxtState = state; // Default next state: stay where we are
  out = 0;         // Default output
  case (state)
    IDLE : begin
      if (B) nxtState = ERROR;
      else if (A) nxtState = WAITFORB;
    end
    WAITFORB : begin
      if (B) nxtState = DONE;
    end
    DONE : begin
      out = 1;
    end
    ERROR : begin
    end
  endcase
end
```

## Example #2 : Edge Detector (Moore)

 

```
localparam A=0, B=1, C=2, D=4, E=5;
reg [2:0] state, // Current state
      nxtState; // Next state
```


```
always @(posedge clk) begin
  if (reset) begin
    state <= A; // Initial state
  end else begin
    state <= nxtState;
  end
end
```

## Example #2 : Edge Detector (Moore)

```

always @(*) begin
  nxtState = state;
  out = 0;
  case (state)
    A : if (in) nxtState = C;
        else nxtState = B;
    B : if (in) nxtState = D;
    C : if (~in) nxtState = E;
    D : begin
        out = 1;
        if (in) nxtState = C;
        else nxtState = E;
      end
    E : begin
        out = 1;
        if (in) nxtState = D;
        else nxtState = B;
      end
    default : begin
        out = 1'bX;
        nxtState = 3'bX;
      end
  endcase
end

```

 


## Example #2 : Edge Detector (Moore)

- Using state assignment for output
  - Only works for Moore FSM


```

always @(*) begin
  nxtState = state;
  out = state[2];
  case (state)
    A : if (in) nxtState = C;
        else nxtState = B;
    B : if (in) nxtState = D;
    C : if (~in) nxtState = E;
    D : if (in) nxtState = C;
        else nxtState = E;
    E : if (in) nxtState = D;
        else nxtState = B;
    default : nxtState = 3'bX;
  endcase
end

```

 

## Example #2 : Edge Detector (Mealy)

 


```
localparam A=0, B=1, C=2;
reg [1:0] state, // Current state
nxtState; // Next state

always @(posedge clk) begin
    if (reset) begin
        state <= A; // Initial state
    end else begin
        state <= nxtState;
    end
end
```
 
## Example #2 : Edge Detector (Moore)

- Output depends on state and input

```
always @(*) begin
    nxtState = state;
    out = 0;
    case (state)
        A : if (in) nxtState = C;
            else nxtState = B;
        B : if (in) begin
                out = 1;
                nxtState = C;
            end
        C : if (~in) begin
                out = 1;
                nxtState = B;
            end
        default : begin
                out = 1'bX;
                nxtState = 3'bX;
            end
    endcase
end
```



## Summary

- Please use “standard” FSM Verilog style shown here
  - Do not be beguiled into thinking this is programming C!
  
- `always @ (posedge clk)` block
  - Use only for registers with simple logic
  - e.g. shifter, counter, enabled register, etc.
  
- Miscellaneous combinational logic
  - `assign` statements (always safe)
  - `always @ (*)` block (be very careful)
    - Think of this as a complex `assign` statement
    - Fine to have more than one