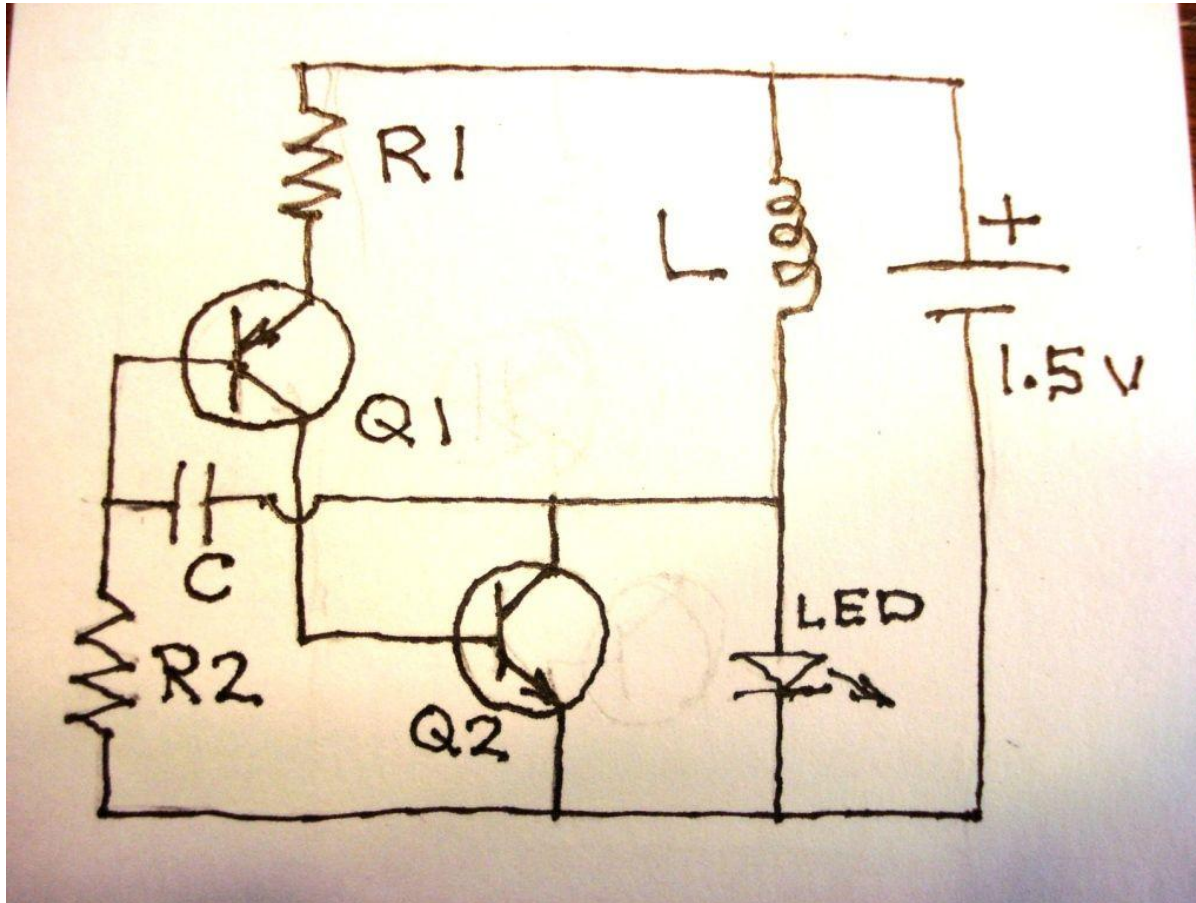


How to light a LED

Workshop on Joule-thief circuit



1. The Circuit





<http://www.instructables.com/id/Joule-Thief-no-IC-and-no-Transformer/>

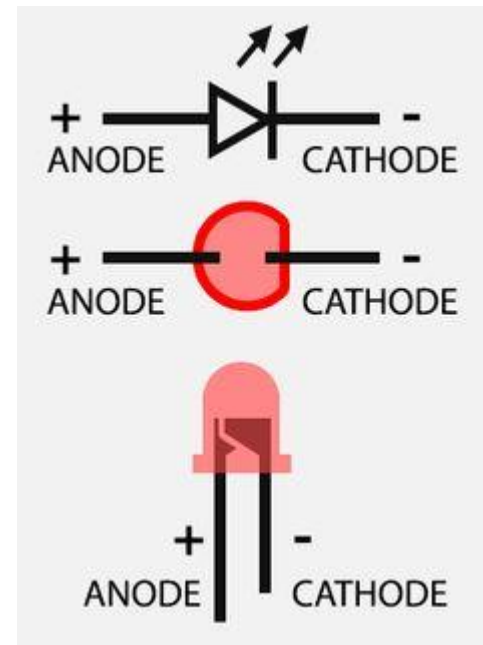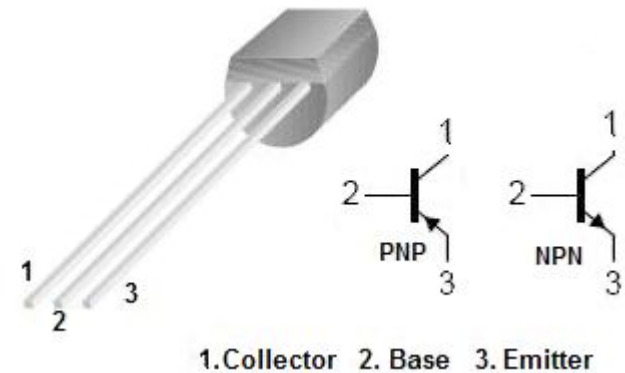2. Identify parts

- R1 resistor 1K (BRK/G)
- R2 resistor 33K (OOO/G)
- C1 capacitor 1 nF
- Q1 BC557 PNP transistor
- Q2 BC457 NPN transistor
- L1 330 microH inductor (OOR/G)
- D1 LED diode
- BAT 1,5 V AAA battery



3. Begin assembly

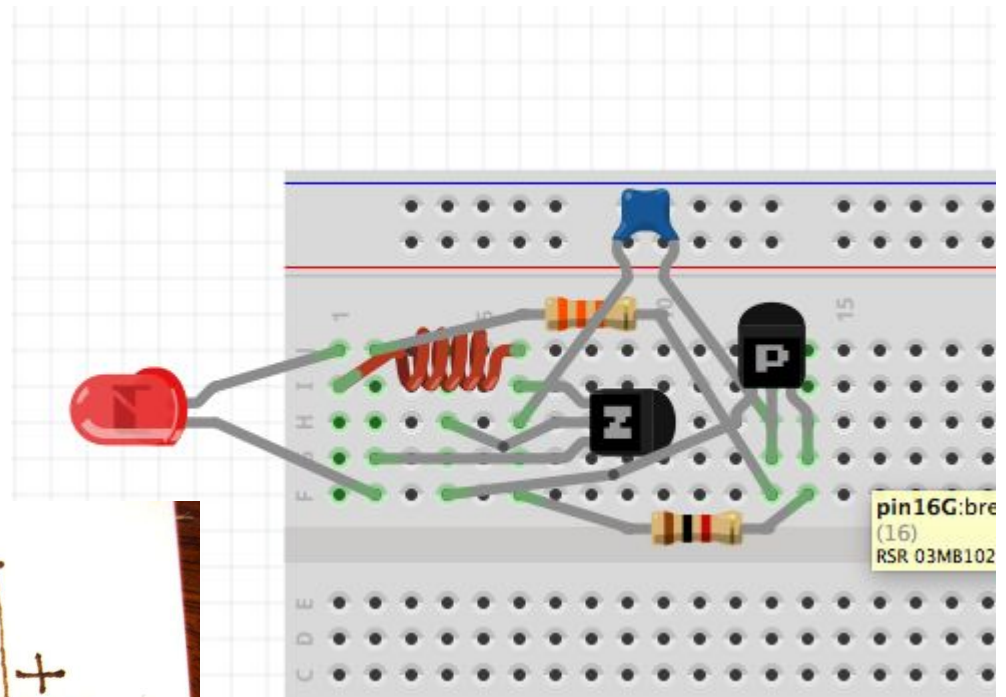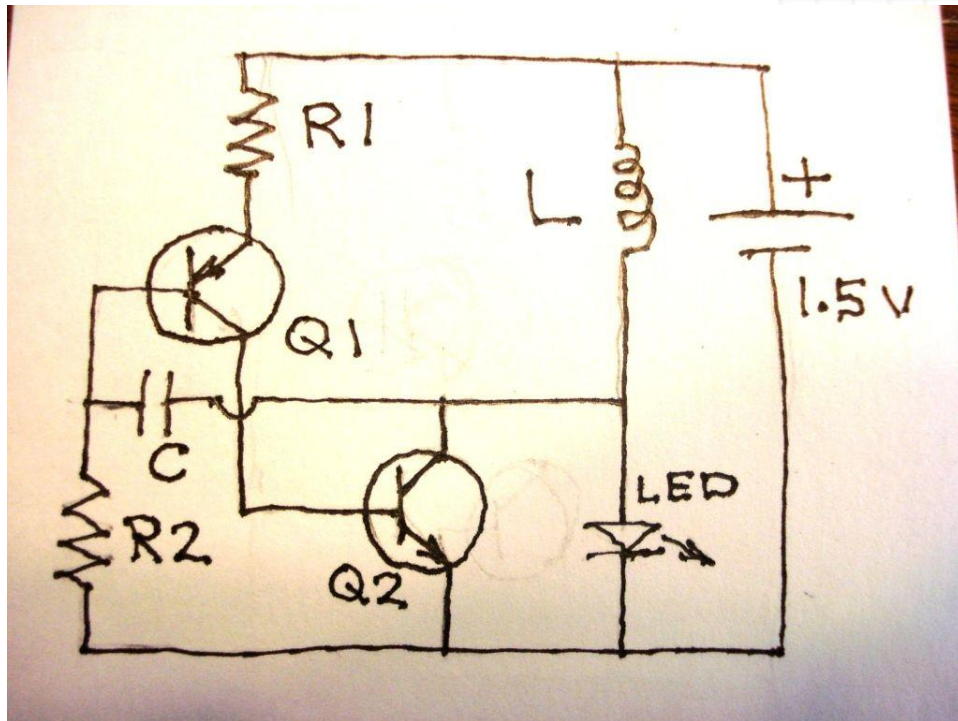

How it works?!

"Ohm's Law" for an inductor

$$v = L \frac{di}{dt}$$

Where,

v = Instantaneous voltage across the inductor

L = Inductance in Henrys

$\frac{di}{dt}$ = Instantaneous rate of current change
(amps per second)