

PH Pädagogische Hochschule Wien



PHOTOVOLTAICS EXPERIMENTS

I.Hantschk/H.Fibi 2009

IP EFEU LLP/AT-230/22/08



ΓΔ Εκπαίδευση και πολιτισμός



GD Bildung und Kultur

Permission to use is granted on the following conditions:

The use is for educational purposes only

No fees or other income is charged

Appropriate reference to this source is made.

Data sources are indicated except pictures and drawings having been taken by the authors respectively publishers.

Published by

OStR. Mag.rer.nat. Hans Fibi & Prof. Ingrid Hantschk

University of Education Vienna

Grenzackerstraße 18

1100 Vienna

Austria

Phone: +436643833955


e-mail: Hans210347@a1.net or johann.fibi@phwien.ac.at

2009


Updated for LLP/AT-230/22/08

This project has been funded with support from the European Commission.

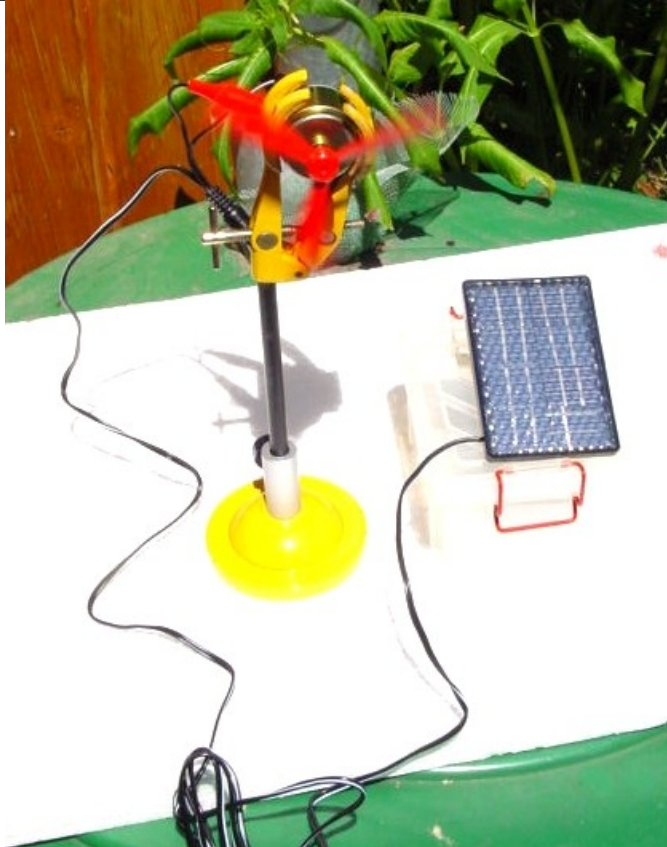This publication [communication] reflects the views only of the author, and the Commission cannot be held responsible for any use which may be made of the information contained therein.




Solar Cell at work)

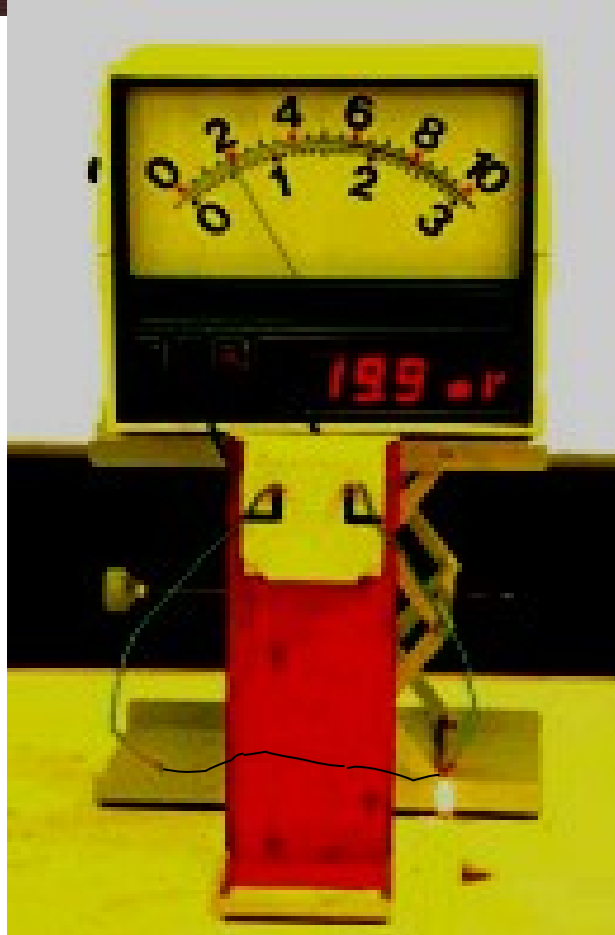

Thermocouple
(Candle instead of
concentrated
sunlight)

intrinsic conduction

traditional schedule

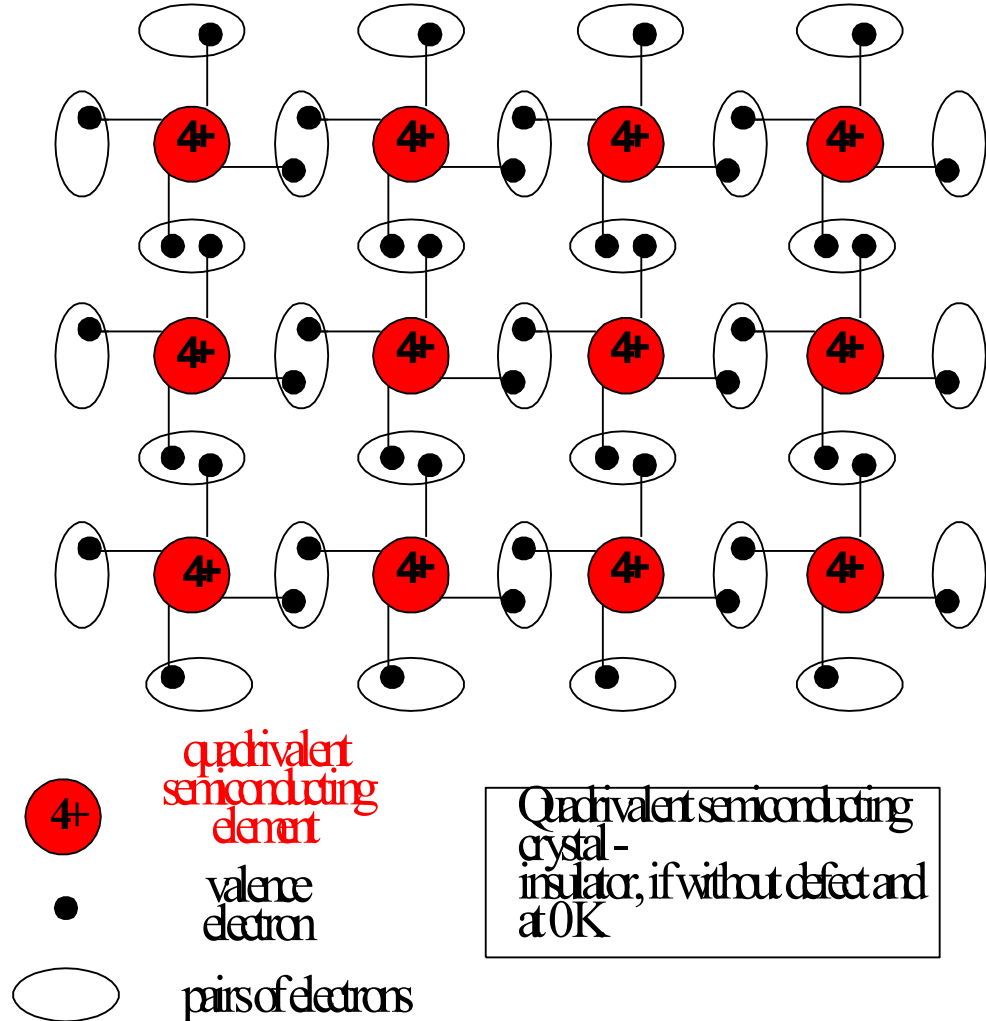

**Lattice of the diamond-type
Because of defects in the crystal and
at rising temperature - input of caloric energy -
some electrons are set free -
the crystal shows intrinsic conduction.**

**Matter: Silicon, Indiumphosphide, Galliumarsenide,
Cadmiumtelluride**

New: Compounds as III-V or II-VI type or organic compounds

Doped Semiconductors


Electrons move to the defective electron (hole)

deficit of electrons

excess of electrons

n-doped

p-doped

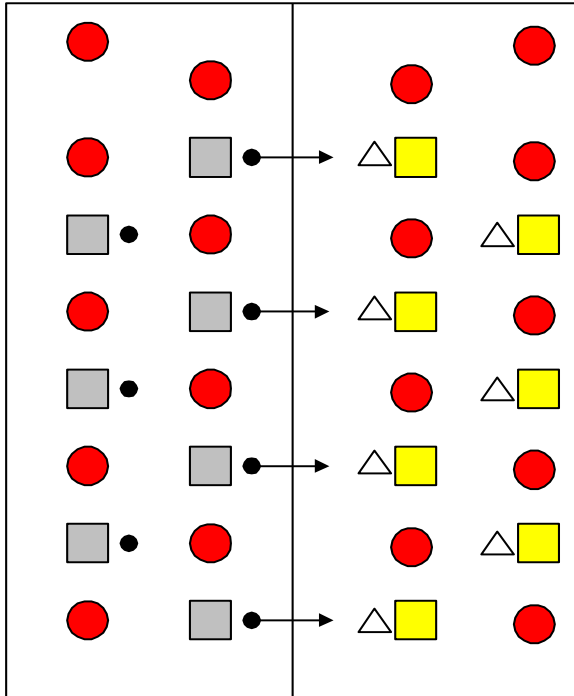


n-doped

+

-

p-doped

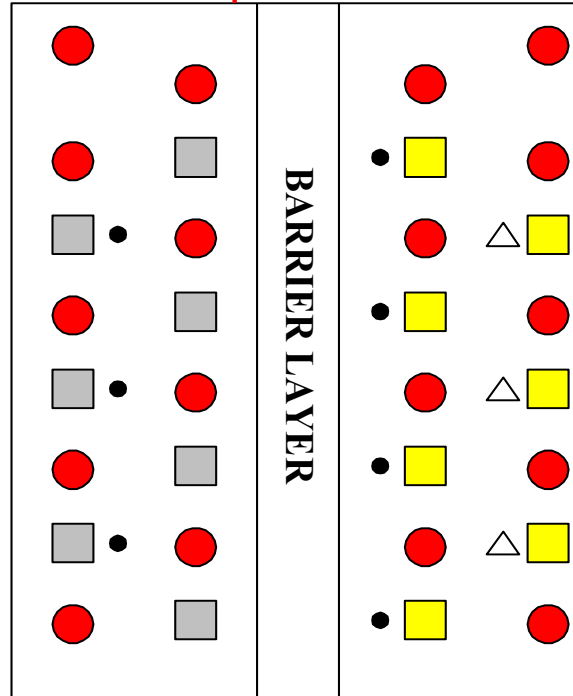

quadrivalent atom


the fifth electron is not used for binding

trivalent atom

electron hole in the lattice (grid)

quivalent atom

moving direction of the electrons

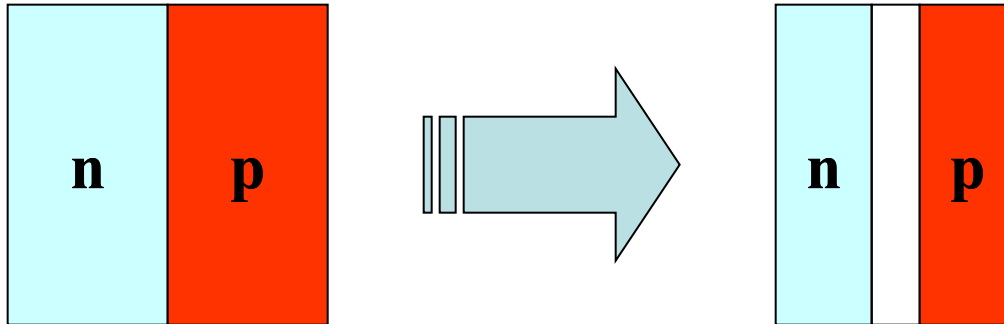


intrinsic (reverse) voltage

There must be:

A carrier – usually a crystal grating

n-layer – providing electrons

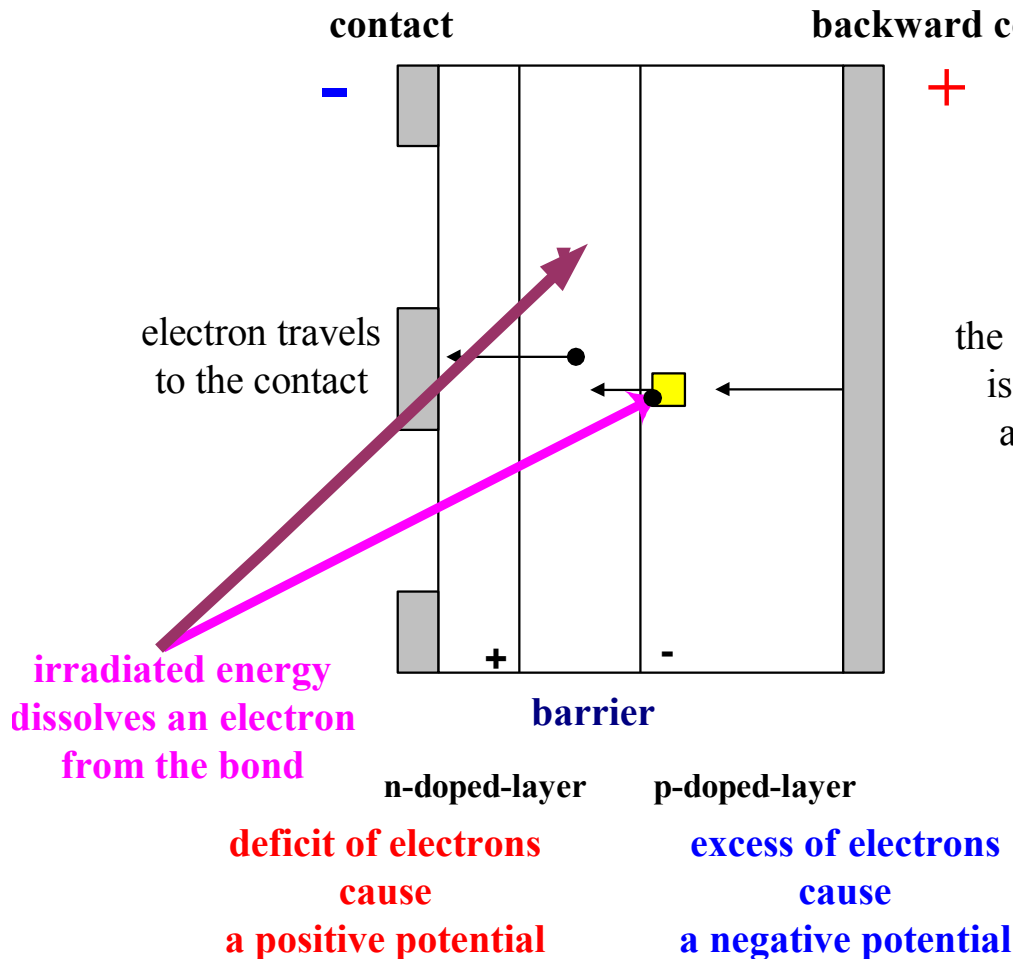
p-layer – providing places for the electrons on travel



the electron hole is refilled by an electron

For generating photovoltage, you need:

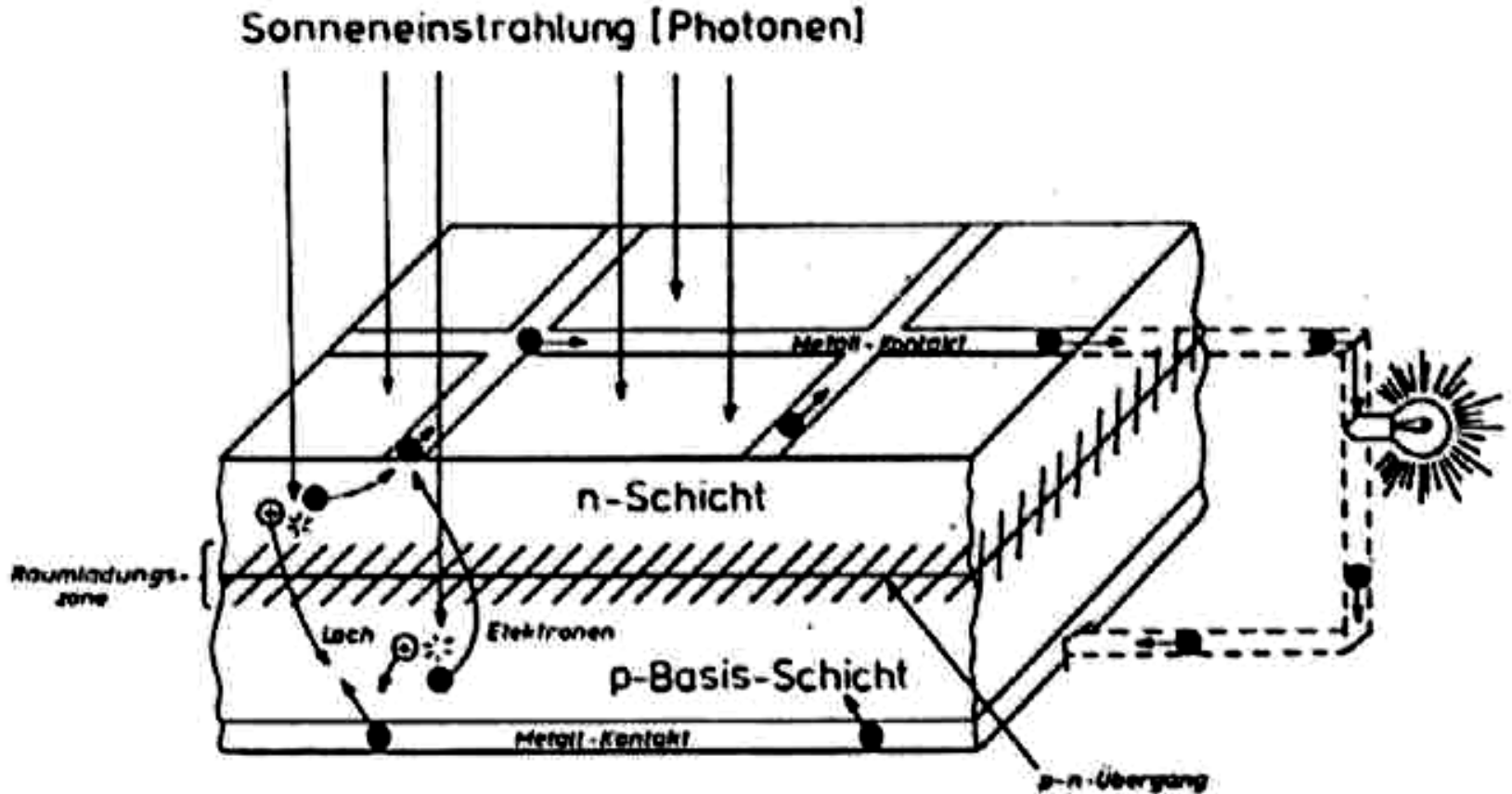- ↳ matter, from which photons are able to dissolve electrons: Si, Ge, semiconducting compounds (InSb, InP, GaAs, GaAsP, CdS, CdTe).
- ↳ Intrinsic potential difference being able to separate the electrons from the positive defective electrons.



The band gaps are:

Si...1,12 eV

maximum of sensitivity: red

long wave limit: IR 1,1 μm

above translucent

Ge...0,7 eV

GaAs...1,42 eV

CdTe...1,5 eV

GeS.....1,5 eV

InSb...0,2 eV (IR)

Efficiencies at 1 kW/m²:
c-Si (crystal Si).....max 28 %
practically 18 %
mc-Si (multicrystal-Si)...16 %
a-Si (amorphous Si)...13-17%




*Solarzelle
polykristallin*

*Solarzelle
monokristallin*



The LED - forward and reverse biased

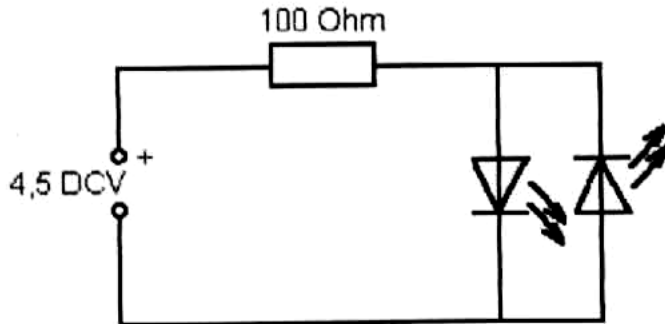

Which of both LEDs is shining ?
Change the poles of the battery
(pole reversal).

Which of the LEDs shines now ?

Remove one of the LEDs.

Measure the drop in voltage cross the LED.

The LED is forward biased, it shines:

$$U = \dots\dots\dots V$$



The LED is reverse biased.

$$U = \dots\dots\dots V$$

If the LED is reverse biased, a high drop in voltage





is to be found cross the LED.

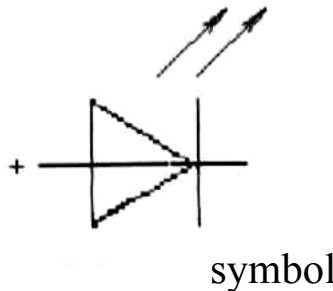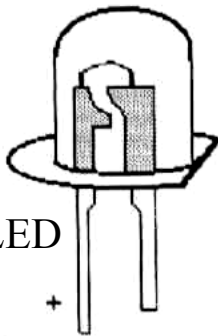
This picture allows you to find out the correct positioning of the LED





Forward voltage drop...measured at the forward biased LED, necessary to force charges passing the LED

The LED - forward and reverse biased

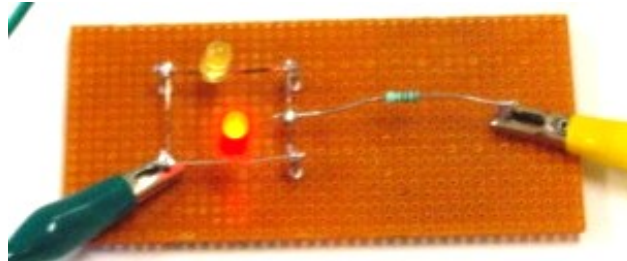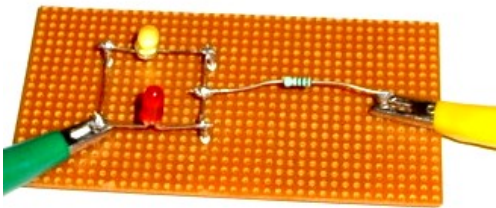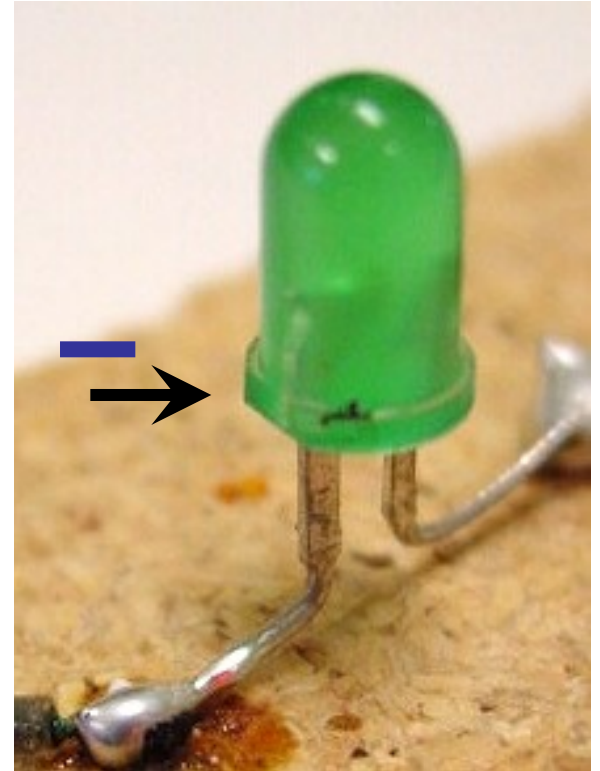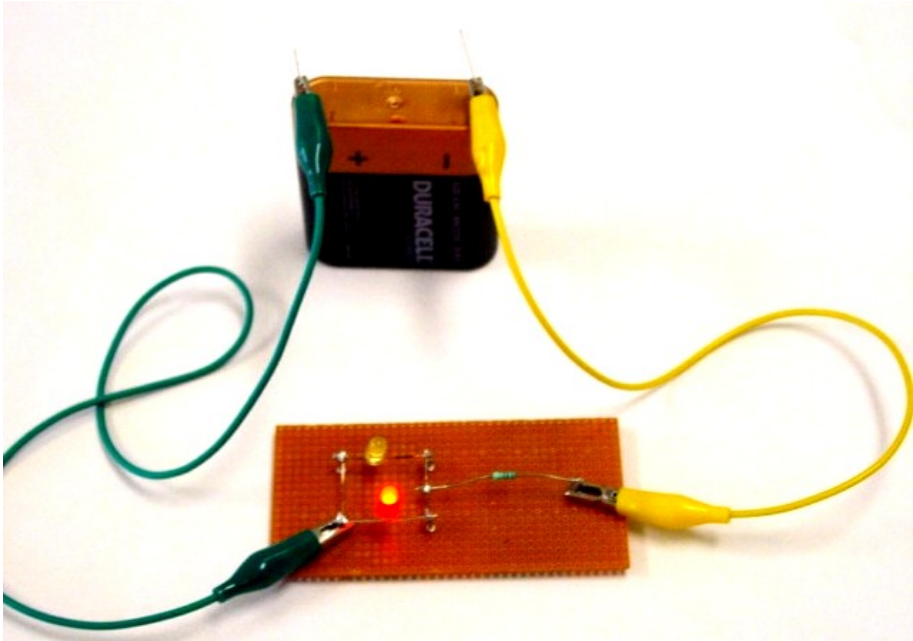

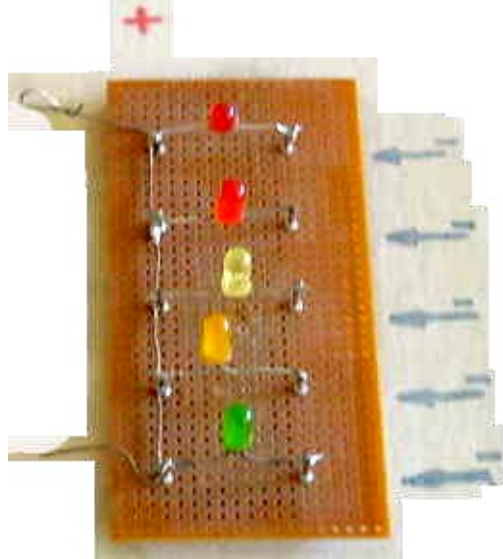

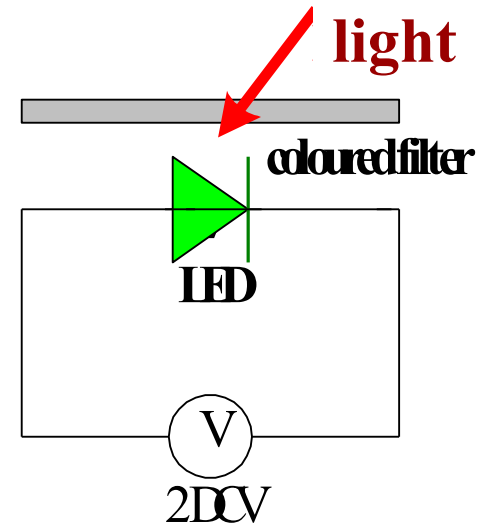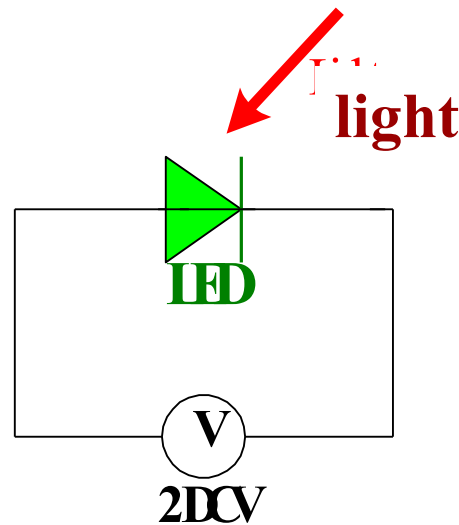Measurement of the voltage generated by irradiation:




LEDred	$U = \dots\dots\dots$ V
LEDgreen	$U = \dots\dots\dots$ V
LED.....	$U = \dots\dots\dots$ V

Note, to which part of the spectrum the different LEDs are sensitive.

	Filter red	Filter green	Filter blue
LEDred	$U = \dots\dots\dots$ V	$U = \dots\dots\dots$ V	$U = \dots\dots\dots$ V
LEDgreen	$U = \dots\dots\dots$ V	$U = \dots\dots\dots$ V	$U = \dots\dots\dots$ V
LED.....	$U = \dots\dots\dots$ V	$U = \dots\dots\dots$ V	$U = \dots\dots\dots$ V



The so generated voltage is called photoelectric voltage.

The LED as Photovoltaic Cell

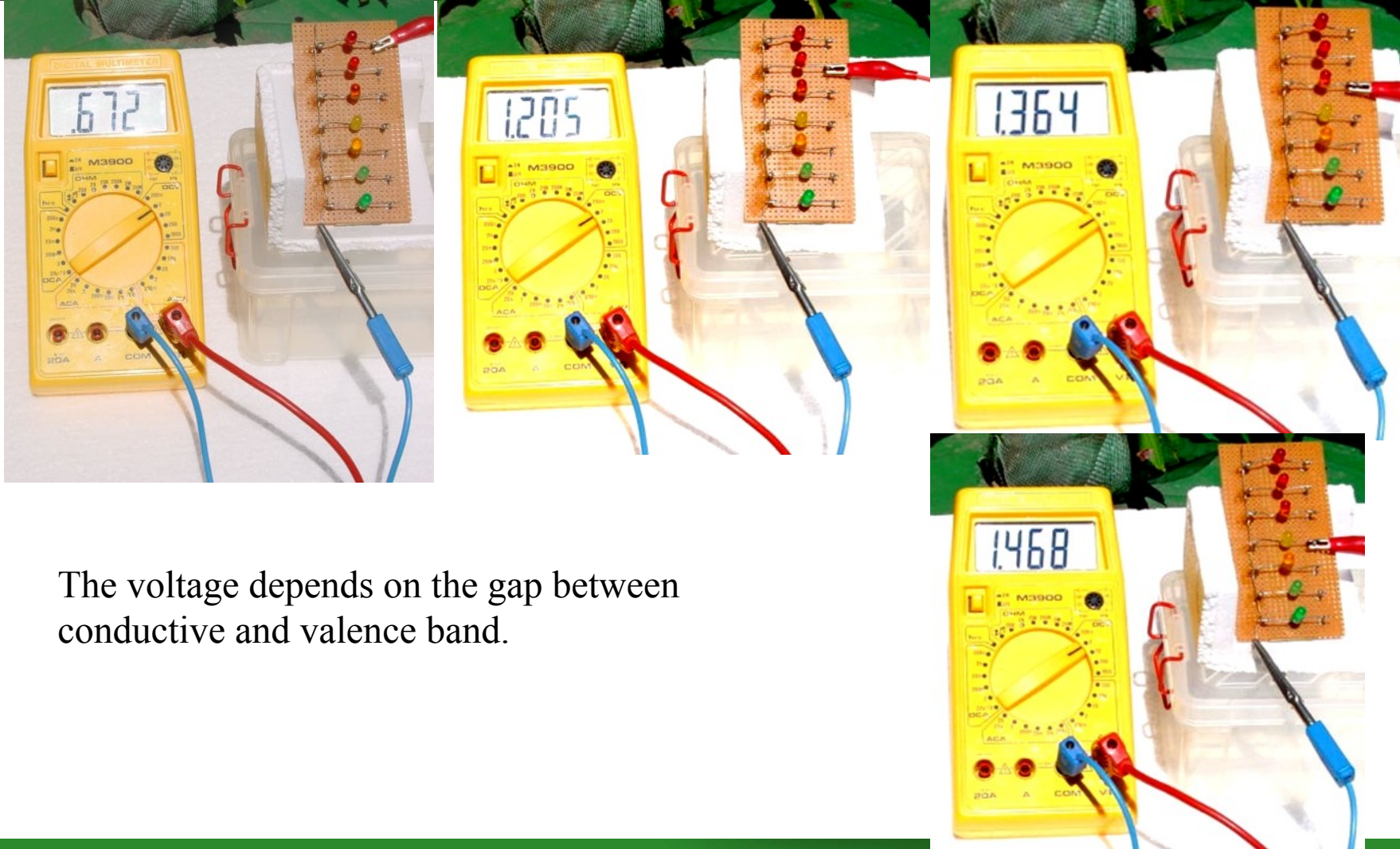


The voltage depends on the gap between conductive and valence band.

The LED as Photovoltaic Cell

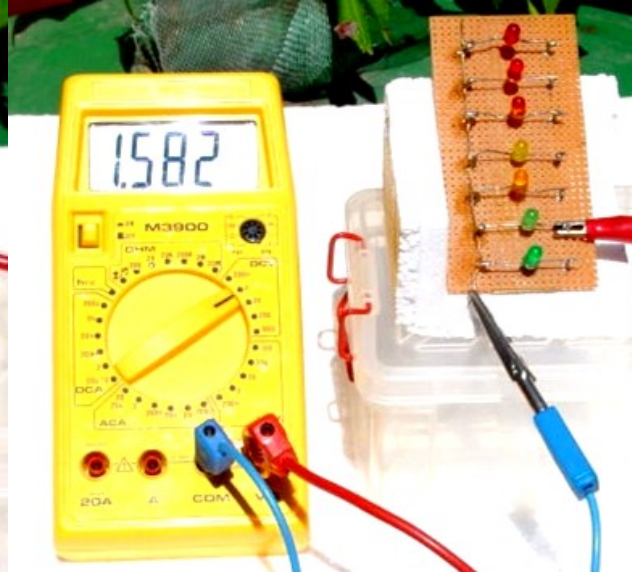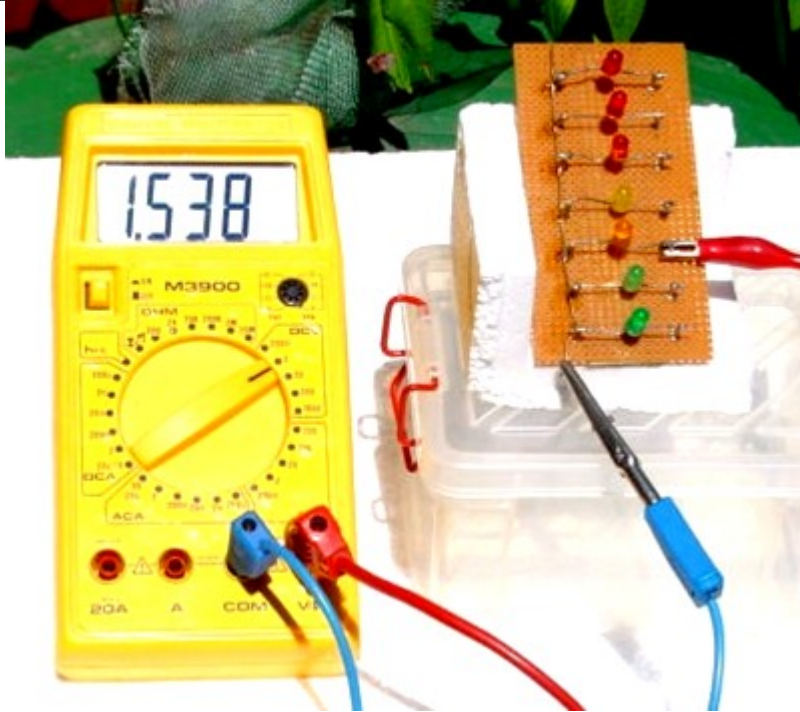


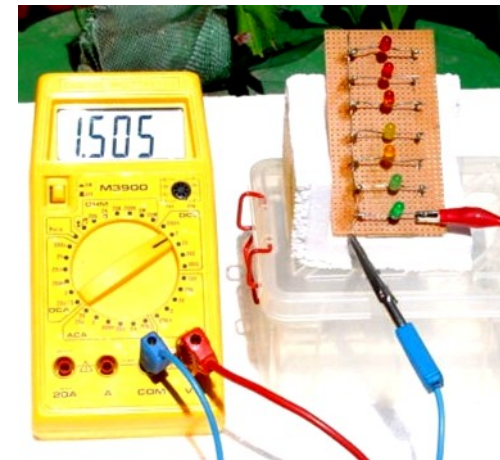**Relatively high Voltage, but...
....about no capacity !!**



The LED is used as PHOTODIODE

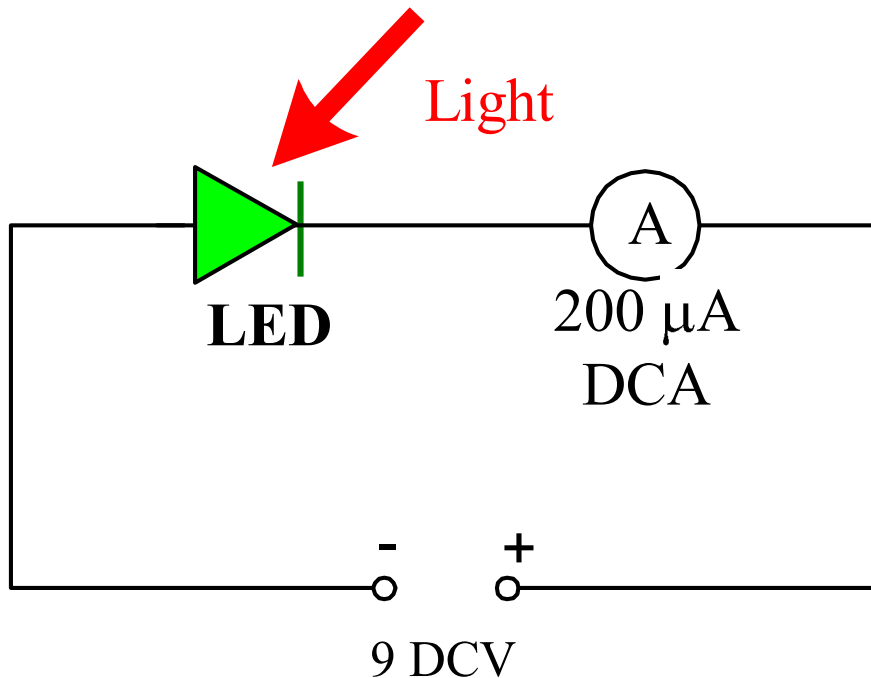The LED is connected into the circuit **reverse biased!!**



Expose the LED to an intensive radiation. The intensity of current is $I = \dots \mu\text{A}$.

Now vary the irradiance only a bit.

In doing this observe the current's intensity.


The result

is:.....

Application: very sensitive exposure meter

The solar cell is reverse biased. Do not use more than 3 DCV.

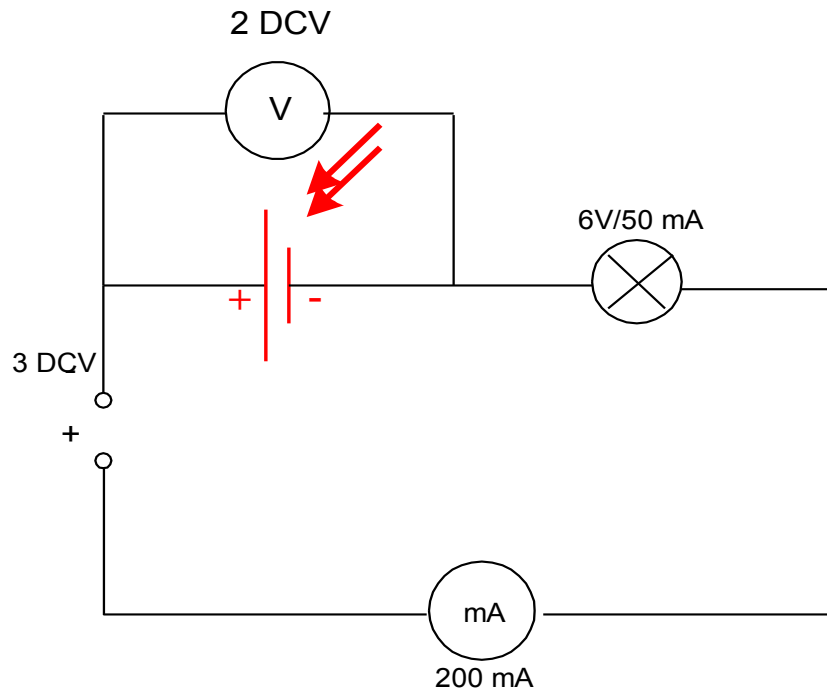
Only use a little surface, if necessary cover the surface partially with a cardboard.



**If the solar cell is shadowed,
it has a
high internal resistance
because of
a high drop in voltage.**

	U (V)	I (mA)	R (Ohm)
Solar Cell exposed to daylight			
Solar Cell totally darkened			

Resistance of a Solar Cell

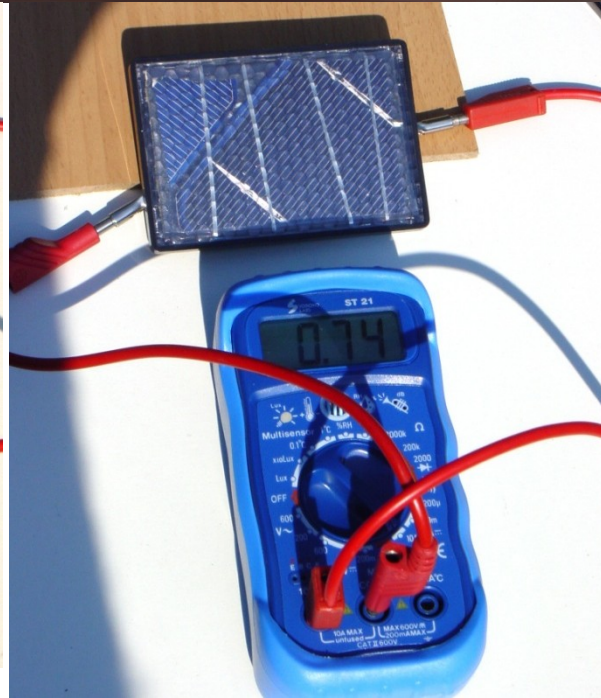

Direct sunshine: $U = 0,55\text{V}$, $I = 0,74\text{ A}$
 $R = 0,8\text{ Ohm}$



Shadowed: $U = 0,47\text{V}$, $I = 0,067\text{ A}$
 $R = 7\text{ Ohm}$



Solar Cells connected in series, one of them being shadowed → bypass diode is necessary.

Darkened: $U = 0,11\text{V}$, $I = 0,0012\text{ A}$
 $R = 92\text{ Ohm}$

Open-Circuit-Voltage of a Solar Cell

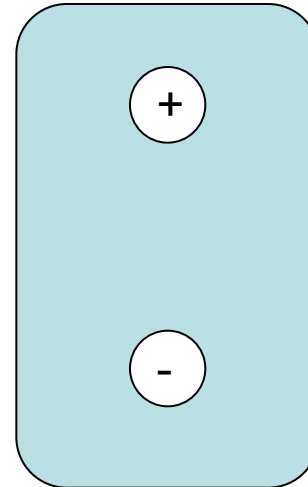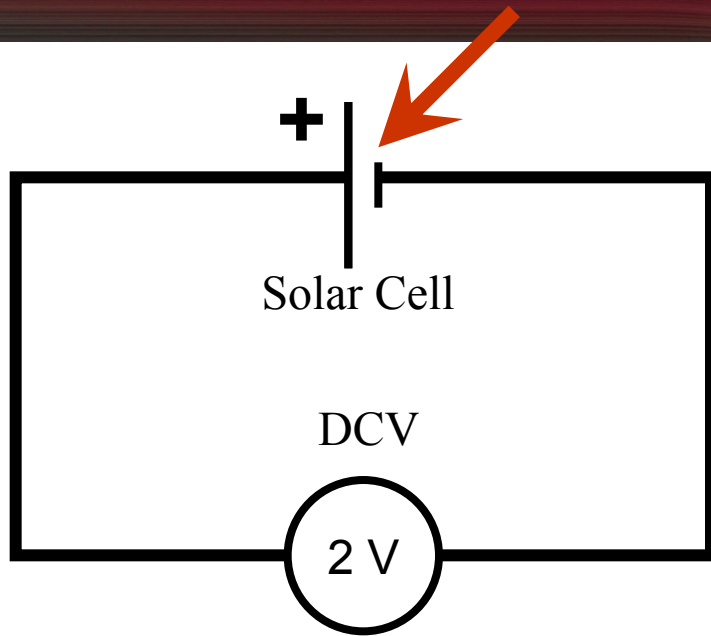

back side
with
connections

	U in V
dim room	
bright room	
shadow	
sun	

The open circuit voltage is measured at different irradiances.

	Irradiance	Open-Circuit-Voltage in V
Sun	$I = 1040 \mu\text{A}$	
Shadow	$I = 450 \mu\text{A}$	
Indoor	$I = 13 \mu\text{A}$	

$$U_{\max} = \dots\dots\dots \text{DCV}$$

You may draw a diagram now.

Open-Circuit-Voltage of a Solar Cell



bright sun: $U = 0,55$ DCV




shadowed: $U = 0,47$ DCV
(scattered radiation)



darkened: $U = 0,11$ V
(Infrared radiation)

OBSERVATION	CURRENT	IRRADIANCE
Sunshine	1040 μ A	1000 W/m^2
Sun, a bit diffuse	820 μ A	820 W/m^2
Sun before dawn	600 μ A	600 W/m^2
shadow, diffusely illuminated	530 μ A	530 W/m^2
clouded	200-300 μ A	240 W/m^2
room, bright	130 μ A	125 W/m^2
very dull	120 μ A	115 W/m^2
room close to the window, shadow	60 μ A	60 W/m^2
room dark	13 μ A	13 W/m^2

Solar Cell $d = 1$ cm

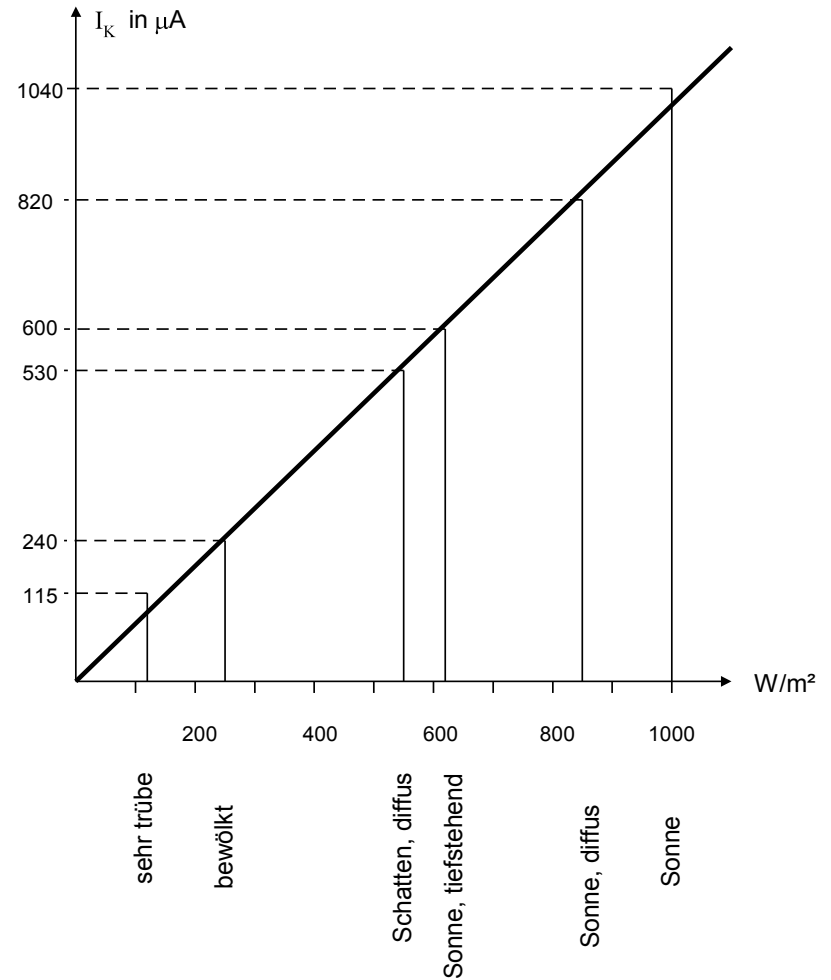

Intensity Short Circuit Current	I in μA	Irradiance in W/m^2	$\mu\text{A}/\text{W}\cdot\text{m}^{-2}$
Sun	1040	1000	1,04
Sun, diffuse	850	820	1,04
Sun, before dawn	620	600	1,03
Shadow, bright	550	530	1,04
clouded	250	240	1,04
Room, bright	130	125	1,04
Outdoor, very dull	120	115	1,04
Indoor close to a window	60	60	1,00
Indoor, dark	13	13	1,00



Thermosäule nach Moll

Thermo-Column

Empfindlichkeit (Sensitivity) 0,16 mV/mW

Wellenlängenbereich (wavelength) 150 nm – 15000 nm


Innenwiderstand (Internal Resistance) 10 Ohm

Einstelldauer (duration for measurement) 2-3 s

Eintrittsfläche (sensitive area) diameter 34 mm





Thermo-Column
thermo-couples
In series

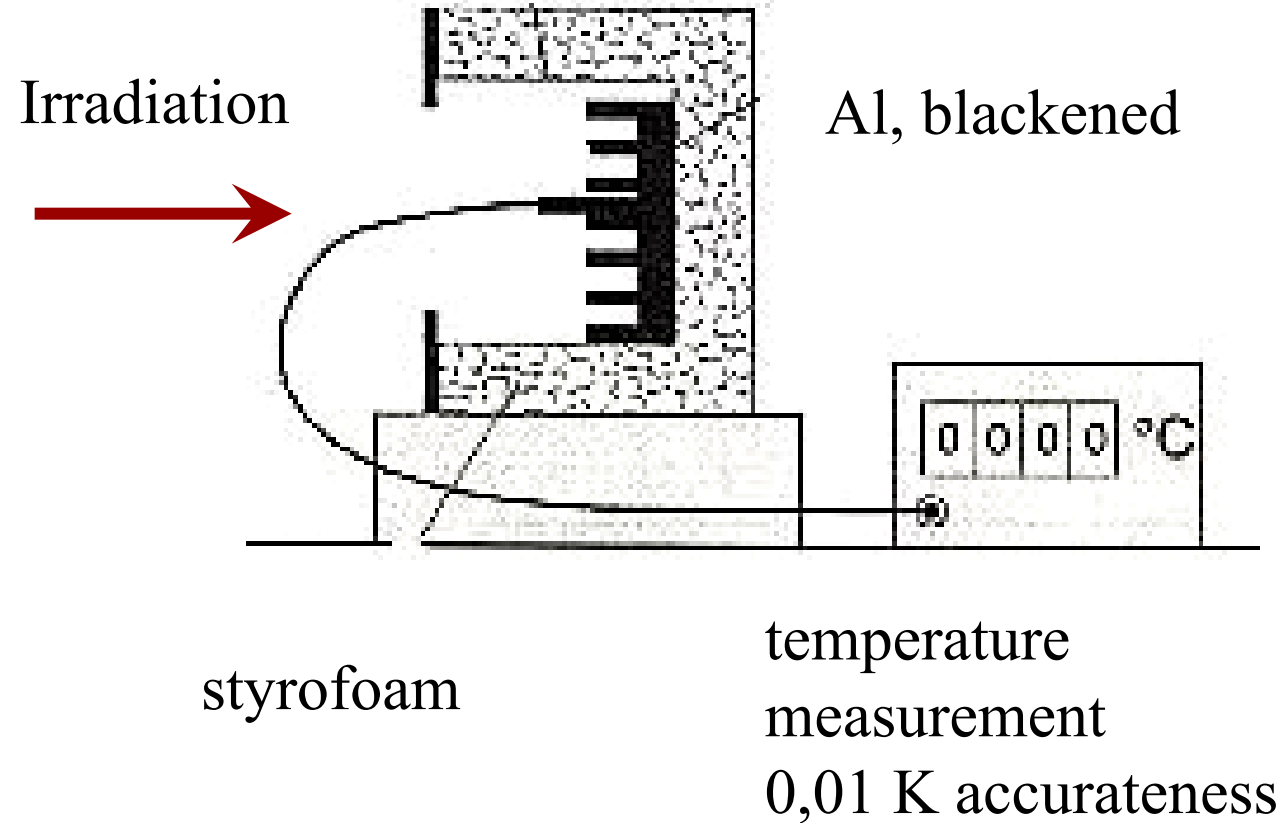

$$dQ \text{ (J)} = \varepsilon \cdot c \cdot m \cdot d\delta$$

ε ...absorption coefficient $\sim 0,95$
 c ...specific warmth, Al-
0,89 kJ/kg.K
 m ...mass-kg
 $d\delta$..temperature difference – K
Measurements duration up to thermal balance

Characteristic Lines of a Solar Cell

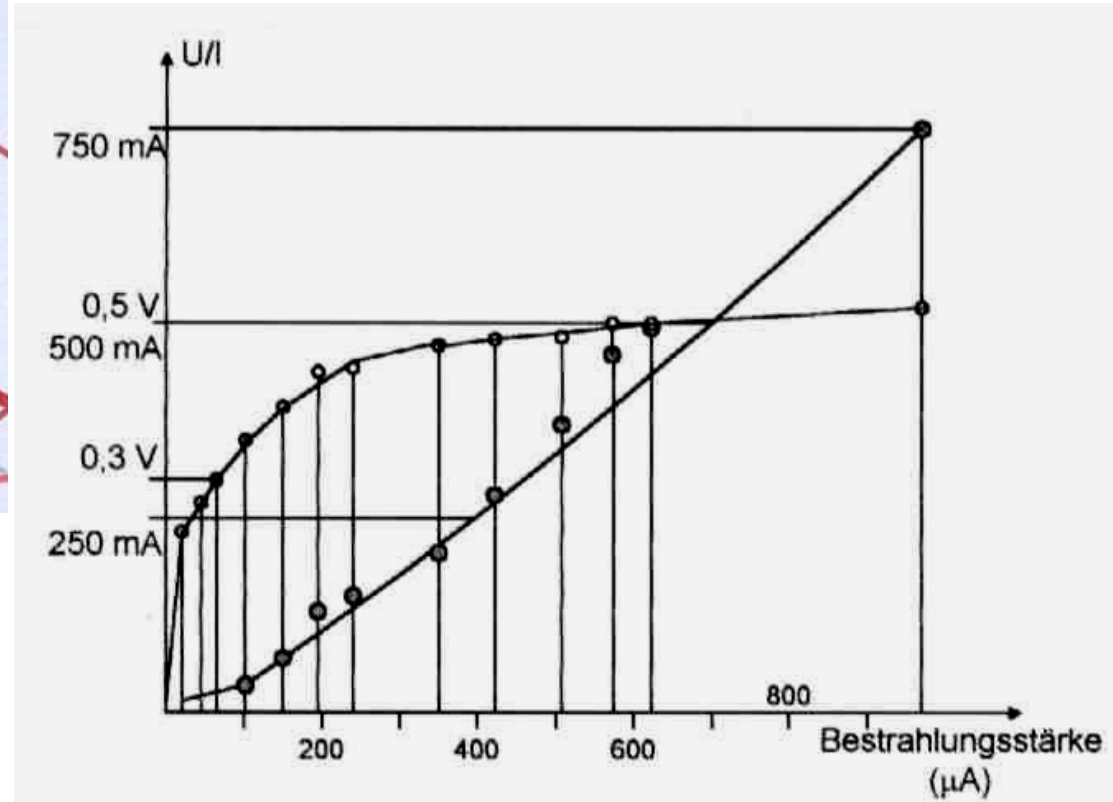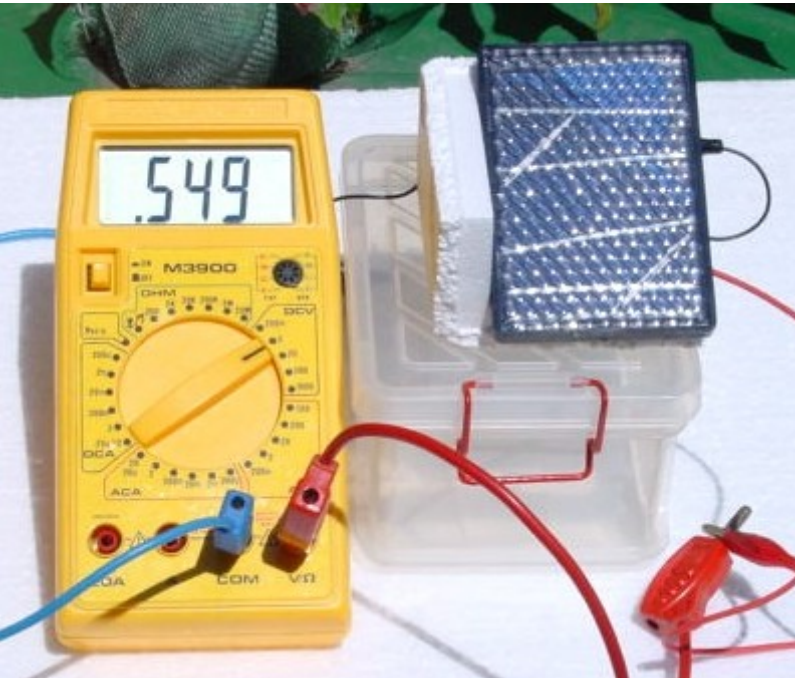

$$U_0 = \frac{kT}{e} \cdot \ln \left(\frac{q \cdot D_E t}{n_0 \cdot L_E^2 + p_0 \cdot L_L^2} + 1 \right)$$


- mit:
- q..Zahl der je Sekunde pro Flächeneinheit der p-n-Schicht gebildeten Elektron-Loch-Paare
 - L...Diffusionslänge
 - D...Diffusionskonstante
 - n_0, p_0 : Gleichgewichtskonzentration der Elektronen bzw. Elektronenlöcher
 - t...Lebensdauer der Elektron-Loch-Paare

Sonderfall:

$$D_E = D_L, L_E = L_L, n_0 = p_0:$$

$$U_0 = \frac{kT}{e} \cdot \ln \left(\frac{j}{j_0} + 1 \right), \quad \text{mit } j = q \cdot e$$


Photovoltage – Exposed Area

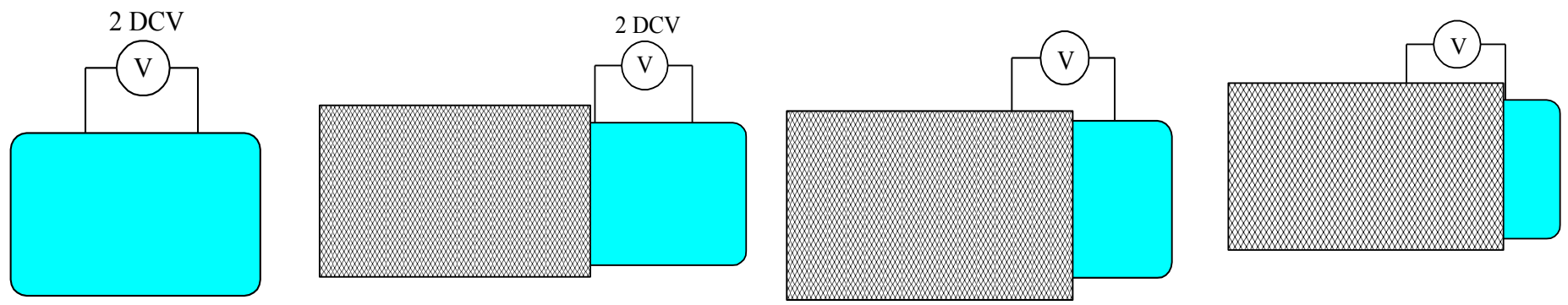

The Solar Cell is directly connected to the voltmeter. (2 DCV)


Cover parts of the surface area and observe the voltage in any case !

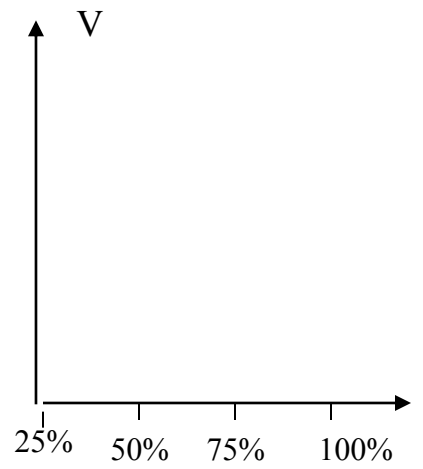Not covered..... $U = \dots\dots V$
 $\frac{1}{4}$ of the surface covered... $U = \dots\dots V$
 $\frac{1}{2}$ of the surface covered... $U = \dots\dots V$
 $\frac{3}{4}$ of the surface covered.... $U = \dots\dots V$



Conclusion:

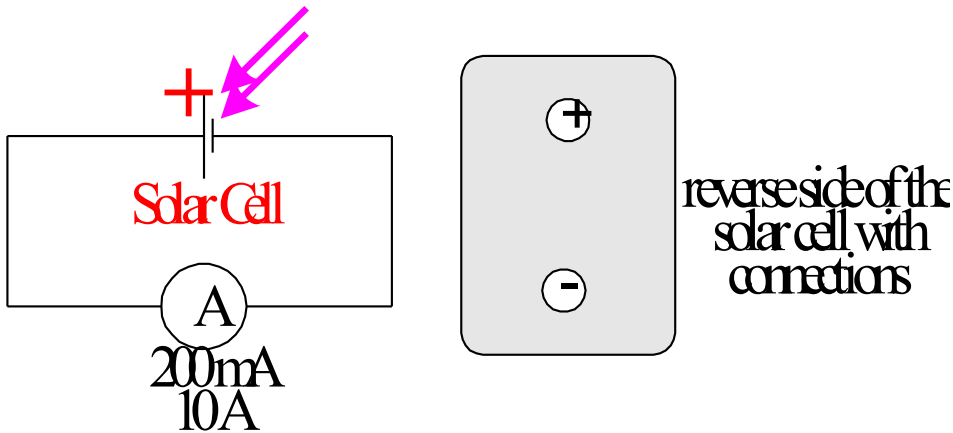The Solar Cell is directly connected to the ammeter.



The intensity of the short circuit current is direct proportional to the irradiance.


The short circuit current is measured at different irradiances.

You may draw a diagram now.

	I in mA
dim room	
bright room	
shadow	
sun	


By this you can measure the illumination.

Short-Circuit-Current of Solar Cells

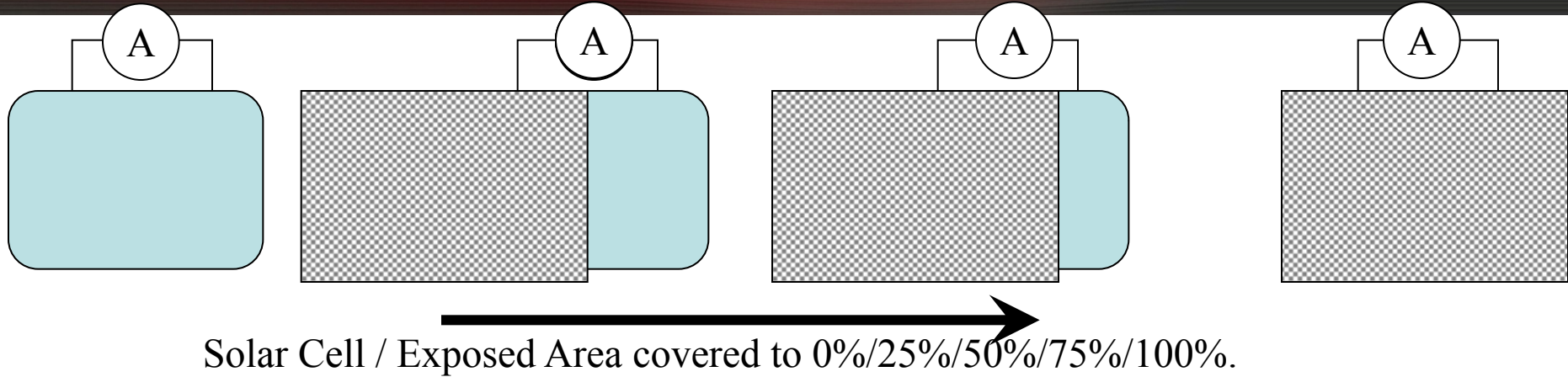

The Solar Cell is directly connected to the ammeter.

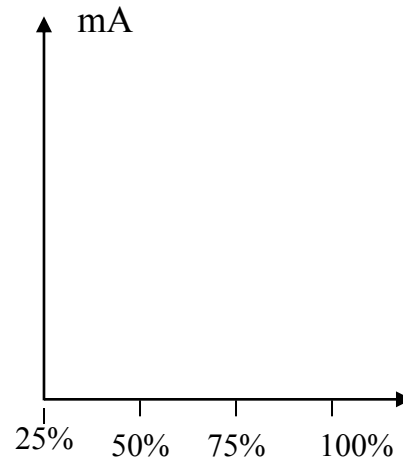Cover parts of the surface area and observe the intensity of current in any case !



Despite the surface is totally covered current is to be measured. This demonstrates the influence of IR.

The Solar Cell is directly connected to an ammeter.




The Solar Cell is directly connected to a voltmeter.

Different Surfaces

about the same voltage – only dependent on the irradiance

Short current's intensity depending on the irradiance and proportional to the surface.

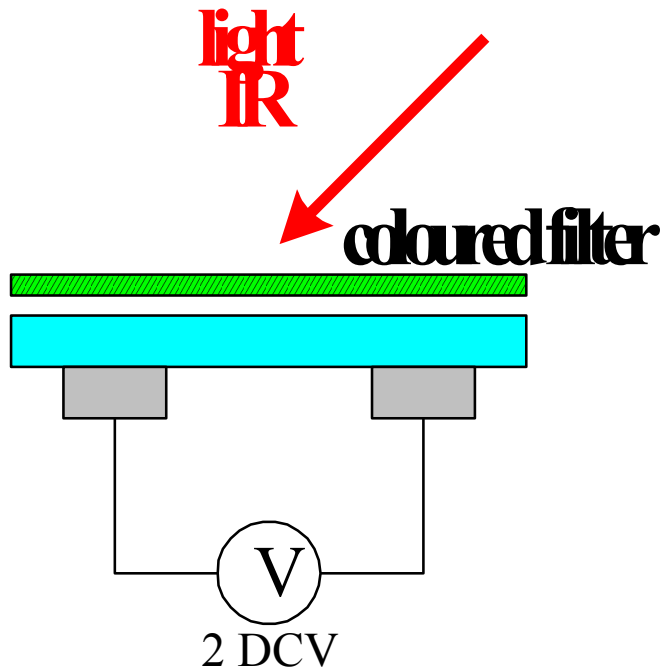
To which colour the solar cell is most sensitive?
 Colour means part of the spectral range - visible and infrared



Sun	U = V
Sun + red coloured filter	U = V
Sun + green coloured filter	U = V
Sun + blue coloured filter	U = V
Infrared	U = V



Highest sensitiveness to red indicates Silicon.

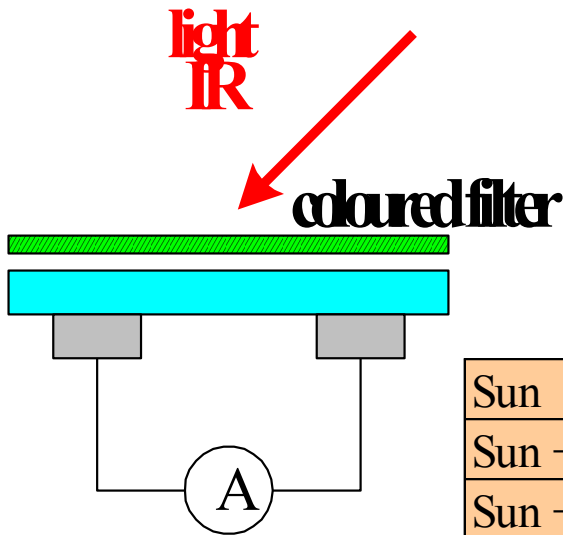To which colour the solar cell is most sensitive?
 Colour means part of the spectral range - visible and infrared



Sun	I = mA
Sun + red coloured filter	I = mA
Sun + green coloured filter	I = mA
Sun + blue coloured filter	I = mA
Infrared	I = mA

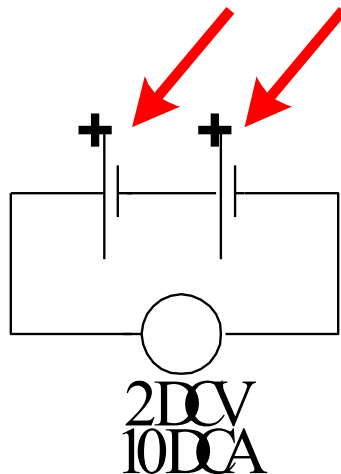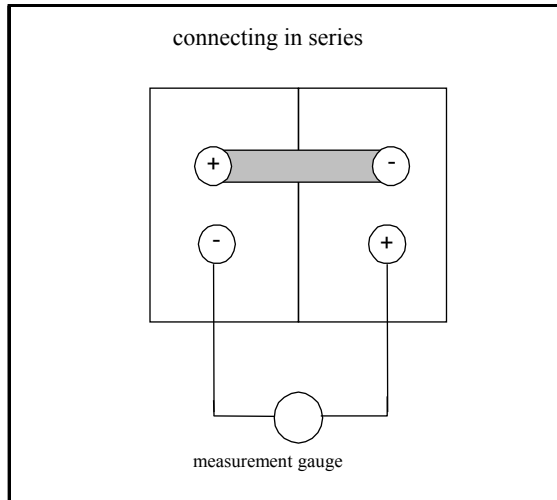**The Solar Cell shows the highest efficiency in the red part of the spectral range.
 This is an indicator for Silicon.**



Measure the open circuit voltage of any of the two solar cells:

$$U_1 = \dots\dots\dots \text{V}$$

$$U_2 = \dots\dots\dots \text{V}$$

Measure the short current intensity of any of the two solar cells:

$$I_1 = \dots\dots\dots \text{mA}$$

$$I_2 = \dots\dots\dots \text{mA}$$





Connect the solar cells into series. Measure now the open circuit voltage as well as the short current intensity of both solar cells:

$$U_1 + U_2 = \dots\dots\dots \text{V}$$

$$I_1 + I_2 = \dots\dots\dots \text{mA}$$


Voltages are added, intensities remain the same.

Connecting Solar Cells into Series

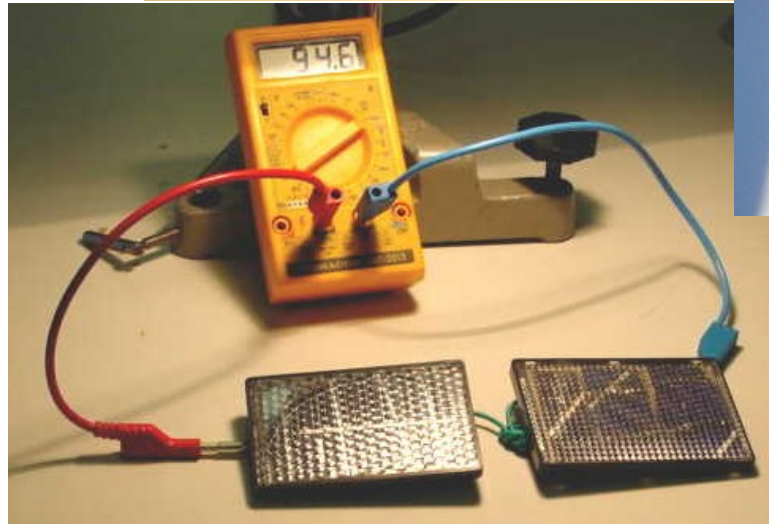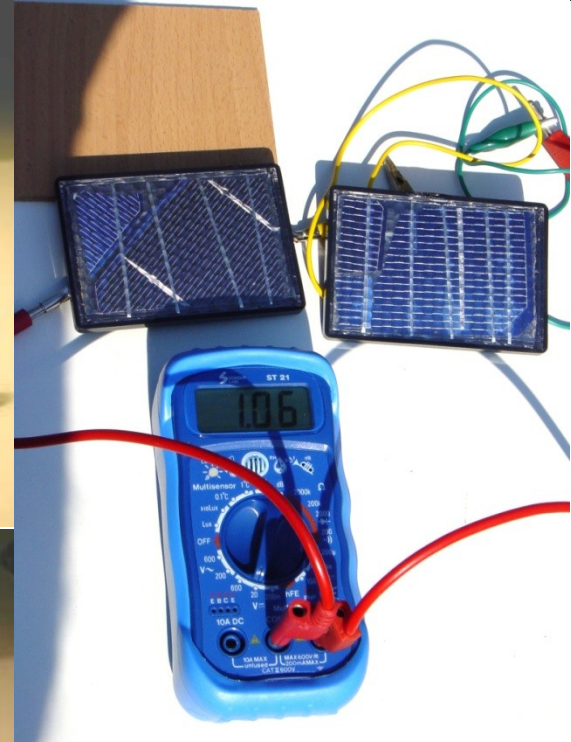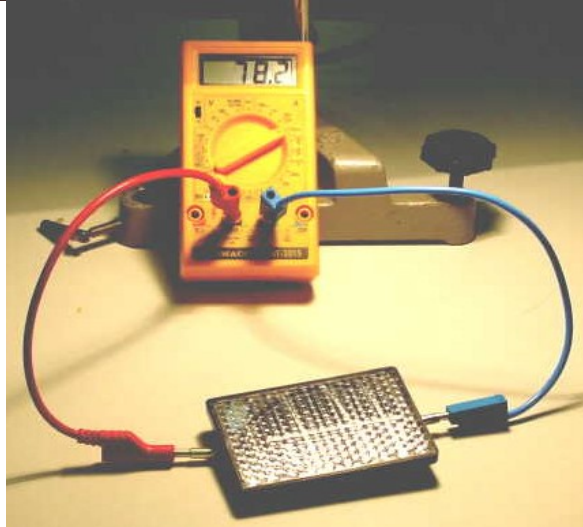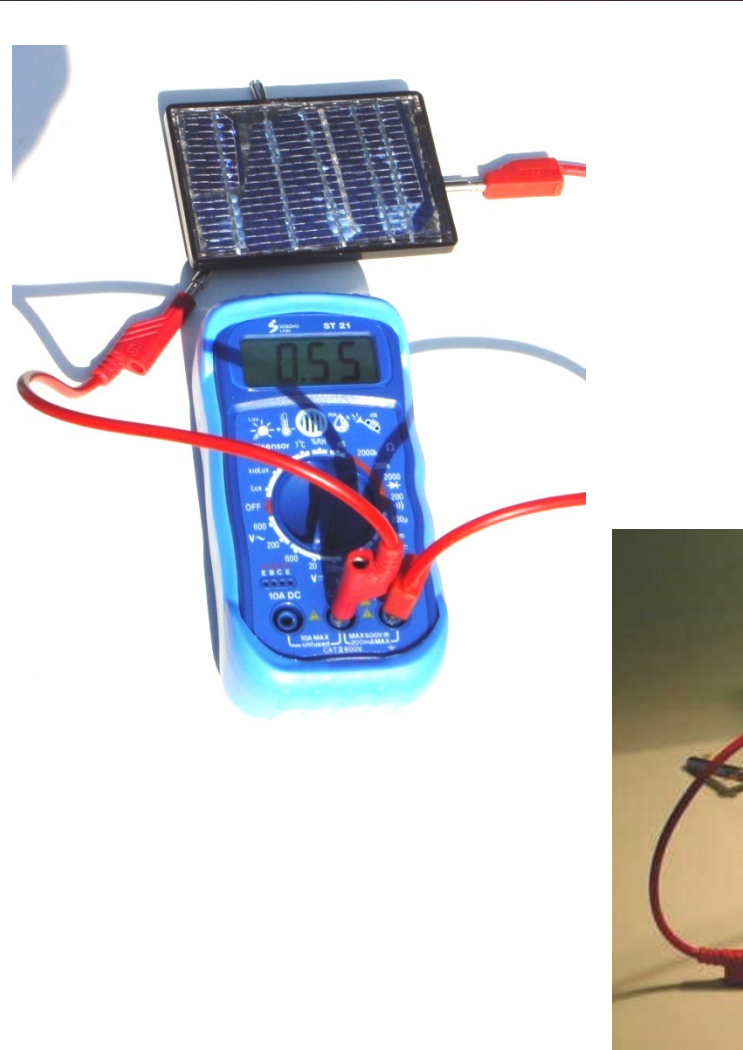

Connecting Solar Cells into Series

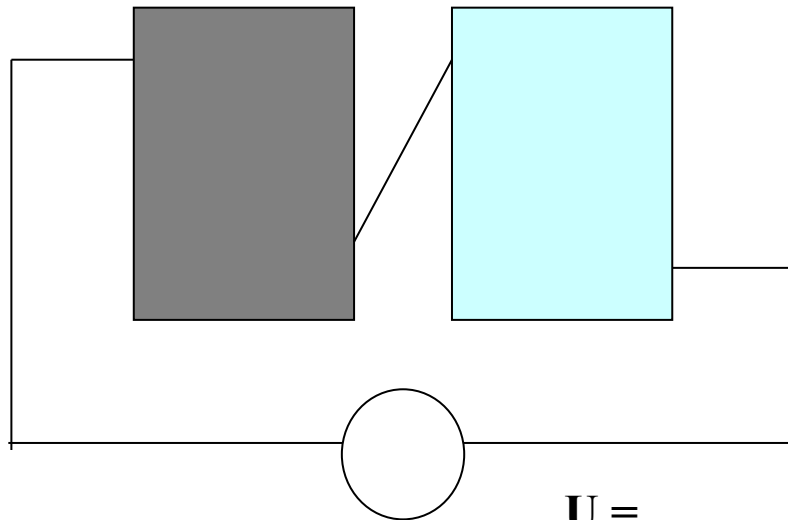
Cover one solar cell. This one cannot produce photovoltage.



mA / V



$U = \dots\dots\dots V$

$I = \dots\dots\dots mA$

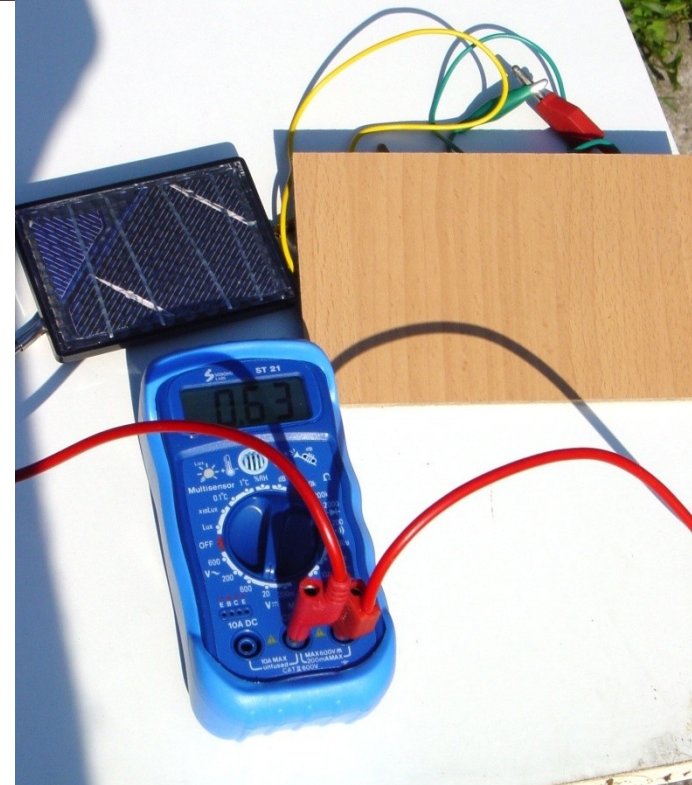

The internal resistance of the clouded solar cell is rather high, so the current's intensity goes to zero. The clouded solar cell blocks the current and therefore has to be bridged by an open-circuit-diode.

paralleled solar cells

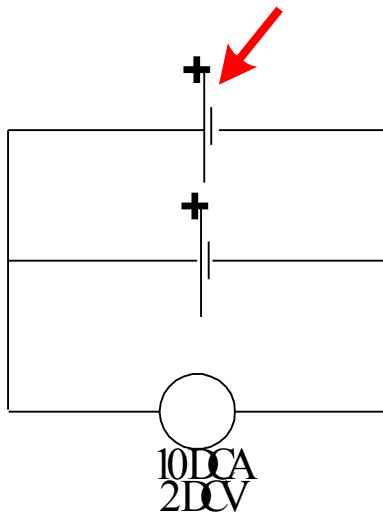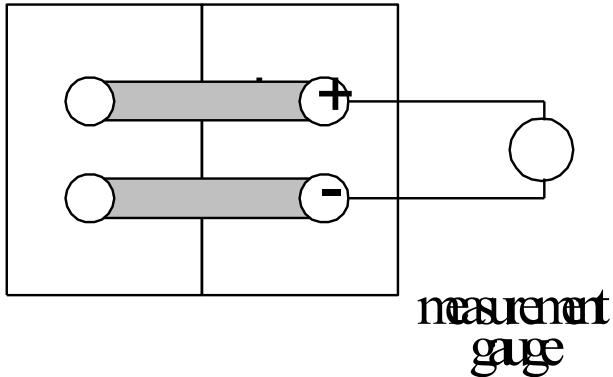

Measure the open circuit voltage of any of the two solar cells:

$$U_1 = \dots\dots\dots \text{ V}$$

$$U_2 = \dots\dots\dots \text{ V}$$

Measure the short current intensity of any of the two solar cells:

$$I_1 = \dots\dots\dots \text{ mA}$$

$$I_2 = \dots\dots\dots \text{ mA}$$

Connect the solar cells into parallel.





Measure now the open circuit voltage as well as the short current intensity of both solar cells:

$$U_1 + U_2 = \dots\dots\dots \text{ V}$$

$$I_1 + I_2 = \dots\dots\dots \text{ mA}$$



Intensities are added, voltages remain the same.

Connecting Solar Cells into Parallel

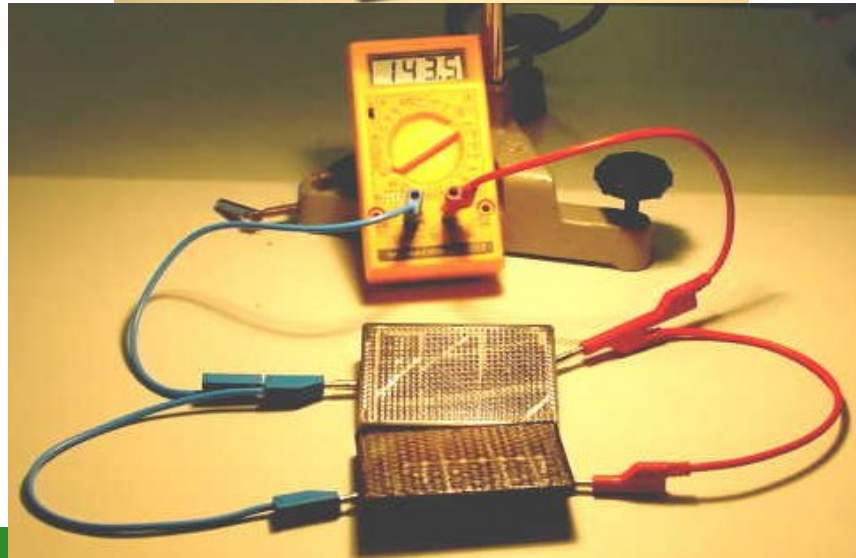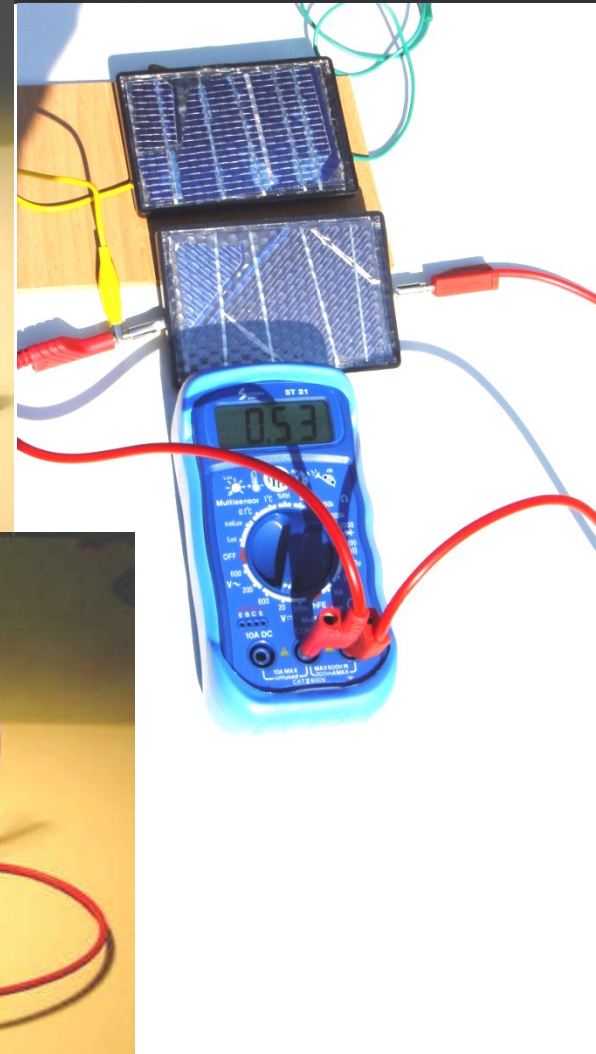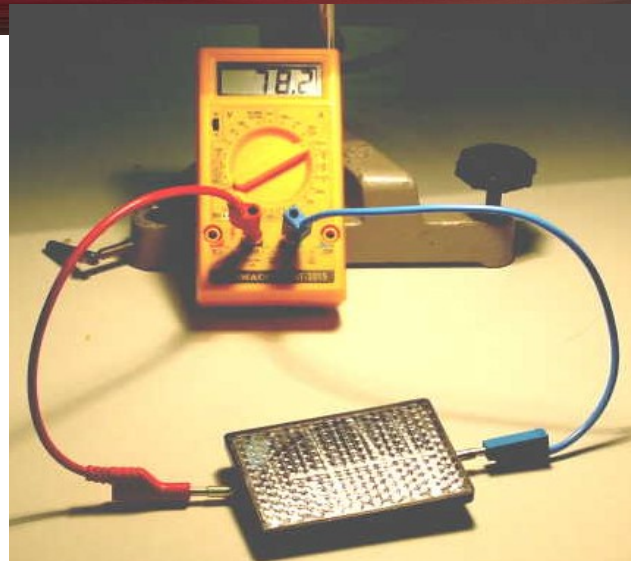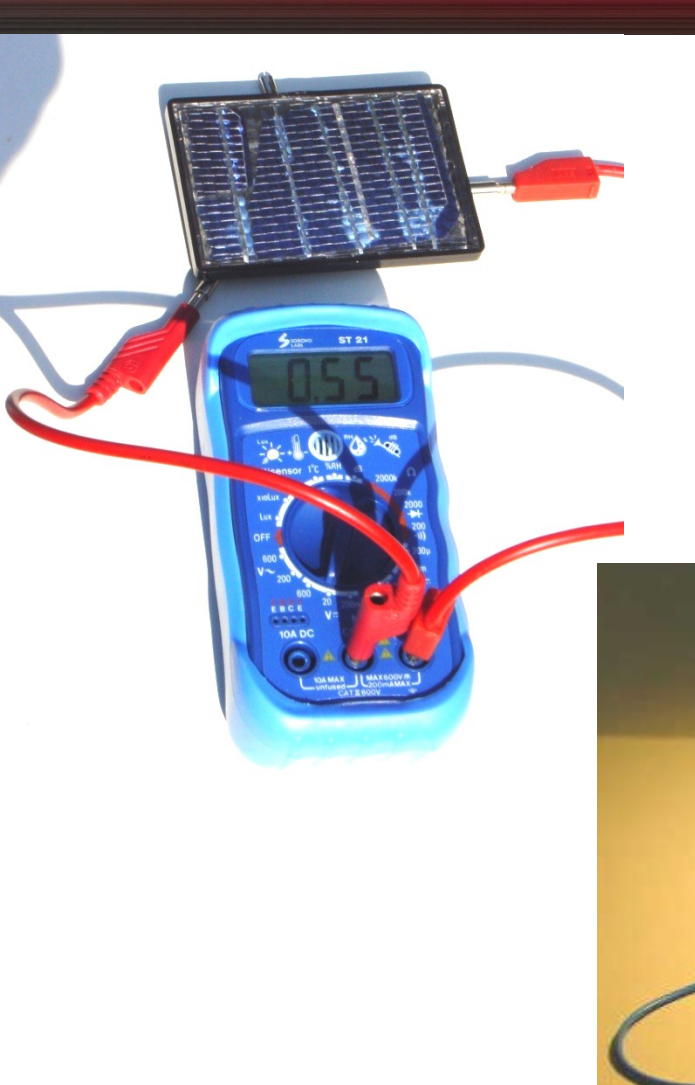

Connecting Solar Cells into Parallel

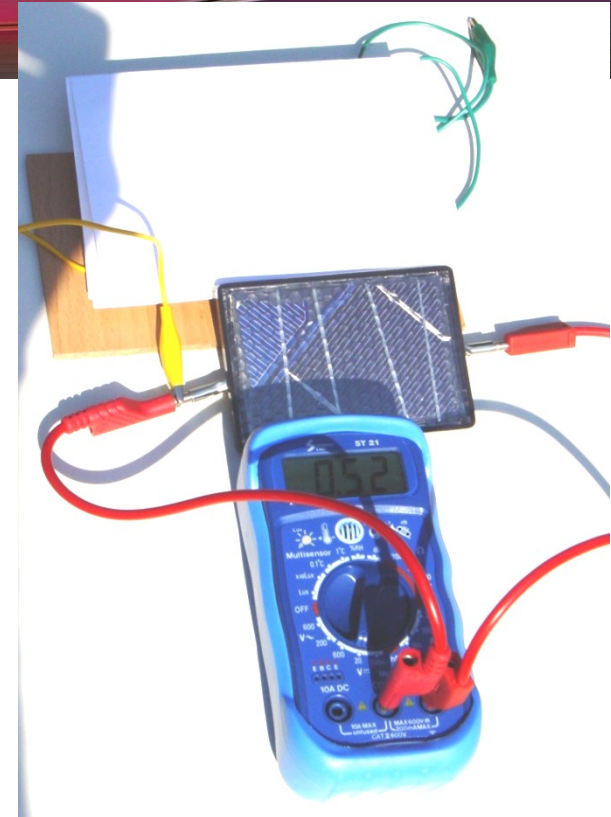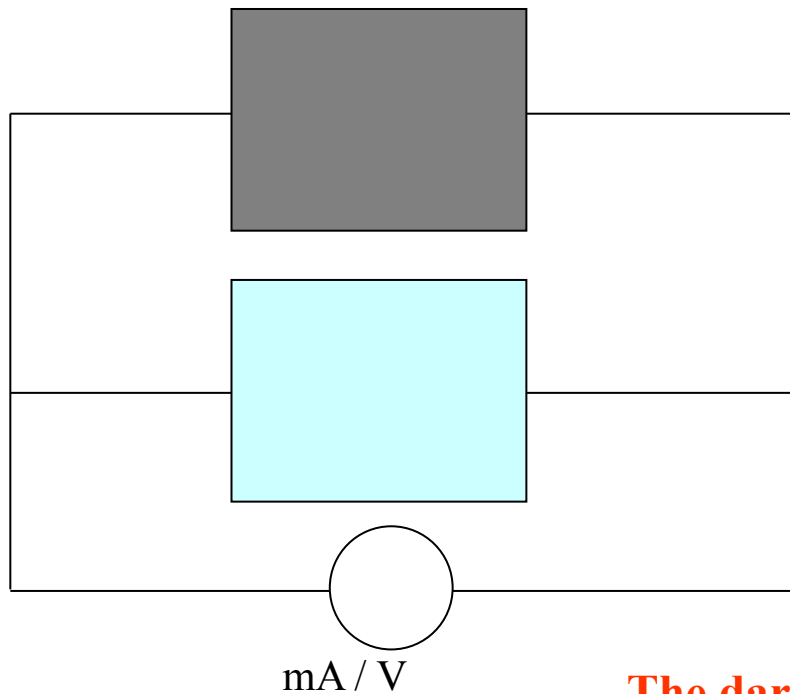Cover one solar cell. This one cannot produce photovoltage.





U = V

I = mA

The darkened solar cell is out of order, this diminishes the current. It has the effect of reducing the exposed surface area.

Running an Engine

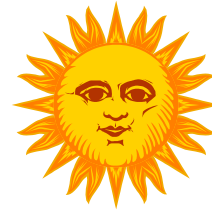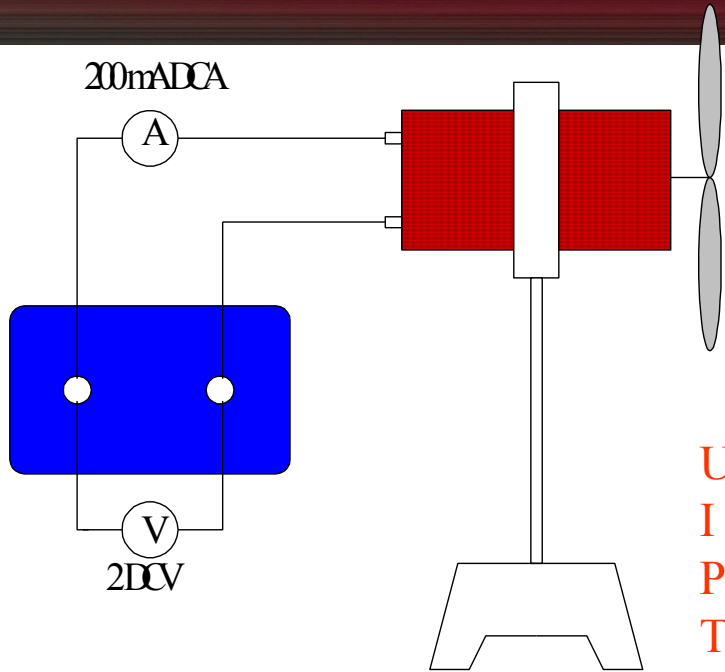

$U = \dots\dots\dots V$
 $I = \dots\dots\dots mA$
 $P = \dots\dots\dots mW$
 The engine runs...
 ...fast
 ...slow
 ...not





$U = \dots\dots\dots V$
 $I = \dots\dots\dots mA$
 $P = \dots\dots\dots mW$
 The engine runs...
 ...fast
 ...slow
 ...not




$U = \dots\dots\dots V$
 $I = \dots\dots\dots mA$
 $P = \dots\dots\dots mW$
 The engine runs...
 ...fast
 ...slow
 ...not

Run the engine at different illumination - sunlight, shadow, indoor.

For shadowing you may use a grid.

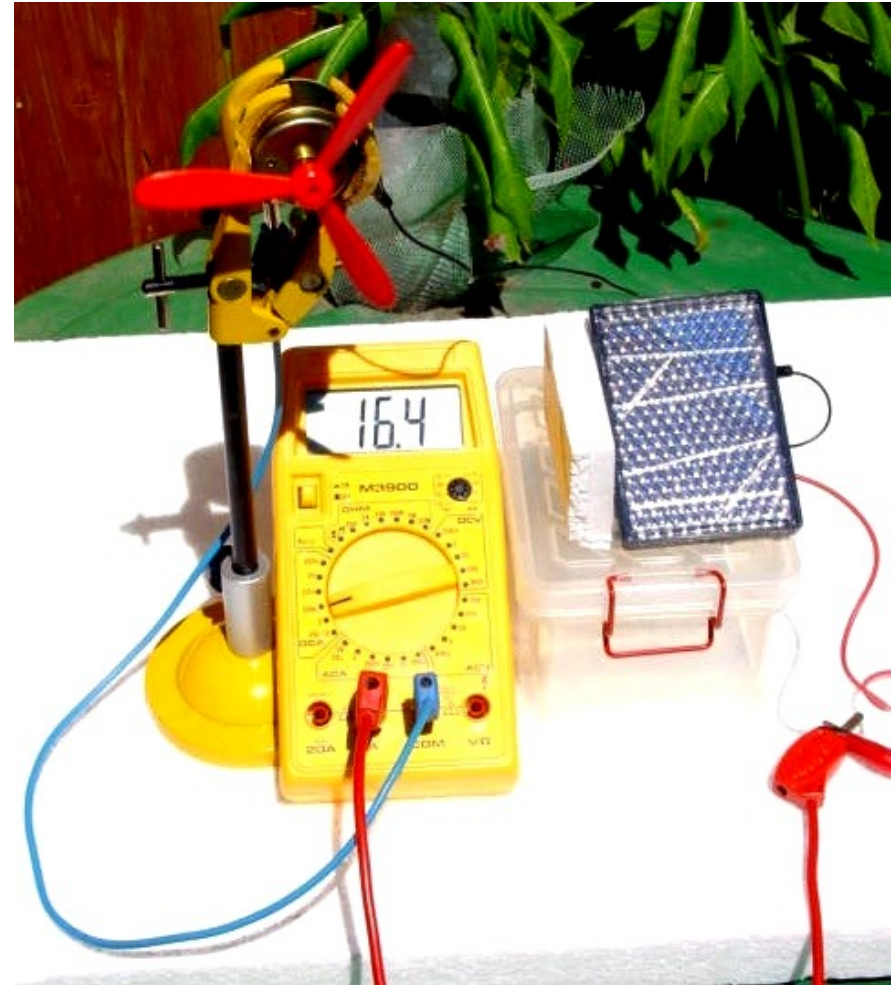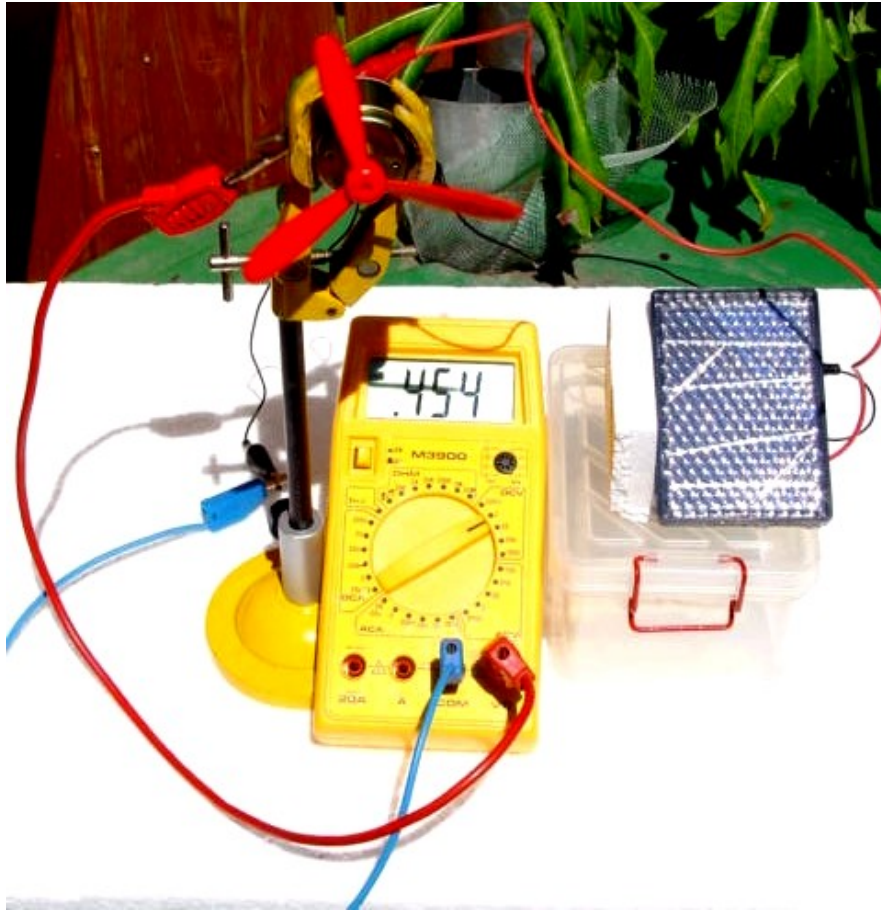

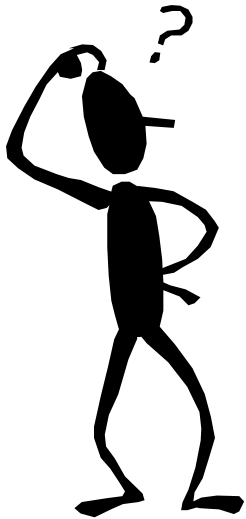

$$\eta = F \cdot A \cdot Q$$




fill factor...share of energy being transferred from the solar cell to the appliance.



absorption ability, depends on material and frequency of radiation



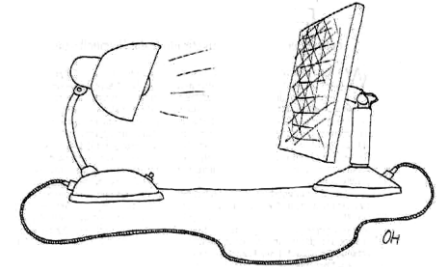yield of quanta energy, abundance, to which photons solve electrons.



For Si it is: $\eta = 0,8 \cdot 0,7 \cdot 0,21 = 0,12$ (12%)

matter		efficiency theor.	efficiency pract.
Si	monocryst.	15%	11-16%
	polycryst.	10-15%	9-12%
	amorphous	20%	11% (4-7%)
GaAs, CdTe, GeS, CdS, ZnSe		up to 20%	up to 16%
	technics		16%
	high-efficiency cells		24%
	Tandem-, sandwich		up to 32%

Calculating the Efficiency / Engine's Experiment

↳ Measurement of the irradiance by means of a calibrated solar cell:

↳ $x \text{ W/m}^2$

↳ Dimensions of the solar cell (battery) used:

↳ $l = \dots \text{ cm}$, $b = \dots \text{ cm}$

↳ $A = \dots \text{ m}^2$

↳ Irradiance P :

$$P = x \cdot A = \dots \text{ W}$$

$$\eta = \frac{W}{V}$$

↳ Measurement of the engine's power:

↳ $U = \dots \text{ V}$


↳ $I = \dots \text{ mA} = \dots \text{ A}$

$$P = U \cdot I = \dots \text{ W}_1$$


Open the table on your disc and calculate !

Solar Cell	Fill in	Result	Comment
Irradiance in W/m ²		0	
Length of the solar cell in cm			
Width of the solar cell in cm		0	A in m ²
Power irradiated to the solar cell		0	P in W
Engine			
Intensity of Current in mA		0	I in A
Voltage in V		0	U in V
Power of the engine in Watt		0	P ₁ in W
Efficiency		k.A	

The Characteristic Line

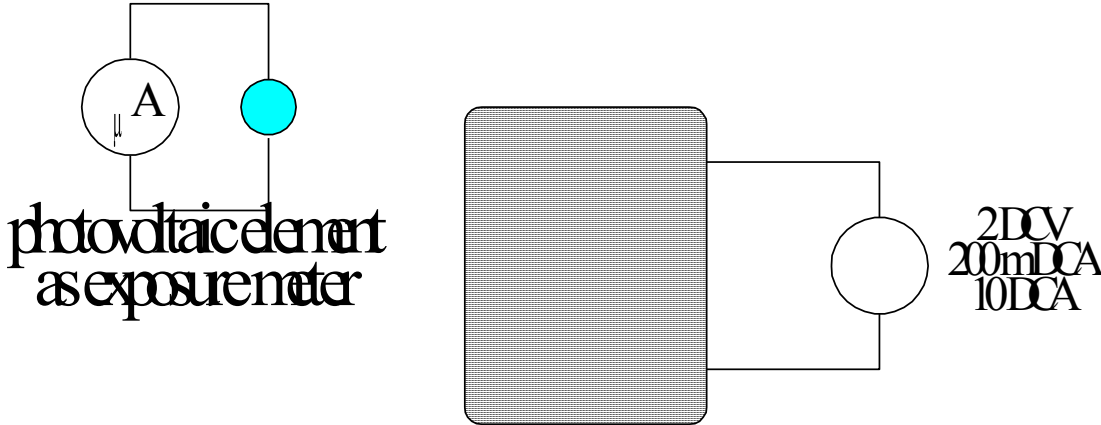

Linear increasing intensity of current

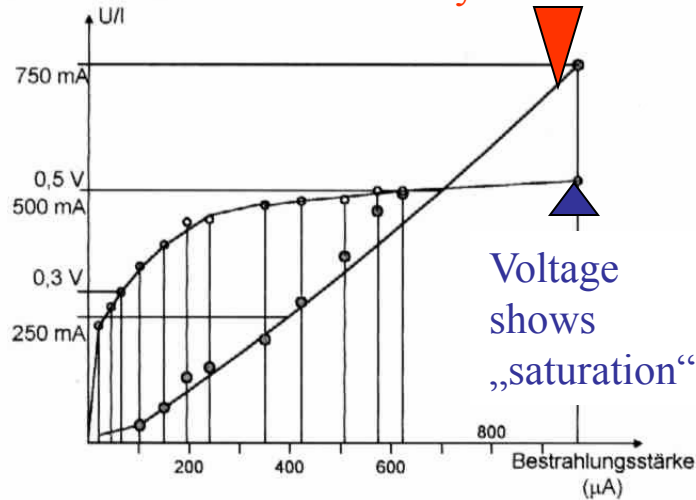

Calculate the resistance when being dark:

$$I_K = 2,6 \mu\text{A}$$

$$U = 0,055 \text{ V} / I = 0,17 \text{ mA}$$

$$R = 204 \text{ Ohm}$$

...when being bright:

$$I_K = 610 \mu\text{A}$$

$$U = 0,502 \text{ V} / I = 496 \text{ mA}$$

$$R = 1 \text{ Ohm}$$


Measured values...

Beleuchtungsstärke in μA	Leerlaufspannung in V	Kurzschlussstromstärke in mA
2,6	0,055	0,27
7	0,08	0,5
20	0,23	6,8
23	0,24	7,6
29	0,257	8,6
35	0,26	10
45	0,277	12,15
64	0,31	17,3
102	0,346	36
150	0,39	64
194	0,444	128
240	0,48	145
350	0,472	193
422	0,476	280
508	0,491	370
572	0,506	460
621	0,502	496
970	0,528	750


The I-U-characteristic of a Solar Cell

$A = 10 \text{ cm} \times 10 \text{ cm}$

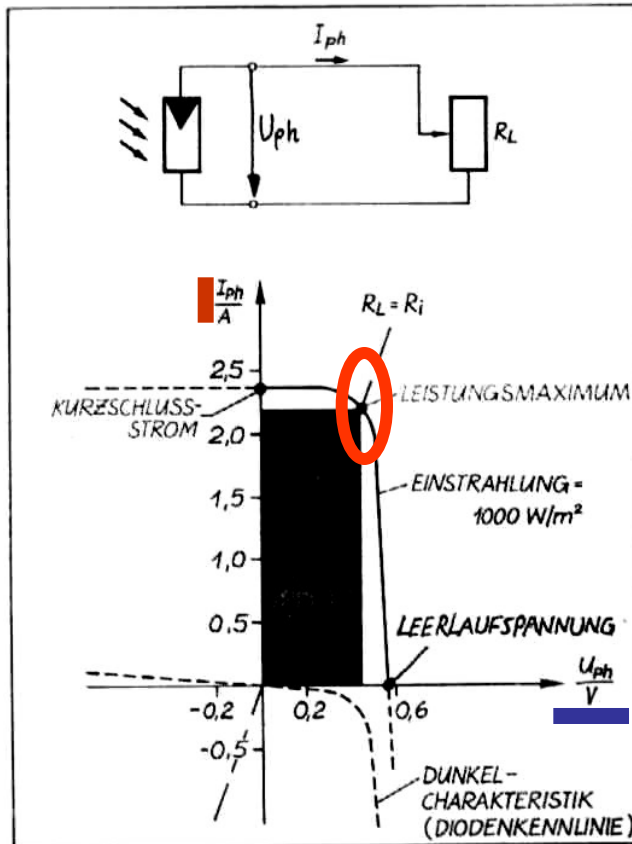irradiance 1000 W/m^2 , $\delta = 25 \text{ }^\circ\text{C}$




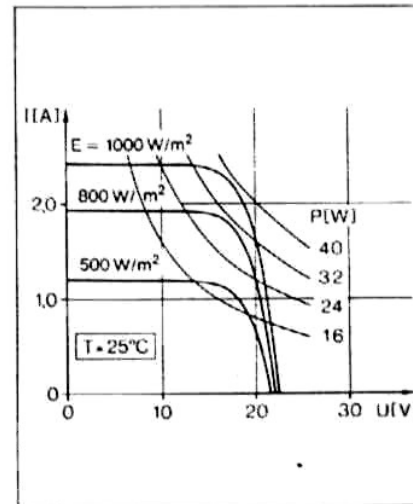
Strom-Spannungs-Kennlinie einer $10 \text{ cm} \times 10 \text{ cm}$ -Solarzelle bei einer Einstrahlungsstärke von 1000 W/m^2 , $\delta = 25 \text{ }^\circ\text{C}$



Typische Kennlinien eines Photovoltaikmoduls (AEG)

I...Short Current
U...Open-Circuit-Voltage
Indicated...Power Maximum

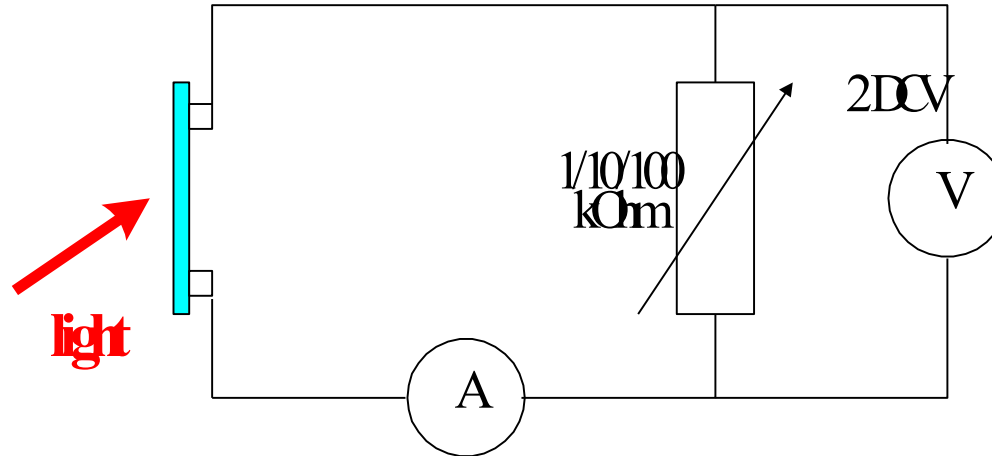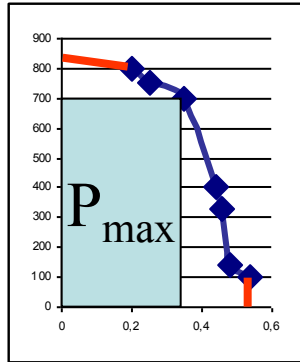Max. power, if external resistance equals the internal resistance of the solar cell.




Problem was:
adaption of the values
of the external resistor

Voltage in V	Current in mA	Power in mW
0	860	0
0,54	100	54
0,48	140	67,2
0,46	330	151,8
0,44	400	176
0,35	700	245
0,25	750	187,5
0,2	800	160
0,55	0	0

Max. power at $U = 0,35$ V and $I = 700$ mA
 $P_{max} = 245$ mW

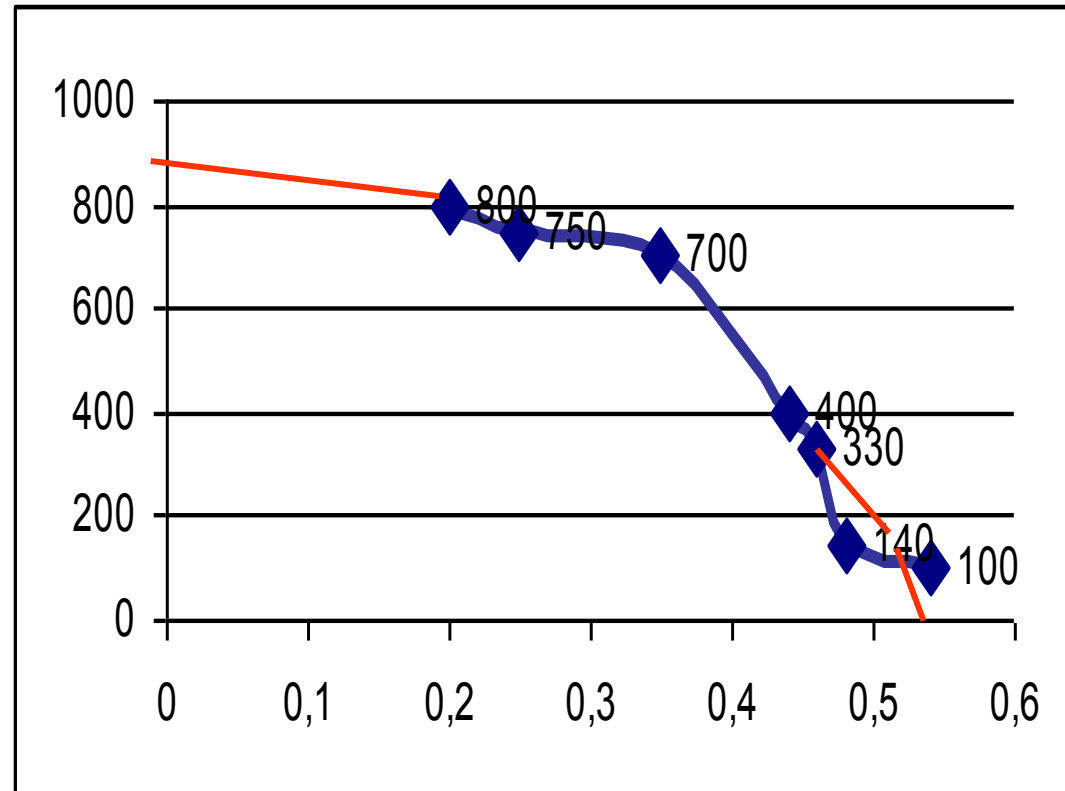Problem was:
adaption of the values
of the external resistor

Caused by this:
problematic
characteristic power
line



Expose the solar cell to an IR-radiator as it is a bulb with power $P = 120 \text{ W}$ or the sun.

Do not overheat the solar cell, it could be destroyed.

Duration of Time in min	Voltage in V	Duration of Time in min	Voltage in V
0	0,561	8	0,493
1	0,550	9	0,488
2	0,540	10	0,482
3	0,530	11	0,477
4	0,520	12	0,468
5	0,514	13	0,464
6	0,507	14	0,460
7	0,500		


We have measured:

Result: The voltage decreases with increasing temperature.

Duration of Time in min	0	1	2	3	4
Intensity of Current in A	0,75	0,77	0,78	0,78	0,78


Result: The intensity of current increases with increasing temperature.

Reverse Blocking Diode

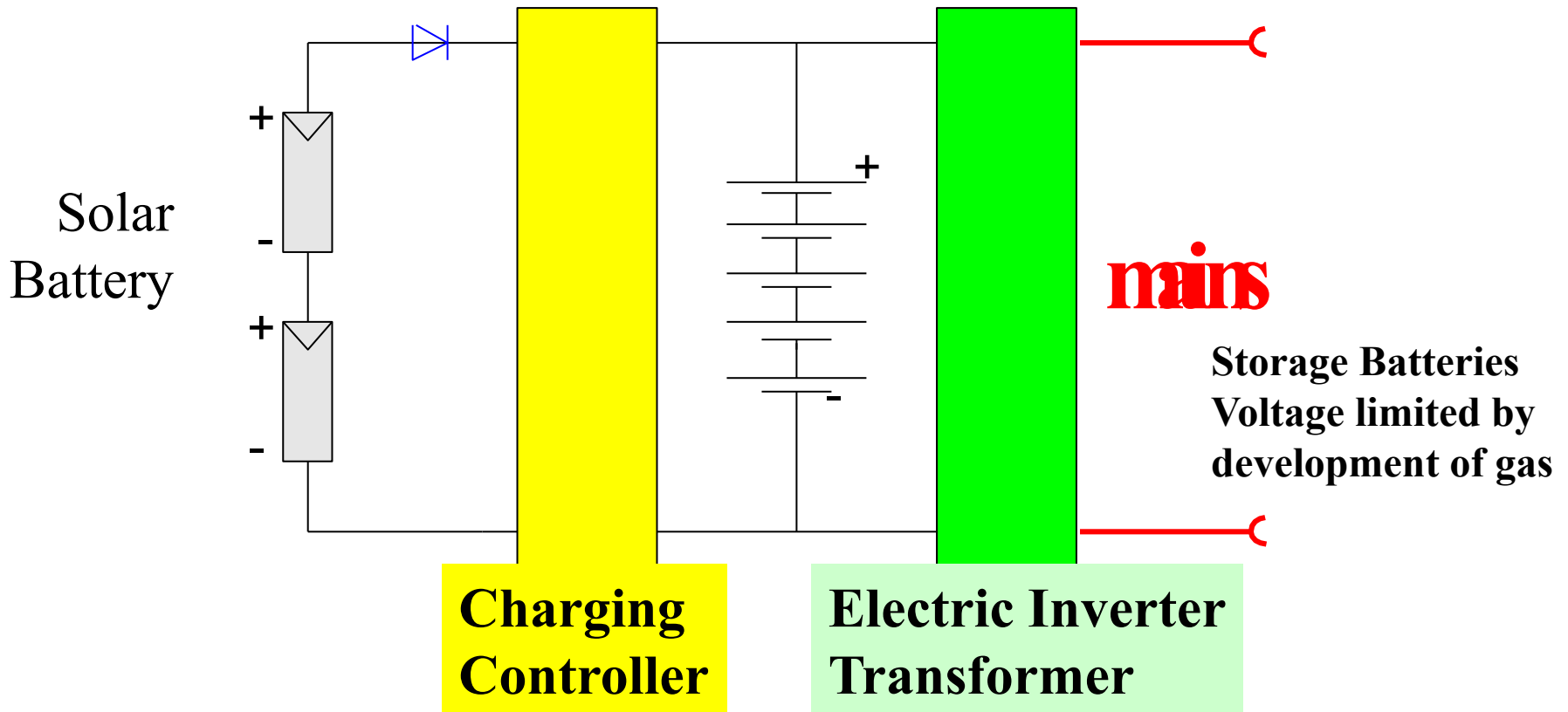

Charging of a Capacitor - Discharging

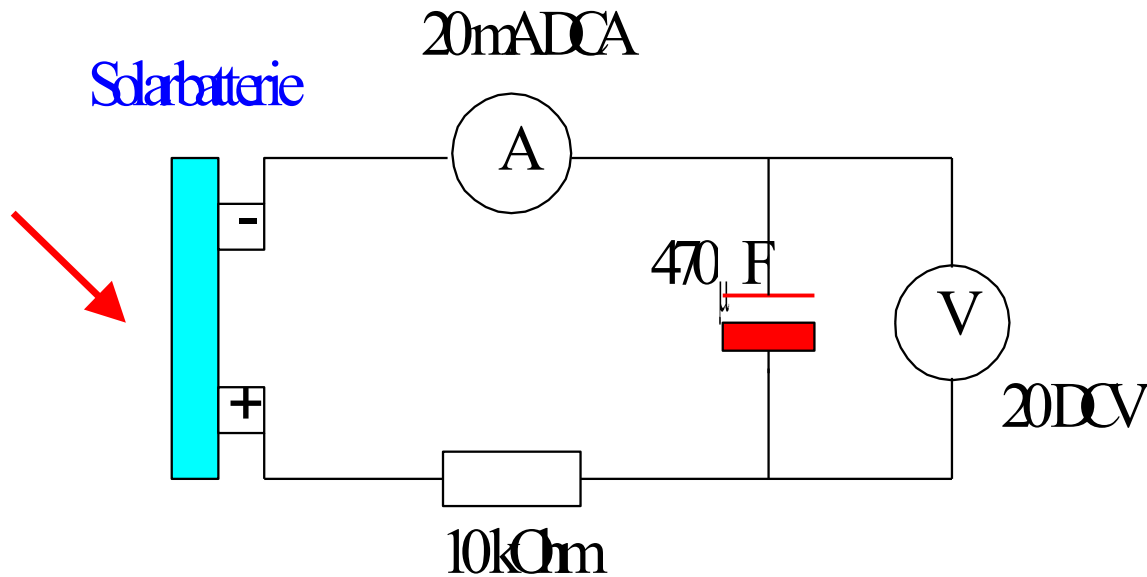Use a solar battery (voltage about 4 DCV) !!



Expose the solar battery to the sun. The capacitor rapidly is charged up to 4 DCV.


$I = \dots\dots\dots$ mA,
 $U = \dots\dots\dots$ DCV

Cover the solar battery, so it's surface is dark. The capacitor discharges cross the solar cell.

$I = \dots\dots\dots$ mA,
 $U = \dots\dots\dots$ DCV

The capacitor is able to store energy, but to avoid discharging in case the solar cell is shadowed, a reverse blocking diode is to be used.

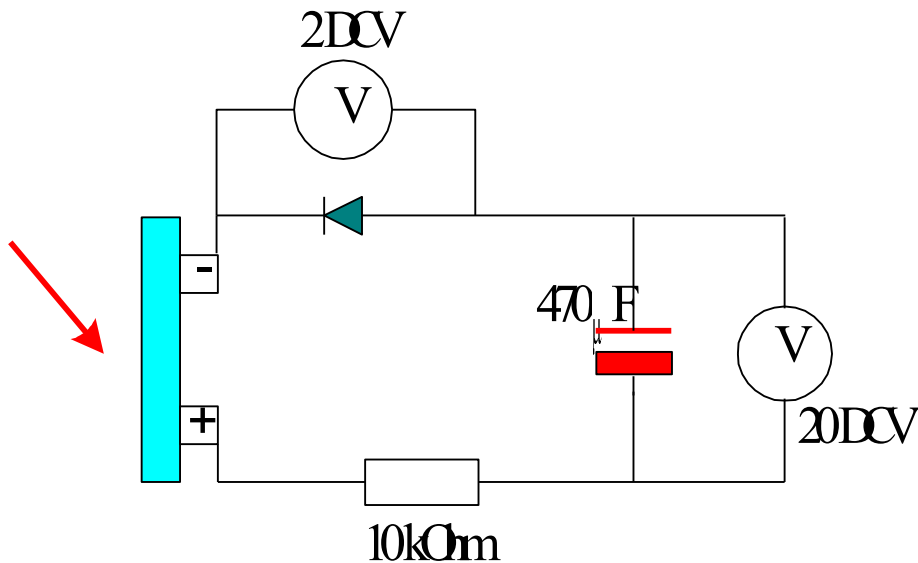Use a solar battery (voltage about 4 DCV) !!




Expose the solar battery to the sun.
The diode is forward biased, so the current can flow. The capacitor rapidly is charged up to
 $I = \dots\dots\dots$ mA, $U = \dots\dots\dots$ DCV
The diode needs about 0,5 V drop in voltage.


Cover the solar battery, so it's surface is dark.
The capacitor does not discharge across the solar cell,
because now the diode is reverse biased.
 $I = \dots\dots\dots$ mA, $U = \dots\dots\dots$ DCV

The capacitor is able to store energy, the reverse blocking diode is a hindrance for discharging.

Charging of a Capacitor - Discharging

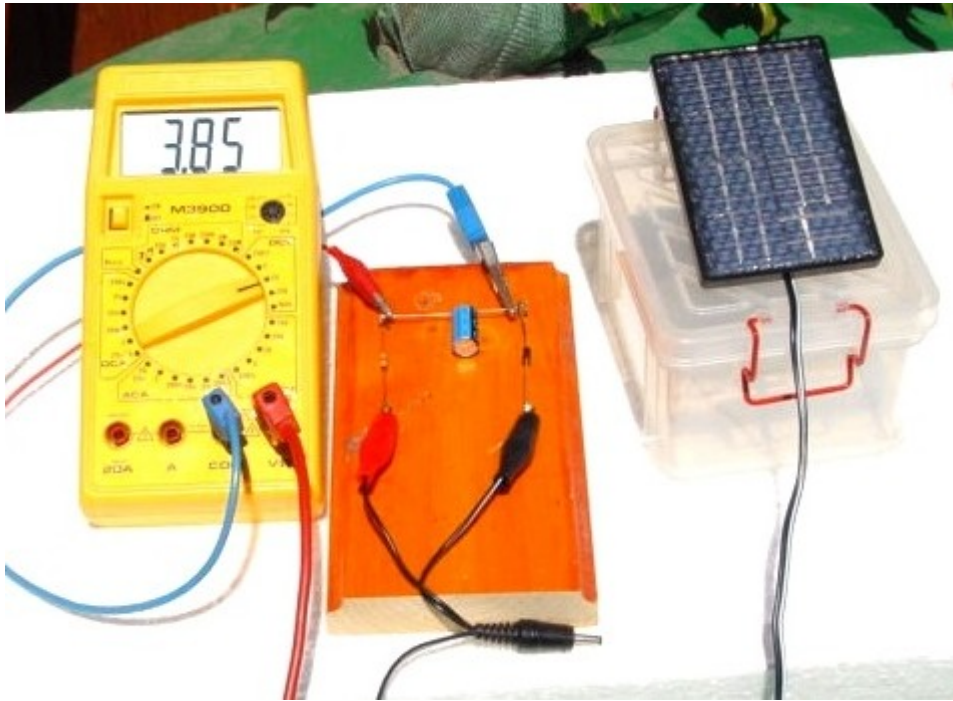


sunshine

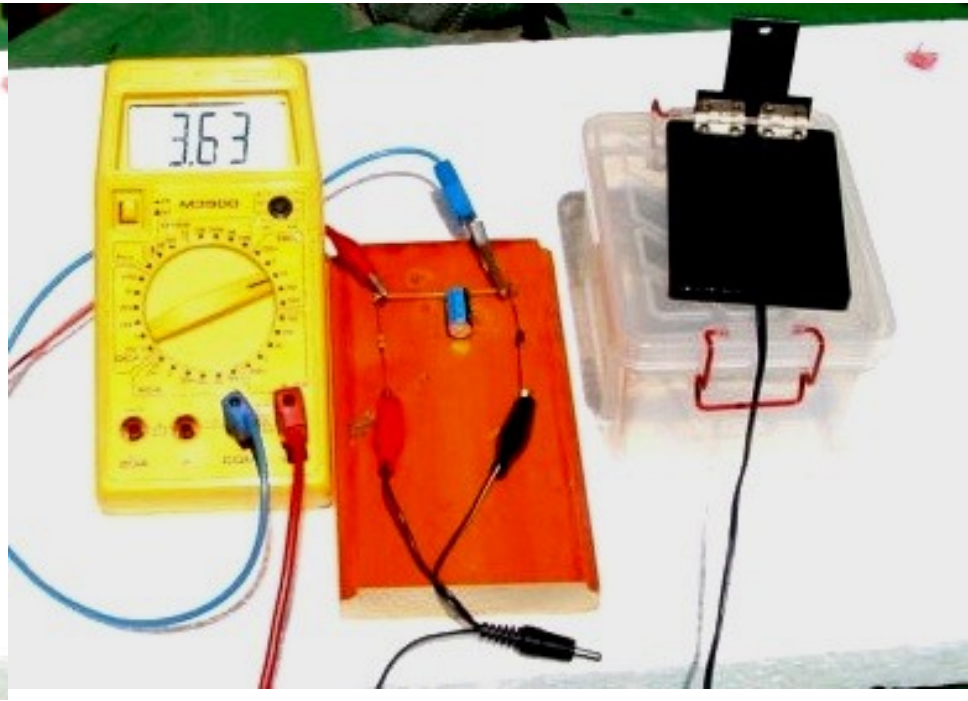


darkness

Charging a rechargeable Battery

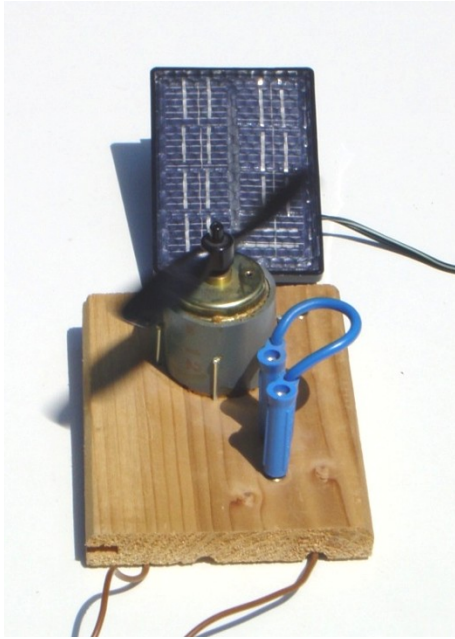

The solar motor is run by a solar cell exposed to bright sunshine.

The battery is charged by a solar cell.

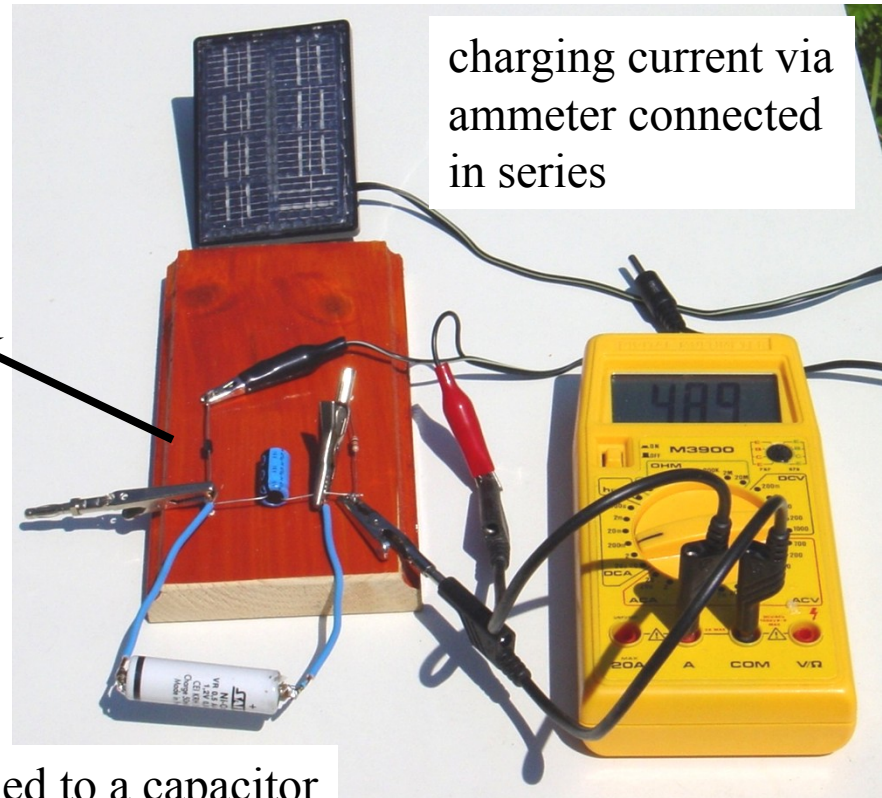



charging current via ammeter connected in series

reverse blocking diode


battery paralleled to a capacitor


solar engine
run by the
charged battery

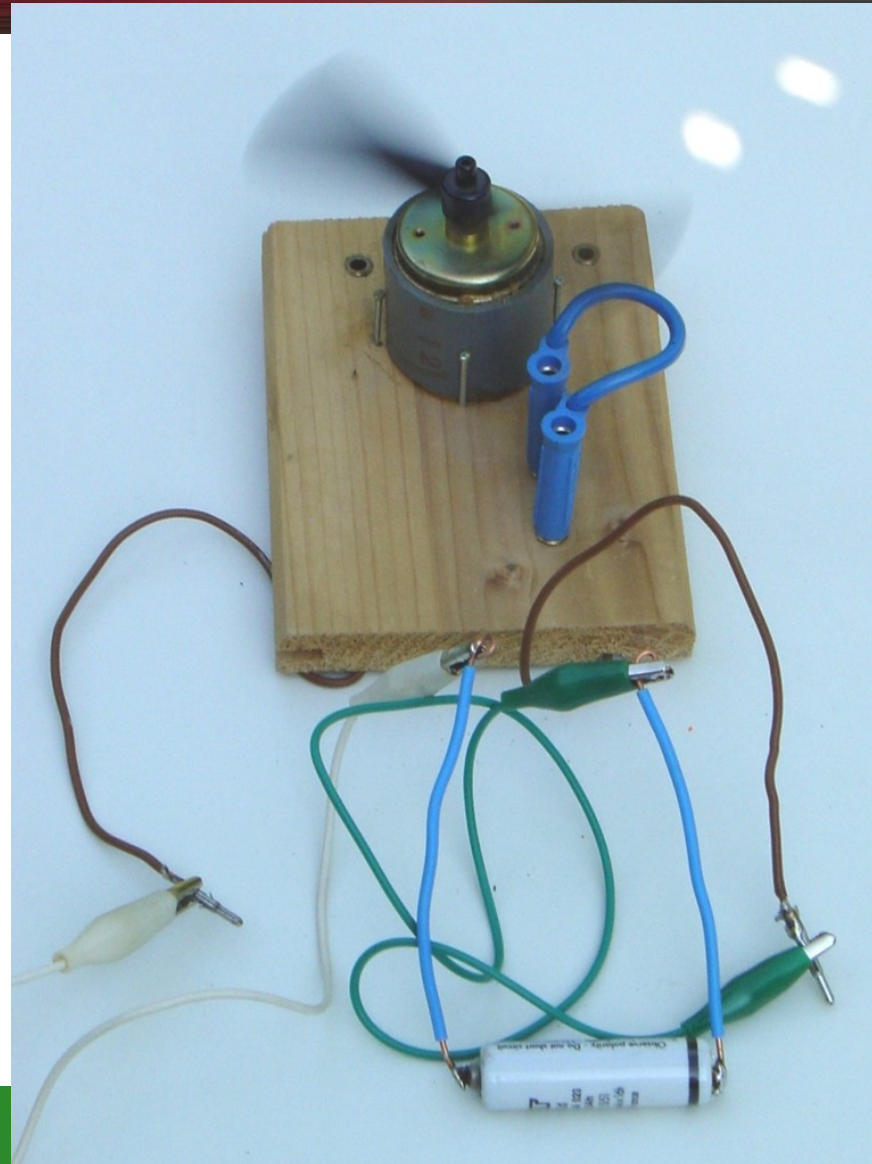

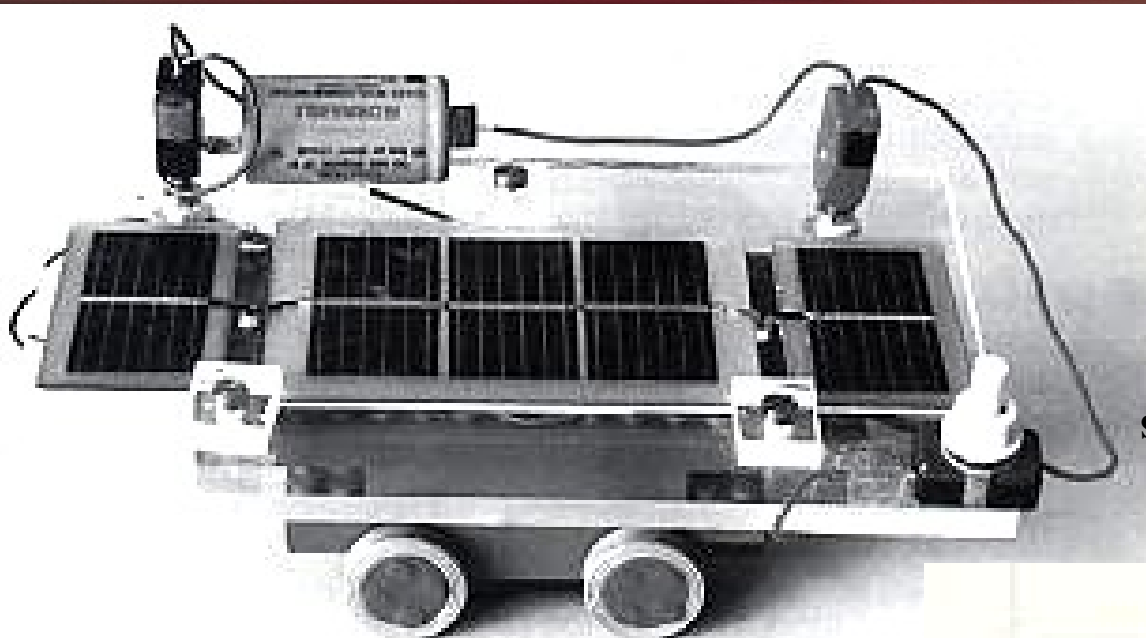


switch to the motor

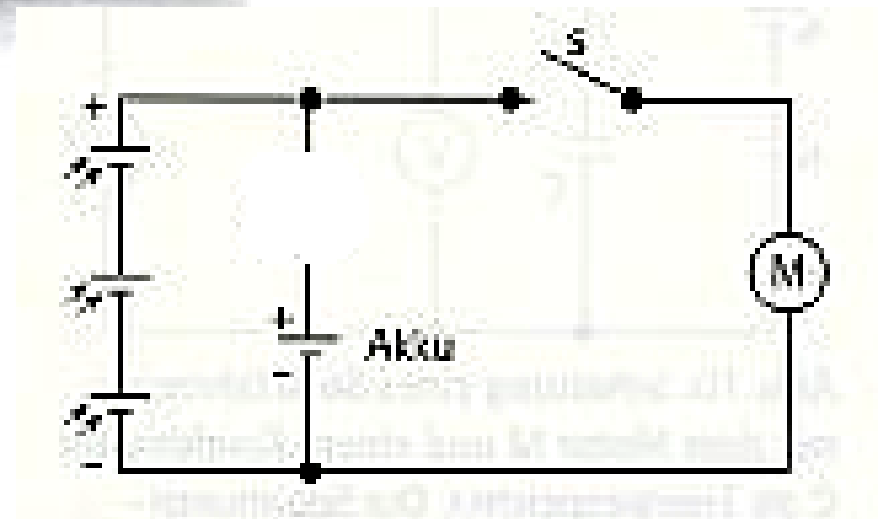


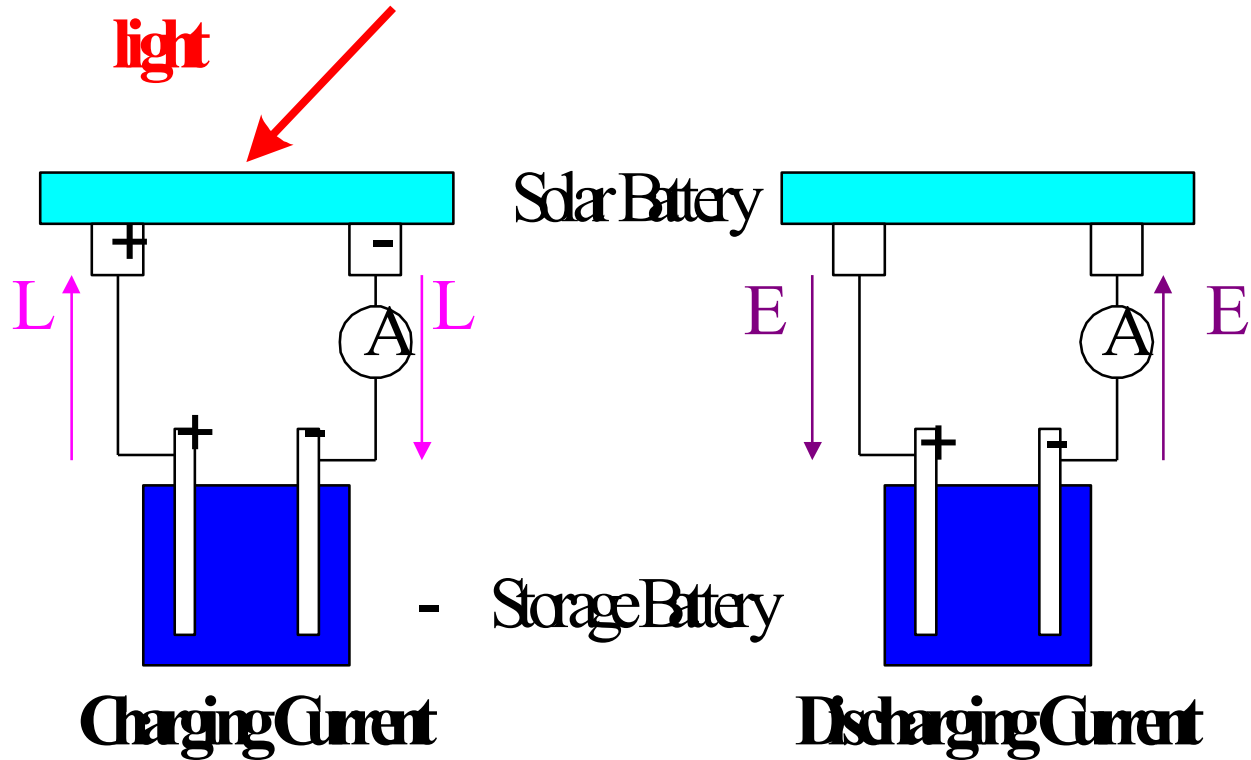

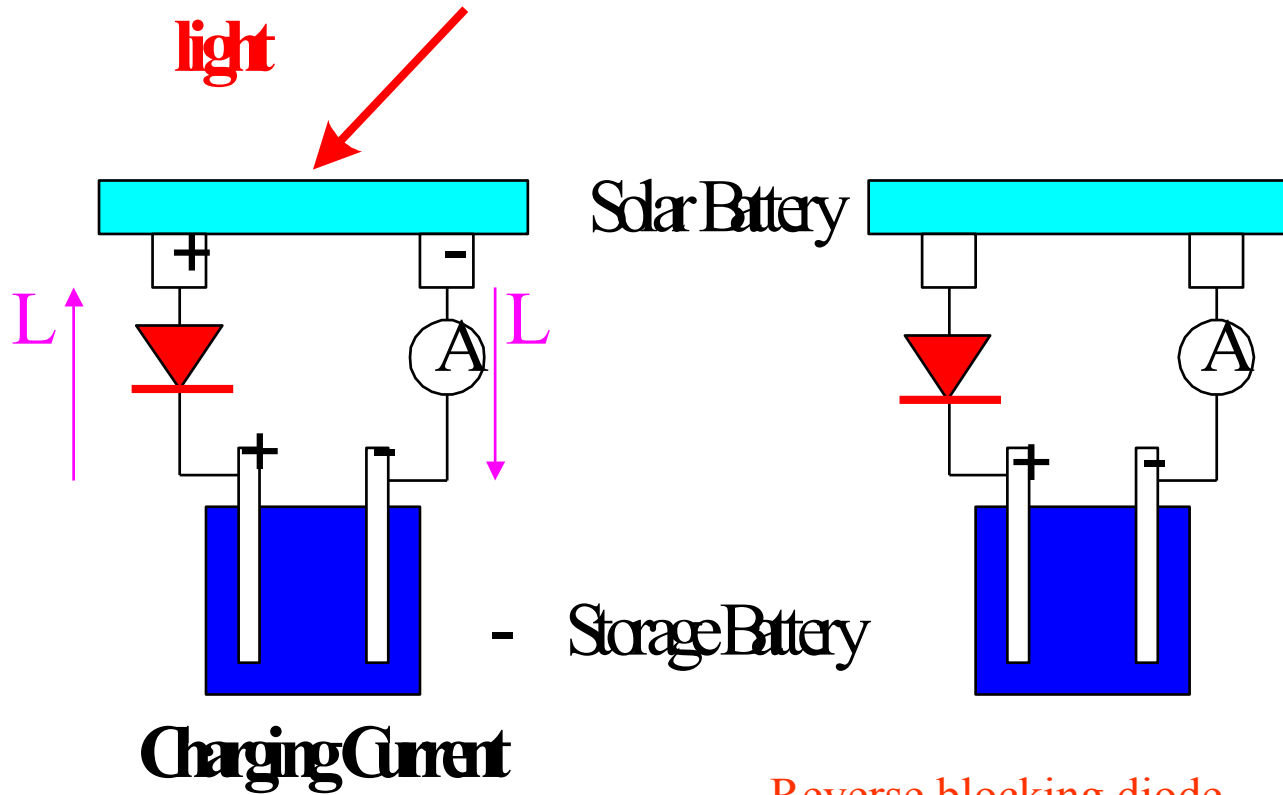For blocking the dischargement a reverse biased diode is used.



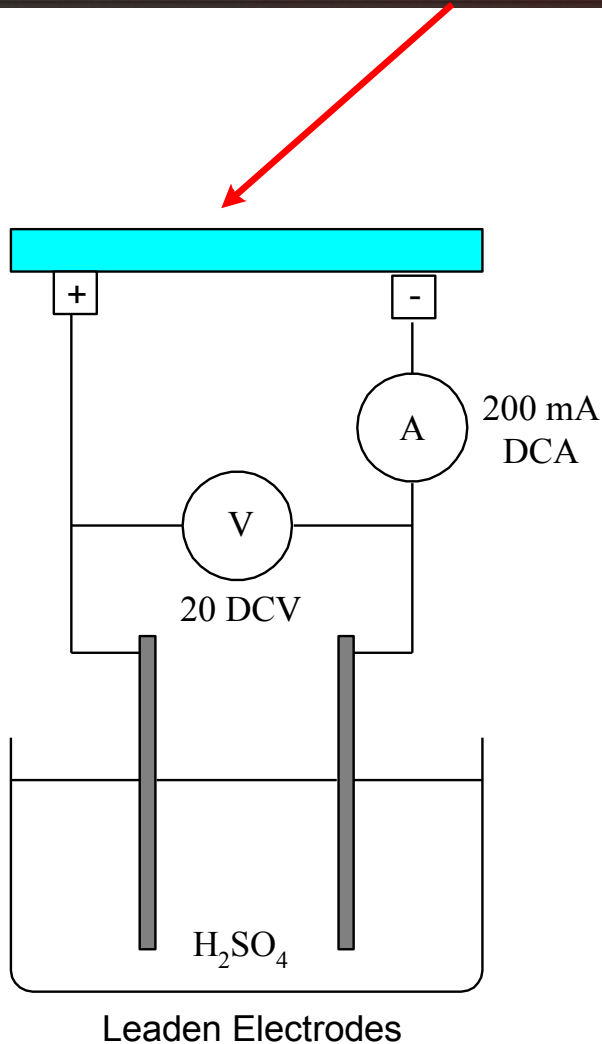Reverse blocking diode
discharging impossible



1. Expose the solar battery to the sun.
2. Read U and I every minute and write it into the schedule.
3. After 10 minutes exchange the solar battery by the electric motor.
4. Read U and I every minute. How long it lasts, that the engine runs ?

See table next page

Charging

Discharging via Engine

T in min	U in V	I in mA	T in min	U in V	I in mA

Measurement of the Irradiance: x W/m² (calibrated solar cell); $x = \dots\dots\dots$ W/m²

Length of the solar battery: $l = \dots\dots\dots$

Width of the solar battery: $b = \dots\dots\dots$

Surface area $A = \dots\dots\dots$ m²

Power irradiated to the surface of the solar battery:

$P = A \cdot x$ W; $P = \dots\dots\dots$ W

Time of exposition: $t = \dots\dots\dots$ h

Energy absorbed: $E = P \cdot t$; $E = \dots\dots\dots$ Wh

The solar battery runs the electric motor:

Voltage at the end of charging: $U_1 = \dots\dots\dots$ V

Intensity of Current: $I = \dots\dots\dots$ A

Time of running: $t_1 = \dots\dots\dots$ h

Voltage at the end of running the motor:

$U_2 = \dots\dots\dots$ V

Power $P_1 = (U_1 - U_2) \cdot I = \dots\dots\dots$ W

Energy needed for running the motor: $E_1 = P_1 \cdot t_1 = \dots\dots\dots$ Wh

$\eta = \frac{E_1}{E}$

Solar Cell	Fill in	Result	Comment
Irradiance in W/m^2		0	
Length of the solar cell in cm			
Width of the solar cell in cm		0	A in m^2
Power irradiated to the solar cell		0	P in W
Time of exposition in min		0	t in h
Engine			
Starting voltage in V		0	U in V
Intensity of Current in mA		0	I in A
End voltage in V		0	U in V
Power of the engine in Watt		0	P_1 in W
Time of running the motor in min		0	t in h
Efficiency		k.A	

Beause of long time measurement: result are average values

Original
and
Source:
Technical
University
Graz
Austria


Stromerzeugung mit der Brennstoffzelle

1. Wasserstoffmoleküle werden an der Anode in Wasserstoffionen und Elektronen zerlegt. Die Anode lädt sich durch den Elektronenüberschuß negativ auf.


2. An der Kathode werden Sauerstoffmoleküle durch Aufnahme von Elektronen in Sauerstoffionen zerlegt. Die Kathode lädt sich durch diesen Elektronenentzug positiv auf.

3. Die positiven Wasserstoffionen werden von den negativ geladenen Sauerstoffionen angezogen. Aus dieser Verbindung entsteht Wasser.

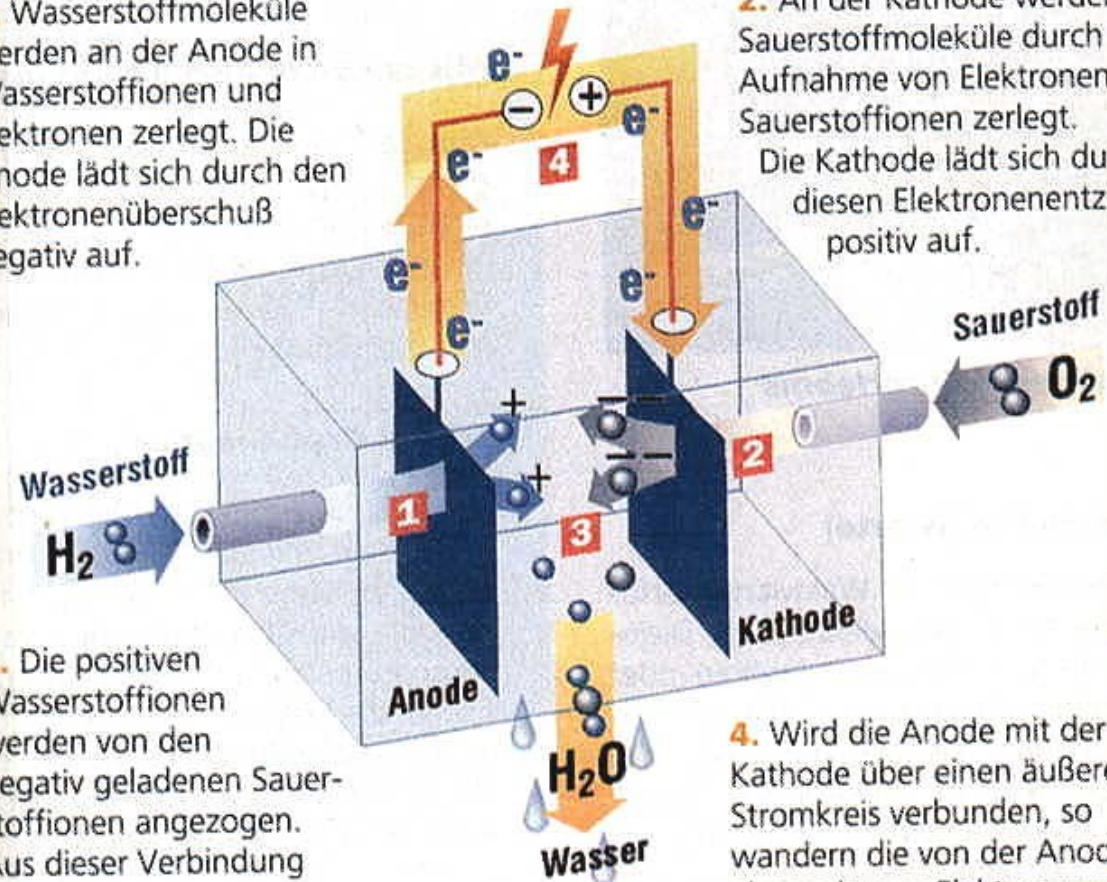4. Wird die Anode mit der Kathode über einen äußeren Stromkreis verbunden, so wandern die von der Anode abgegebenen Elektronen zur Kathode. Es fließt Strom.




APA-Grafik, Quelle: TU Graz

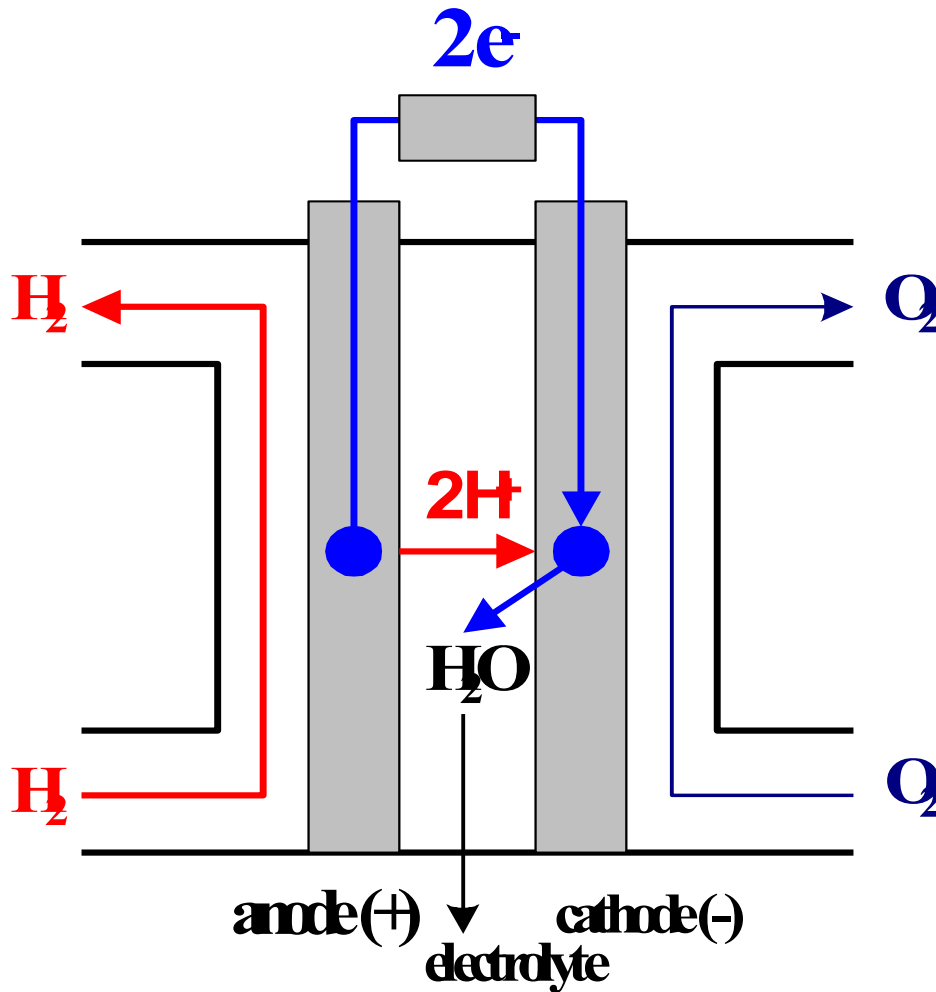


Anode's reaction:



Cathode's reaction:

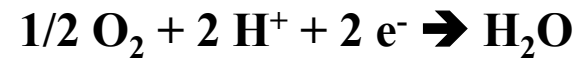


Sum:

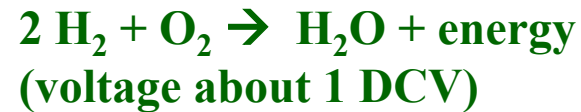






Enthalpy of 286,2 kJ/mol H_2O is set free.


This reaction is called
"Cold Combustion"


Electrolytical Dissociation of Water

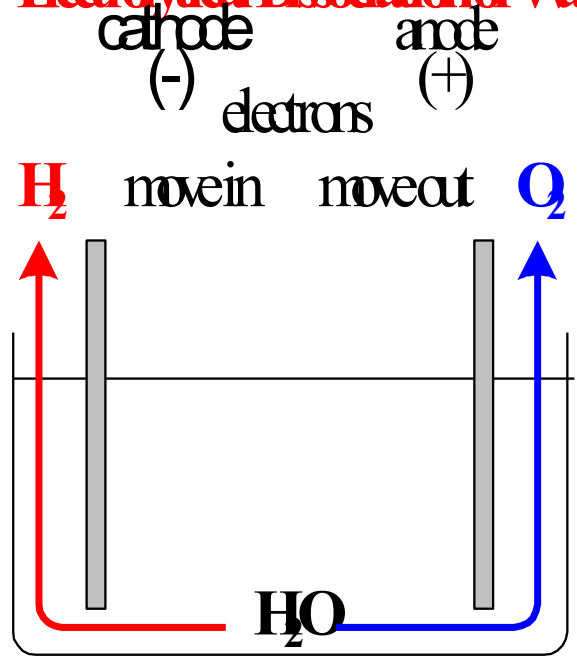

FUEL CELL

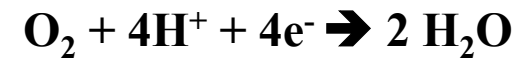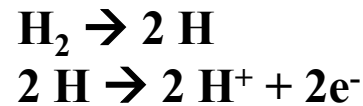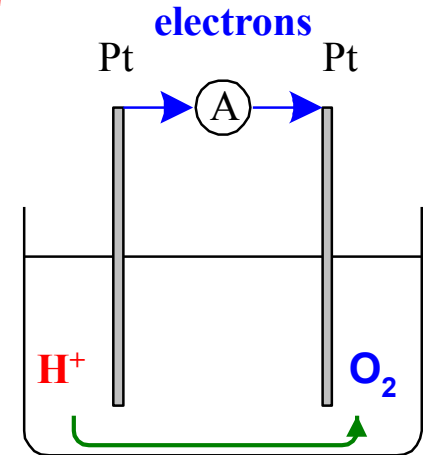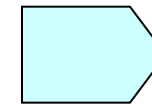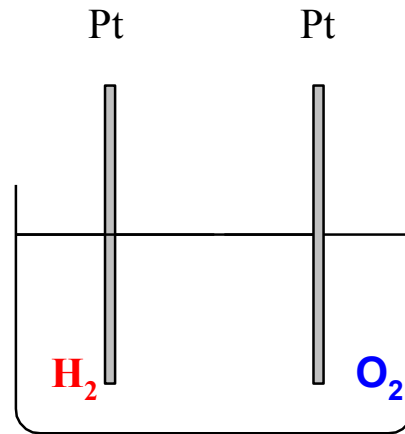

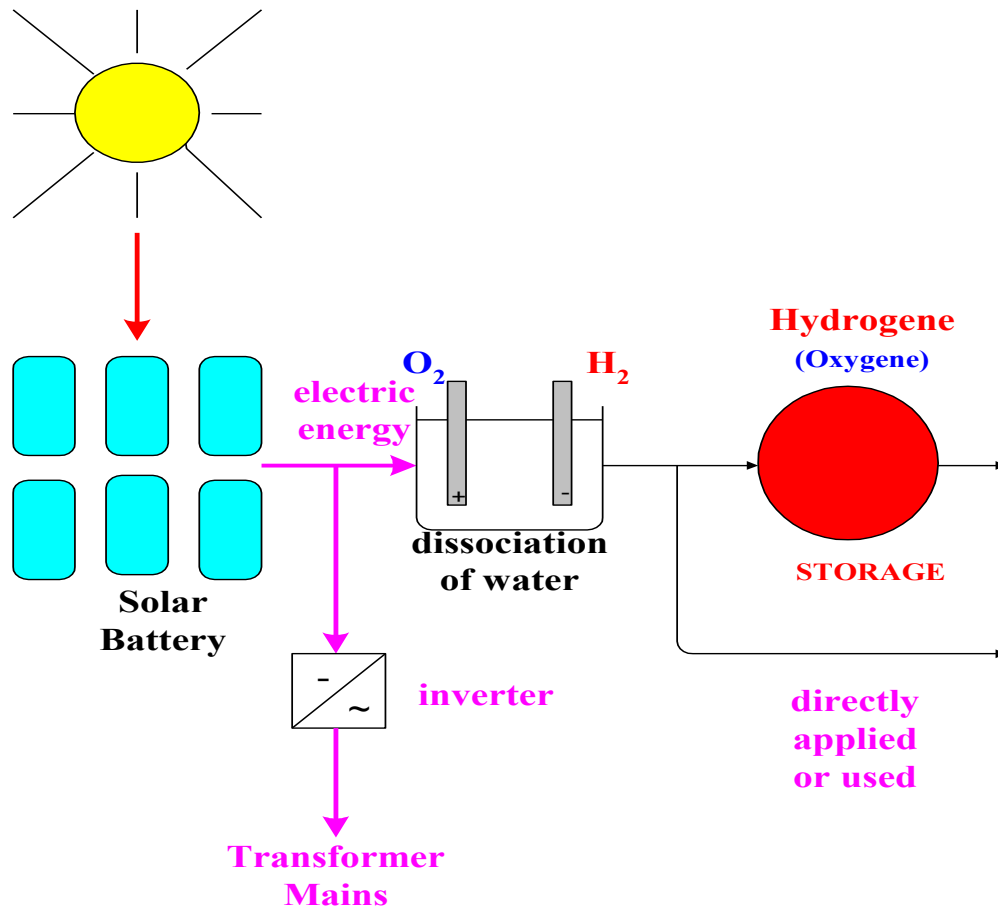


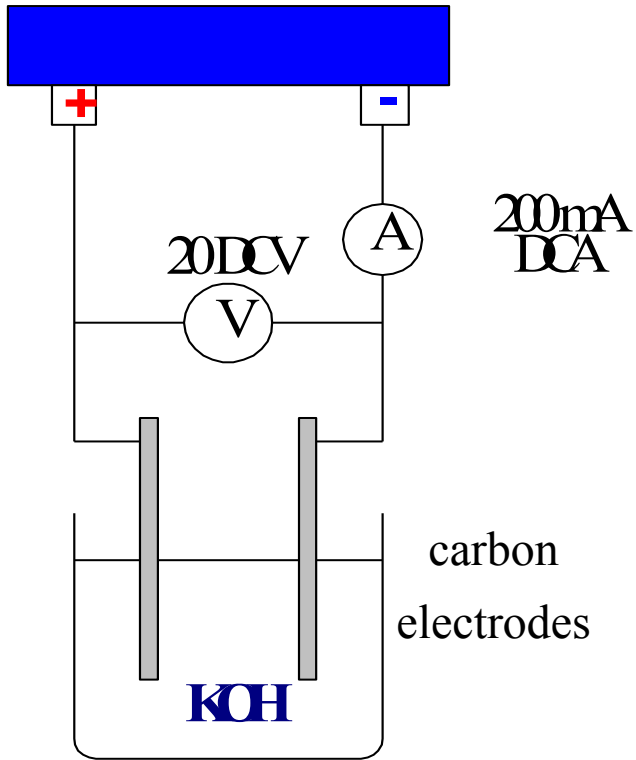


Potassium hydroxide solution (6 m):
11 g sodium hydroxide pastilles to 100 ml water


- ↪ Expose the solar battery to the sun.
- ↪ Observe the gasing - hydrogene and oxygene are developed.
- ↪ After about 10 minutes: separate the solar cell and connect the engine to the carbon electrodes.
- ↪ Read U and I.
- ↪ Observation:
The electric motor firstly runs with high speed, after about one minute with low speed.
- ↪ Voltage and intensity of current are going down.

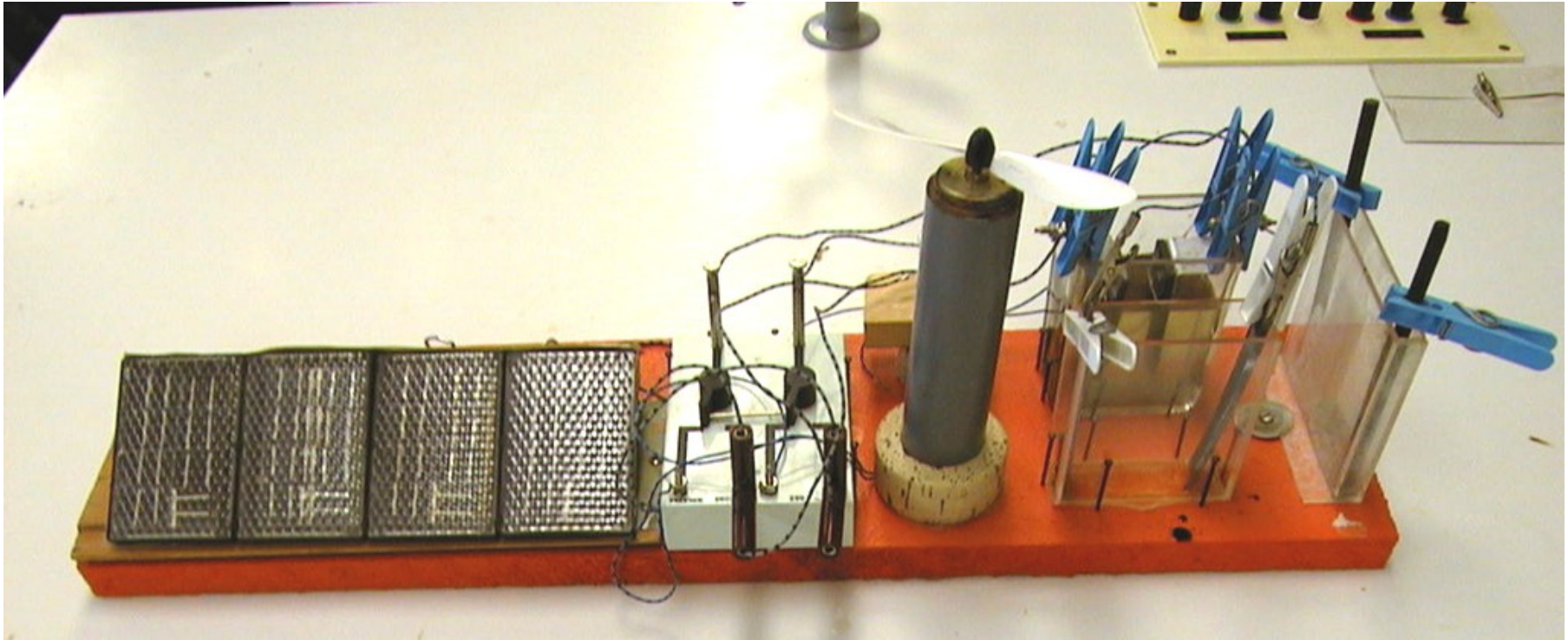Photovoltaic generated hydrogen is turned to energy by means of the FUEL CELL. By this process electric energy is produced.



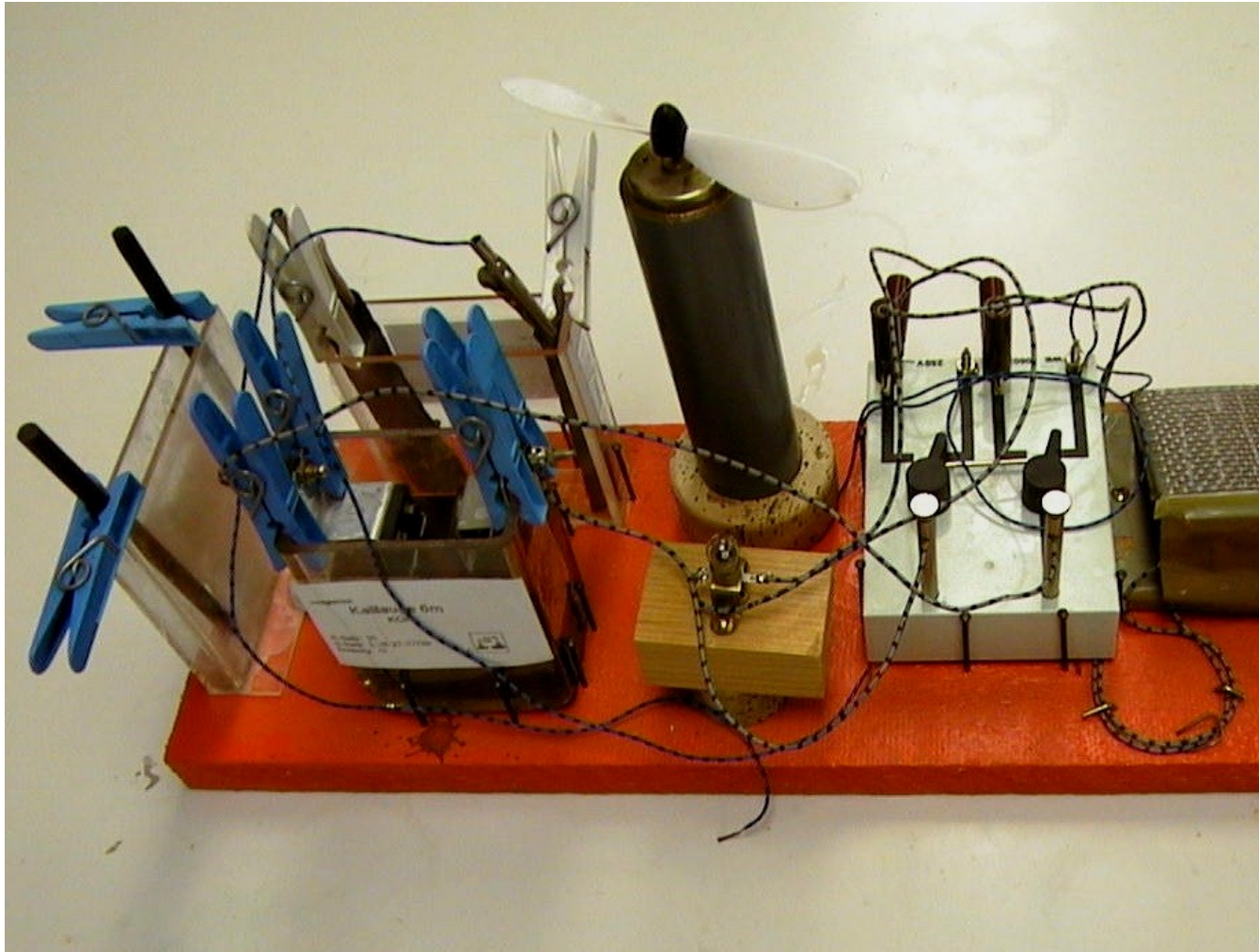

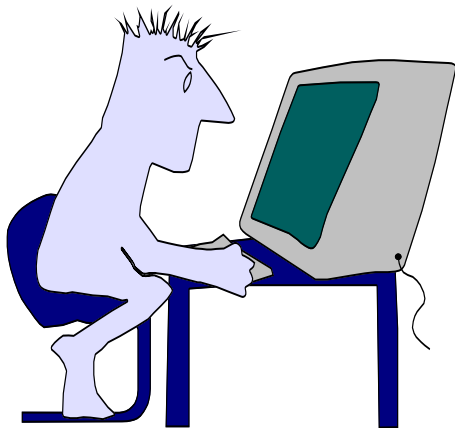Note:
You have to average all values of voltage and intensity of current in calculating the energy the engine has taken.



Fuel Cell	Hit in	Result	Comment
Irradance in W/m^2			0
Length of the solar cell in cm			
Width of the solar cell in cm			0 A/m^2
Power irradiated to the solar cell			0 $P_{in} W$
Time of exposition in min			0 t_{inh}
Engine			
Starting voltage in V			0 $U_{in} V$
Intensity of Current in mA			0 $I_{in} A$
End voltage in V			0 $U_{in} V$
Power of the engine in Watt			0 $P_1 in W$
Time of running the motor in min			0 t_{inh}
Efficiency		kA	

It should be something about some percents...