


**M U N I**  
**F I**

# **PA221: Clock Domain Crossing (CDC): Selected Parts**

# Clock Domains in FPGAs
 
# Clock Domain


- ❑ A group of Flip-Flops (registers) sensitive to the same clock edge (usually rising one) of the same clock signal.
- ❑ A minimal difference of clock signal propagation delay to individual Flip-Flops is expected (minimal skew); i.e. all the registers flip at exactly same time instant.




 
# Why to use more clock signals?

- ❑ In real designs, more clock signals are enforced by system requirements. For example, data acquisitions requires different clock frequency than a standard communication interface.
- ❑ Formally: Globally asynchronous, locally synchronous sequential systems




# Why to use more clock signals?

- ❑ **High clock frequency** is only suitable for critical parts of the design (fast interfaces, fast data processing blocks) because:
  - ❑ **Lower clock frequency** puts **lower requirements** on the programmable interconnect → faster Place and Router procedure (relaxed requirements)
  - ❑ **Lower clock frequency** → **lower dynamic power consumption** (lower thermal dissipation)
 
# Problem: Interfacing between clock domains

- There are usually many data and/or control signals that must pass from one clock domain to another. As clock domains are **asynchronous** to each other, a special care must be taken to avoid **metastability** and **data loss/duplication**.




MUNI  
FI

# Signal Crossing over Clock Domain Boundary

 
# CDC: Common Mistake

- ❑ Data interface between two clock domains having same reference frequency but derived from their own oscillators.



- ❑ The oscillators may have same nominal frequency, but the actual frequency is always slightly different.
- ❑ The difference is not stable over time – clock jitter / wander.
- ❑ When reading data on the receiver side (in FPGA on the example shown) some data words may be duplicated or skipped.


# Possible Effects

 

Skipping some  
data words

$$F_{clkA} > F_{clkB}$$


# Possible Effects

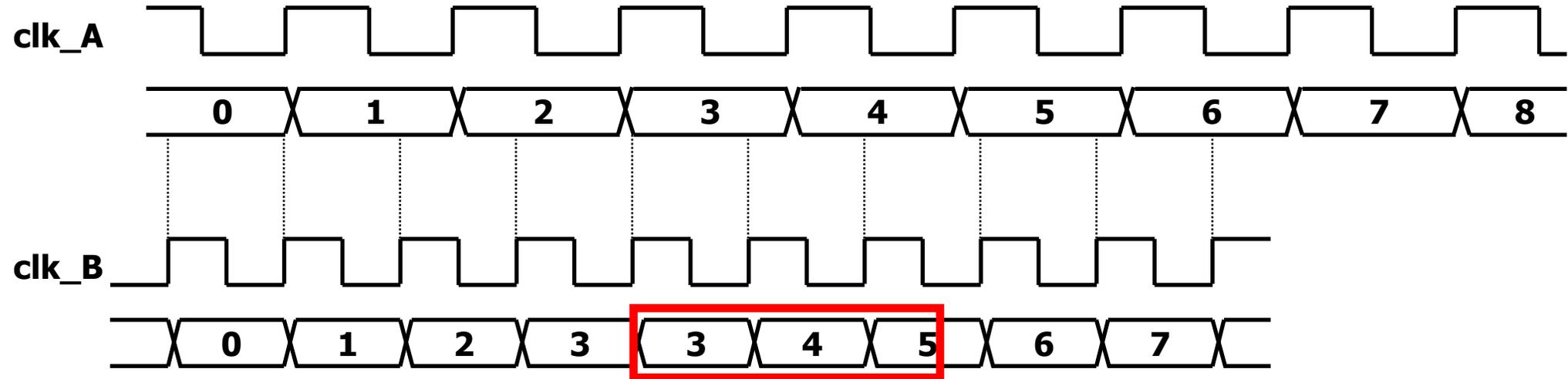

Duplicity of some  
data words

$$F_{\text{clkA}} < F_{\text{clkB}}$$


# Possible Effects

 

$$F_{clkA} < F_{clkB}$$

A metastability can occur when setup/hold time is violated. Invalid (random) data read.


# Possible Effects: Incorrect Bus Data

 
 
# Solution

- ❑ **Simple synchronizer** – suitable for control signals or slow data
- ❑ **Asynchronous FIFO buffer** – with independent clocks at write and read side; suitable for high-speed data transfers


Both solutions can deal with data transfer in one direction only; for bidirectional transfer it is necessary to double each structure.


 
# Solution

- ❑ The actual solution depends on:
  - ❑ Single bit or multiple-bit signal
  - ❑ Clock frequency of source and destination domains
  - ❑ Character of the signal (long or short impulse)
  - ❑ Is a transfer required every clock cycle?


<http://www.fpga4fun.com/CrossClockDomain.html>



MUNI  
FI

# Assignment


# Template

 

# Assignment

- ❑ Observe the cross-domain effects in signaltap
- ❑ Add FIFO on sig\_src to achieve a proper domain crossing
- ❑ Create your own synchronizer for clock enable signal (and signals with similar waveforms)

# Solution

 

# cdc\_flag

## In source domain:

- ❑ Convert the short input pulses to level changes
  - ❑ each impulse will toggle a signal
  - ❑ prolonged signals can cross the clock-domain boundary

## In destination domain:

- ❑ Add two D-flops to remove metastability
- ❑ Edge detector converts the level changes back one-clock-cycle impulses

# cdc\_flag

**Recommended port naming:**

clk\_src



clk\_dst

arst\_src (optional)

arst\_dst (optional)

flag\_src

flag\_dst

  

# cdc\_flag

- ❑ You should add timing constraints → timing analyzer should ignore only the path with cdc\_flag.
- ❑ Other paths will be unaffected and still analyzed for timing correctness.